

Circuits

-

Superposition & Thévenin/Norton equivalence

NYU
上海



SHANGHAI
纽约大学

Spring 2022



Superposition

Linear systems

having one independent source at one time.

Linear circuits

We will analyze linear circuits.

One of the most interesting consequence of linearity is **superposition**

Superposition

The response of a circuit having more than one **independent** source can be obtained by **adding the responses** caused by the **independent sources acting alone**

$$f(x_1 + x_2) = f(x_1) + f(x_2)$$

$$f(ax_1) = a f(x_1)$$

$$\begin{aligned} v &= \frac{V}{R} \\ &= \frac{V_1 + V_2}{R} \\ &= \frac{V_1}{R} + \frac{V_2}{R} \end{aligned}$$


Superposition

上海交通大学
SHANGHAI JIAO TONG UNIVERSITY
GHAI

Turning off sources

Since the response of the circuit can be obtained by superposition, **all the independent sources but one have to be turned off** at a time


Voltage source turned off (zeroed out)

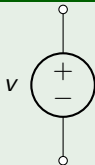

When turned off \Rightarrow



Current source turned off (zeroed out)

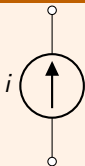


When turned off \Rightarrow



Superposition



Determine the voltage v

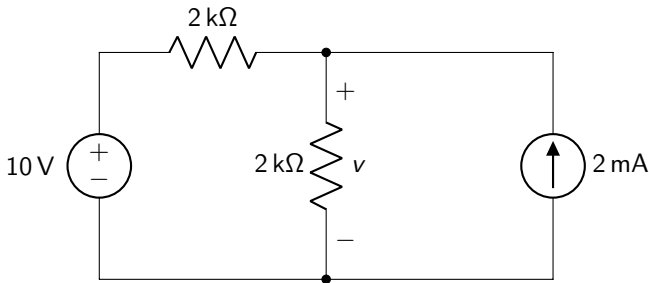

Nodal analysis (for example):

$$\blacksquare 2\text{ mA} + \frac{10\text{ V} - v}{2\text{ k}\Omega} = \frac{v}{2\text{ k}\Omega}$$


$$\blacksquare v = 7\text{ V}$$

Superposition



When there're too many independent sources, superposition


Analysis 1

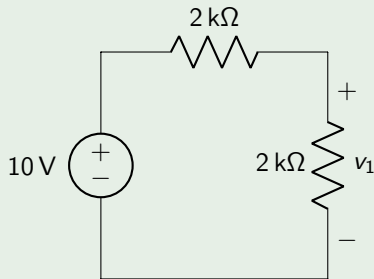

■ $v_1 = 5\text{V}$

Analysis 2

's not helpful

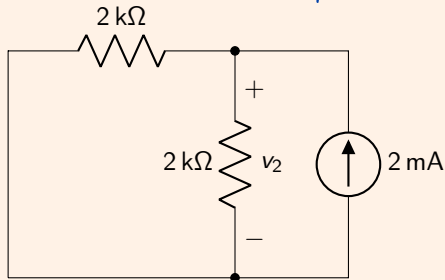


■ $v_2 = 2\text{V}$

Superposition


■ $v = v_1 + v_2 = 7\text{V}$

Examples


Determine the voltage across each current source.

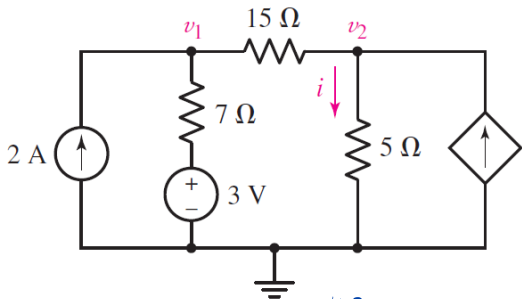

Analysis 1

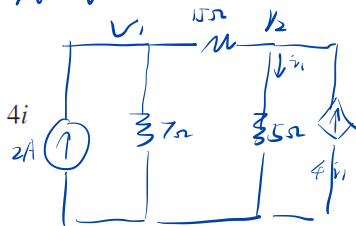

Analysis 2

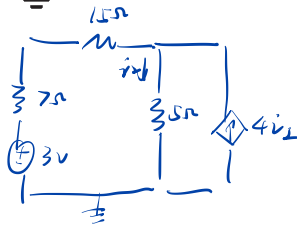

Then use
Nodal
Analysis

Superposition



上海纽约大学
NYU SHANGHAI

Summary

- Superposition relies on linearity
- Analyze as many circuits as there are **independent sources**
- Dependent sources are never zeroed out
- More circuits to analyze, sometimes leading to more equations. . .
- But the different circuits are also simpler to analyze, with simpler equations



Source transformation



Concept

A voltage source with a resistor in series is **equivalent** to a current source with a resistor in parallel

Equivalence

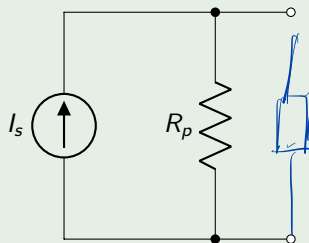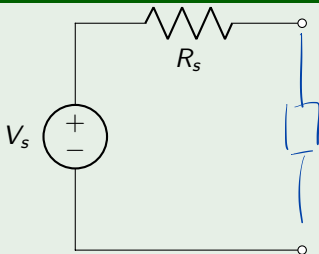



Validity

The equivalence holds if both circuits have the **same voltage-current relationship** at their terminals

Source transformation



上海纽约大学
NYU SHANGHAI

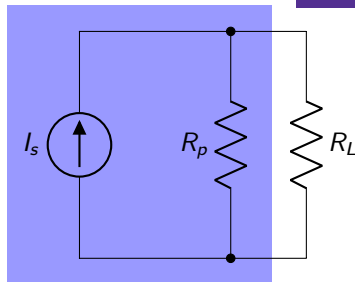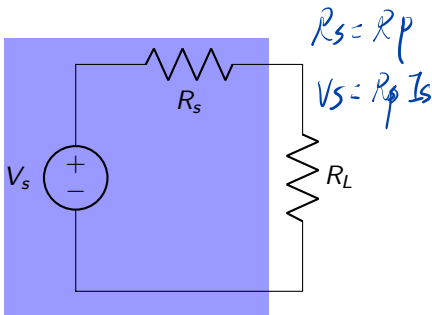

Double check the polarity. check the current direction

Terminal

$$\blacksquare V = \frac{R_L}{R_s + R_L} V_s$$

$$\blacksquare I = \frac{V_s}{R_s + R_L}$$

Terminal

$$\blacksquare V = \frac{R_L}{R_p + R_L} R_p I_s$$

in the load

$$\blacksquare I = \frac{R_p I_s}{R_p + R_L}$$


Source transformation



上海纽约大学
NYU SHANGHAI

the head of the current source should correspond to the positive sign of the voltage source

Equivalence

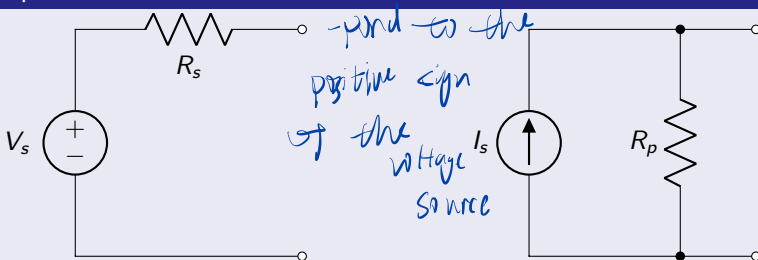

Equivalent when:


- $R_s = R_p = R$
- $V_s = RI_s$

what's the role of the polarity of the voltage source & the direction of the current source

Source transformation



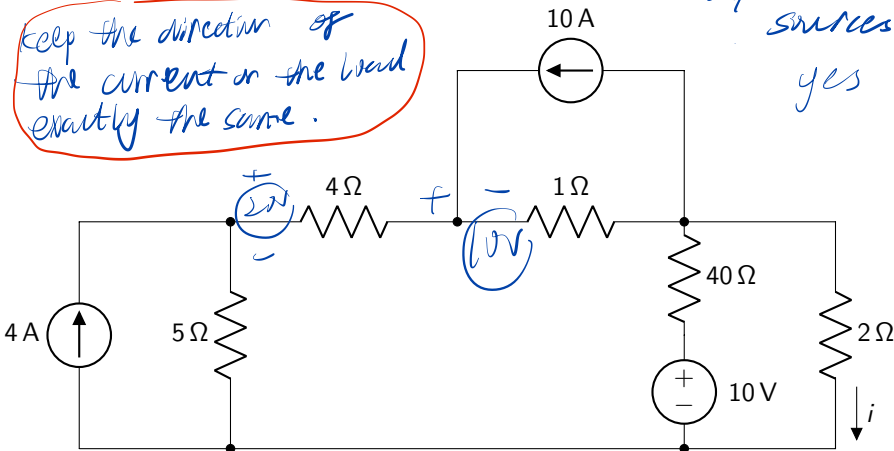Can we apply source transformation to dependent sources?
 Apply multiple source transformation to determine i
 keep the direction of the current on the load exactly the same.
 yes




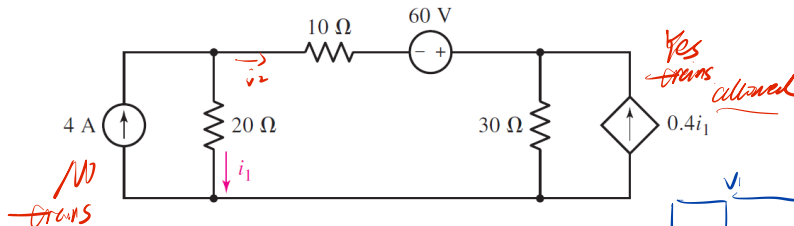Examples




上海纽约大学
NYU SHANGHAI

Determine the source transformation should be performed or not.



$80V$ \oplus \ominus

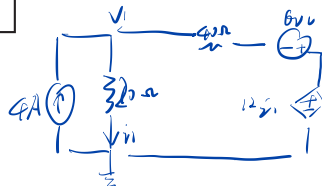$20\Omega \rightarrow i_2$ this is not i_1 .
it's the current on
the top branch



Thévenin equivalent circuit



上海 纽约 大学
NYU SHANGHAI

Theorem

A **two-terminal linear circuit**, constituted of sources and resistors, is equivalent to a **voltage source in series with a resistor**

Application



Usually, it allows us to simplify the analysis of a circuit when only a few values need to be determined

for example, previous example. . .

Thévenin equivalent circuit

上海交通大学
SJTU

Equivalence

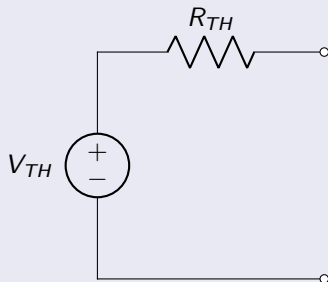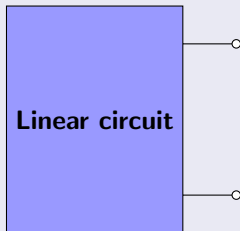

How to determine the Thévenin equivalence?

Several methods:

- 1 Evaluate the **open-circuit voltage**
- 2 Evaluate the **short-circuit current**
- 3 Evaluate the **resistor value** by turning off every independent source




上海纽约大学
NYU SHANGHAI

Thévenin equivalent circuit

① V_{ab} . Req

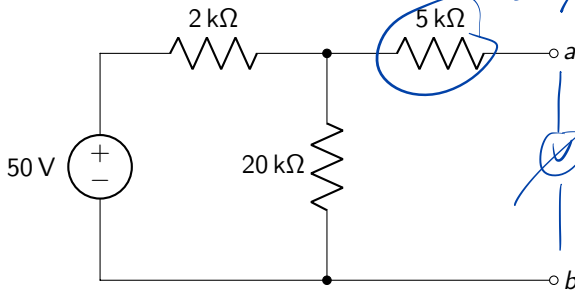② I_{ab} . Req. Source Transformation
Find the Thévenin equivalence (terminal ab)




no voltage drop across the $5\text{ k}\Omega$ resistor.

Thévenin equivalent circuit

上海纽约大学
NYU SHANGHAI

① Evaluate the **open-circuit voltage**

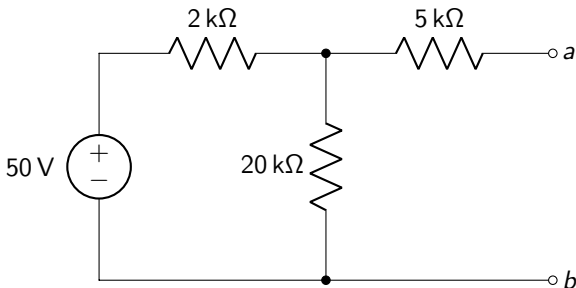

(no current in 5 k Ω resistor)


$$V_{OC} = \frac{20}{22} 50 \text{ V} = 45.45 \text{ V}$$

Thévenin equivalent circuit



上海纽约大学
NYU SHANGHAI

② Evaluate the **short-circuit current**

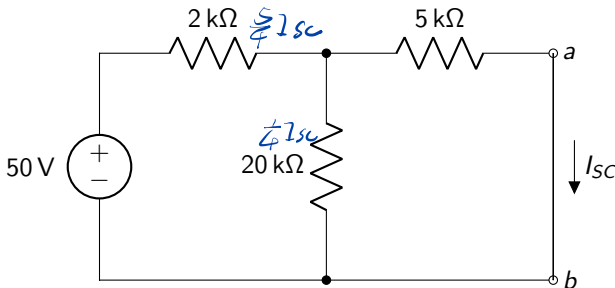


(current $I_{SC}/4$ in the $20\text{ k}\Omega$ resistor)

$$50\text{ V} = \left(\frac{5}{4} 2\text{ k}\Omega + 5\text{ k}\Omega\right) I_{SC} \quad \Rightarrow \quad I_{SC} = 6.67\text{ mA}$$

Thévenin equivalent circuit

上海纽约大学
NYU SHANGHAI

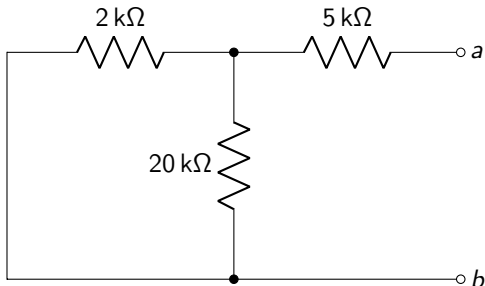- ③ Evaluate the **resistor value** by turning off every independent *all of them at the same time* source





$$R_{eq} = 5 \text{ k}\Omega + \frac{2 \text{ k}\Omega \cdot 20 \text{ k}\Omega}{22 \text{ k}\Omega} = 6.82 \text{ k}\Omega$$



Thévenin equivalent circuit

Equivalence

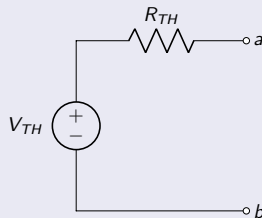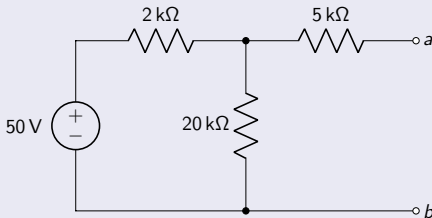

Values

Actually, only 2 experiments are necessary:

- $V_{TH} = V_{OC} = 45.45 \text{ V}$

- $R_{TH} = R_{eq} = 6.82 \text{ k}\Omega$

- $V_{TH} = R_{TH} \cdot I_{SC}$ *Source Transformation*

Thévenin equivalent circuit



上海 纽约 大学
NYU SHANGHAI

Presence of dependent sources

It seems that determining the **open-circuit voltage** and the **equivalent resistance** (when independent sources are turned off) is the most straightforward technique to find Thévenin equivalence

But, what happens when we have dependent sources?

Answer: connect a source to the terminals

- connect a voltage source (or a current source) to the terminals
- the source value can be **any value**

- $R_{eq} = \frac{V}{I}$

Thévenin equivalent circuit




上海纽约大学
NYU SHANGHAI


independent sources are zeroed out

Determining R_{eq} with dependent sources

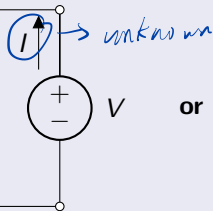Linear circuit
Independent
sources are off



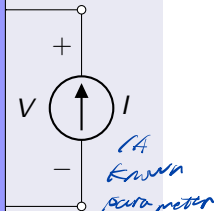Linear circuit
Independent
sources are off



R_{eq} with dependent sources

Beware!

With dependent sources, it is possible to find **negative values** for R_{eq} !!!

Due to dependent sources, equivalent resistance may be a negative value





上海纽约大学
NYU SHANGHAI

Thévenin equivalent circuit

Find the Thévenin equivalence (terminal ab)

Source Transformation to simplify first.

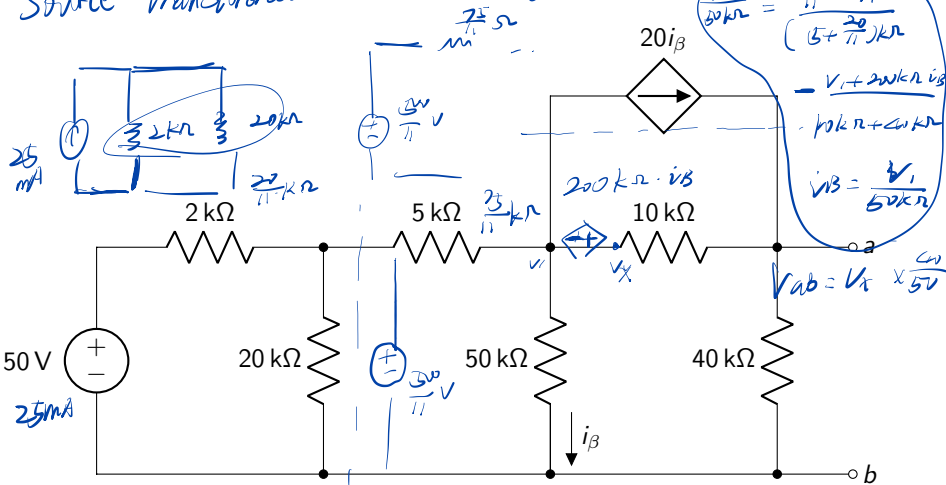

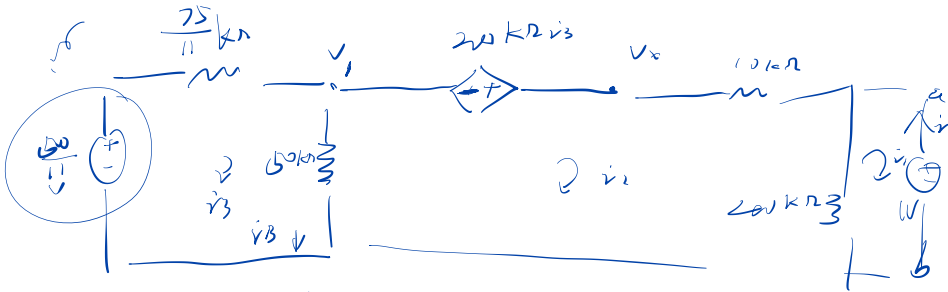

$$R_{ab} = \frac{1\text{V}}{i}$$

$$1\text{V} = 20\text{ k}\Omega \cdot (i_1 - i_2)$$

Norton equivalent circuit

上海 纽约 大学
NYU SHANGHAI

Theorem

A **two-terminal linear circuit**, constituted of sources and resistors, is equivalent to a **current source in parallel with a resistor**

Application



Usually, it allows us to simplify the analysis of a circuit when only a few values need to be determined

for example, previous example. . .

Norton equivalent circuit



Equivalence

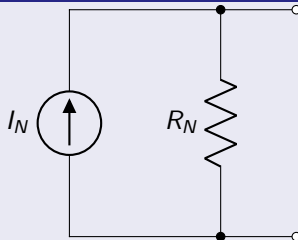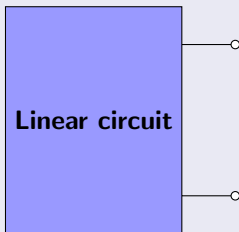

How to determine the Norton equivalence?



Several methods:

- 1 Evaluate the **open-circuit voltage**
- 2 Evaluate the **short-circuit current**
- 3 Evaluate the **resistor value** by turning off every independent source

Norton equivalent circuit



Equivalence

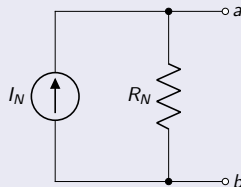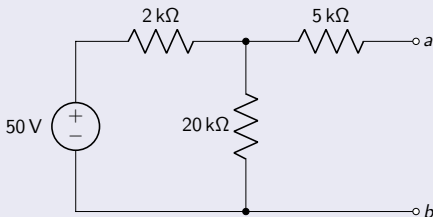

Values

Actually, only 2 experiments are necessary:

- $I_N = I_{SC} = 6.67 \text{ mA}$
- $R_N = R_{eq} = 6.82 \text{ k}\Omega$
- $I_N = \frac{V_{OC}}{R_N}$

Norton equivalent circuit

上海纽约大学
NYU SHANGHAI

Find the Norton equivalence (terminal ab)

