

Circuits

-

Nodal and Mesh analysis



Spring 2022

Analysis



Until now

Each circuit is unique and the analysis was generally a mix between:

- KCL
- KVL
- Ohm's law

Approach

Usually, we need some **experience** to know when to apply which law. . .

Methodical approach

We are gonna see 2 generic approaches:

- Nodal analysis
- Mesh analysis

Nodal Analysis



Principle

Nodal analysis is based on KCL

Essential node: definition

An essential node is a point at which **3 or more elements** are connected to

Reference node

Nodal analysis will introduce a reference node: voltages will be defined from that node


the earth ground

Nodal Analysis

上海纽约大学
NYU SHANGHAI

How many nodes? 5

How many essential nodes? 3

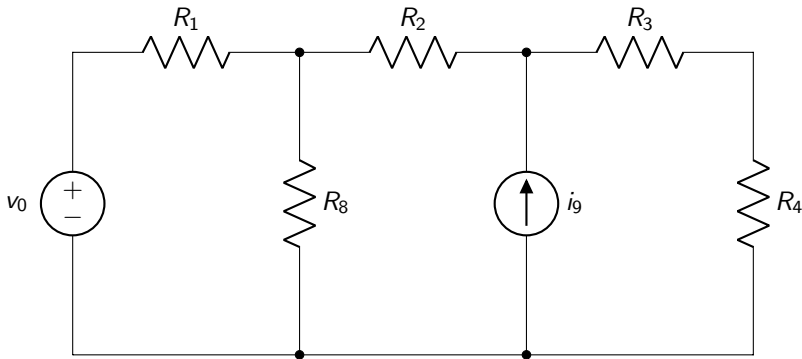

Nodal Analysis

上海纽约大学
NYU SHANGHAI

Pick a reference node

Usually, the analysis is **easier** if you choose the node that **interconnects the most branches**

- mandatory to be an essential node
- classically located at the bottom of the circuit
- use a symbol similar to **ground**


Symbols for ground



Nodal Analysis

上海纽约大学
NYU SHANGHAI

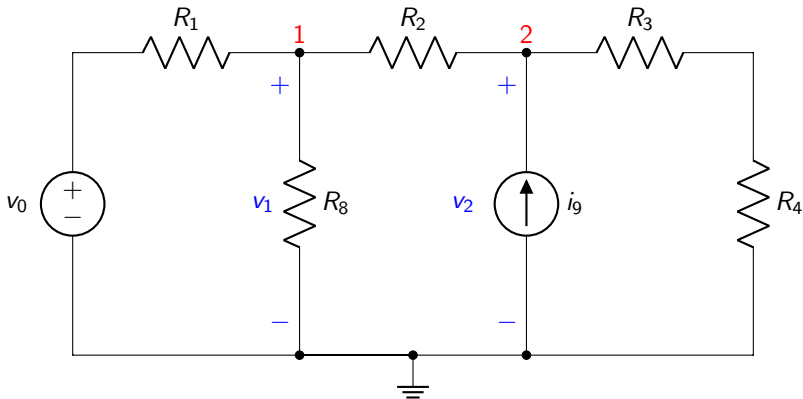Place the reference node and label the essential nodes




Nodal Analysis

上海纽约大学
NYU SHANGHAI

Equivalent representation

we use ohm's law
to represent
the current

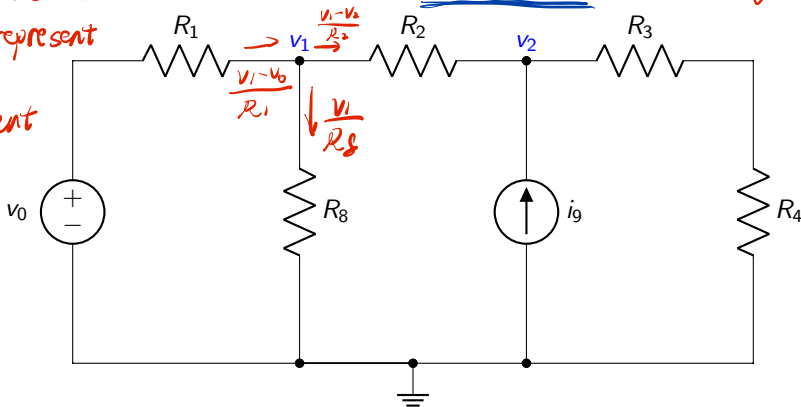when applying Nodal Analysis
we should label voltage at the
essential nodes. instead of currents



Nodal Analysis



Strategy

- Express the **currents** as functions of the **voltages** at essential nodes
- and then **apply KCL** at each essential node (excluding the reference node)

System of equations

It should lead to a system of N equations with N unknowns

N is the number of essential nodes (excluding the reference node), and the unknowns are the **voltages at these nodes**


Nodal Analysis



上海纽约大学
NYU SHANGHAI

the direction of current
at every

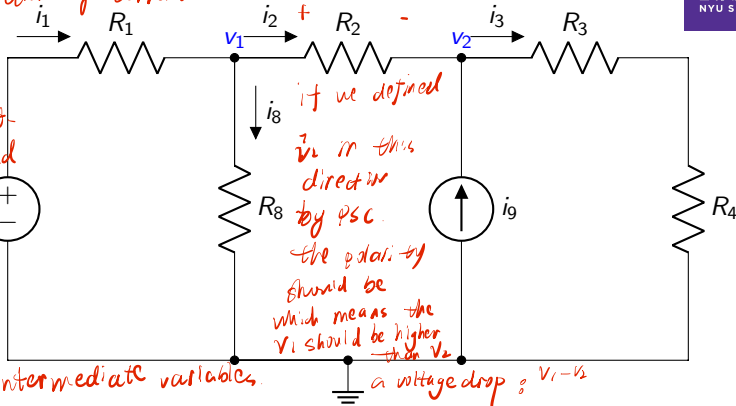branch's
very important
& should
be
labelled



if we defined
 i_2 in this
direction
by psc.

the polarity
should be
which means the
 v_1 should be higher
than v_2

a voltage drop: $v_1 - v_2$

just intermediate variables.

$$i_1 = \frac{v_0 - v_1}{R_1} \quad i_2 = \frac{v_1 - v_2}{R_2}$$


not unknowns.

$$i_3 = \frac{v_2}{R_3 + R_4}$$

$$i_8 = \frac{v_1}{R_8}$$

$$\blacksquare i_1 = i_2 + i_8$$


$$\blacksquare i_2 + i_9 = i_3$$

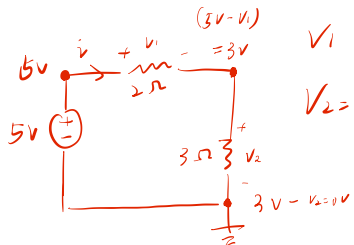

$$V_1 = 5V \cdot \frac{2\Omega}{5\Omega} = 2V$$

$$V_2 = 3V$$

Nodal Analysis

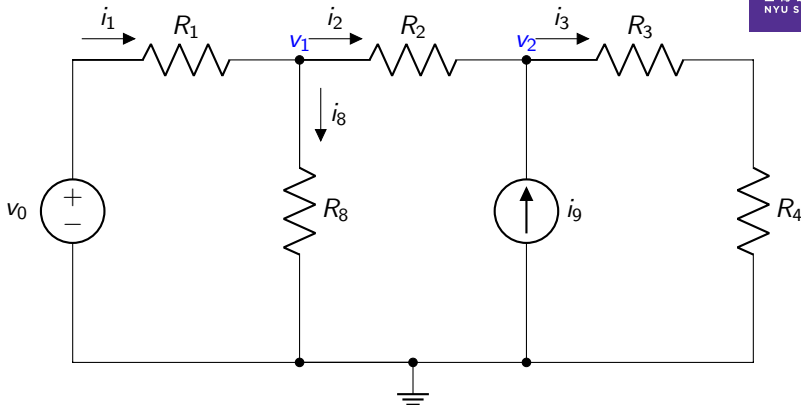上海 纽约 大学
NYU SHANGHAI

$$\blacksquare \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_8} \right) \cdot v_1 - \frac{1}{R_2} \cdot v_2 = \frac{v_0}{R_1}$$

$$\blacksquare -\frac{1}{R_2} \cdot v_1 + \left(\frac{1}{R_3 + R_4} + \frac{1}{R_2} \right) \cdot v_2 = i_9$$

Nodal Analysis

上海纽约大学
NYU SHANGHAI

Summary

7 steps to follow:

- 1 Identify essential nodes
- 2 Pick a reference node *(essential. bottom, most branches)*
- 3 Label other essential nodes with voltages
- 4 Apply KCL to these nodes
- 5 Determine the currents as functions of nodal voltages
- 6 Solve linear system of equations for the voltages
- 7 Post-process any variable of interest


equations = # essential nodes we label

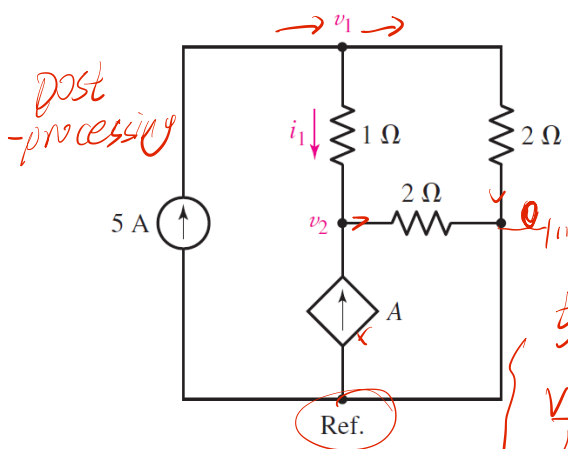Examples



上海交通大学
SJTU

Determine the voltage v_1 if A is (a) $2i_1$; (b) $2v_1$.



We only need to label two essential nodes

we need 2 equations help us decide the # of equations needed.

$$5A = \frac{V_1 - V_2}{1\Omega} + \frac{V_1}{2\Omega}$$

$$\frac{V_1 - V_2}{1\Omega} + X = \frac{V_2}{2\Omega}$$

$$X = \begin{cases} 2i_1 = 2 \frac{V_1 - V_2}{1\Omega} \\ 2v_1 \end{cases}$$

Supernode

上海纽约大学
NYU SHANGHAI

Problem with nodal analysis

If essential nodes (excluding the reference node) are connected through a branch with a single voltage source (dependent or independent), the current in that branch cannot be expressed simply as a function of node voltages.


We can't decide the current on that branch

Solution

Get rid of the current variable in that branch by applying KCL to a **supernode**

An extra equation is then required (voltage equation for that branch)


Supernode

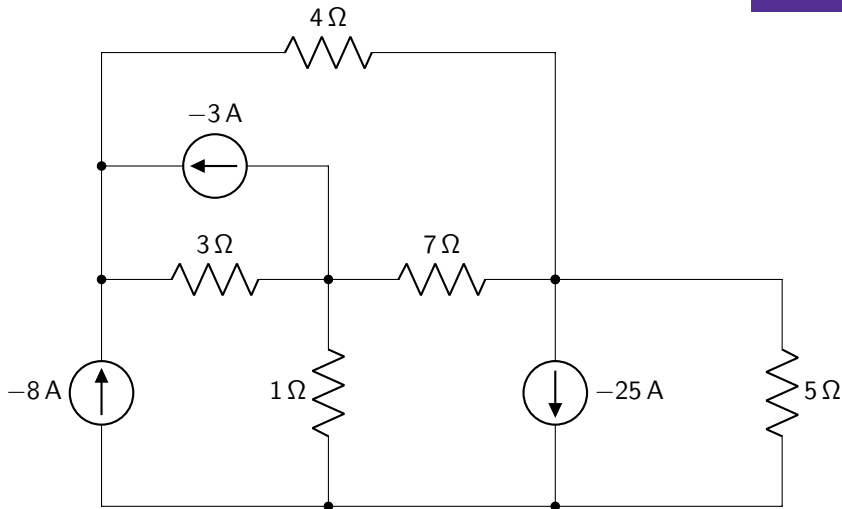上海 纽约大学
NYU SHANGHAI

Supernode



上海纽约大学
NYU SHANGHAI

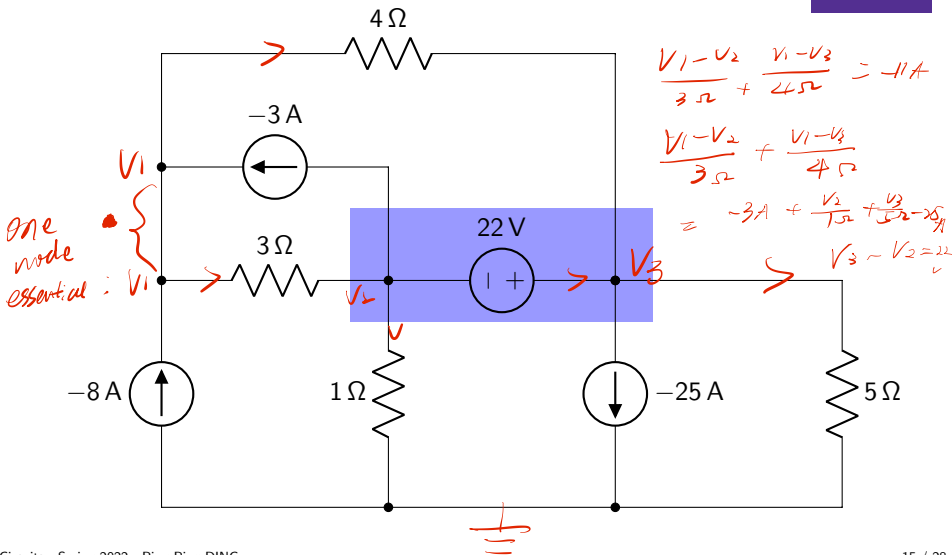


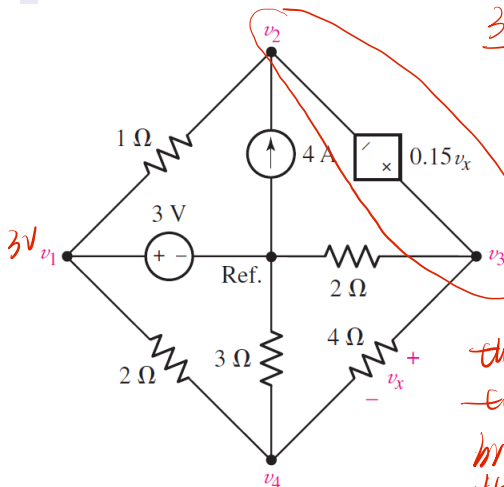Examples



上海交通大学
GHAI

Determine the nodal voltages in the circuit.



$$\frac{3-v_2}{1} + 4 + \frac{-v_3}{2} + \frac{v_4-v_3}{4} = 0$$

$$\frac{3-v_4}{2} + \frac{-v_4}{3} + \frac{v_3-v_4}{4} = 0$$

$$v_3 - v_2 = 0.15v_x$$

$$= (v_3 - v_4) \times 0.15$$

the supernode need
to include the total
branch having the
voltage sources.

Mesh Analysis

上海纽约大学
NYU SHANGHAI

Principle

Mesh analysis is based on KVL

Mesh: definition

A mesh is a loop that does not enclose another loop

Virtual currents


The strategy for mesh analysis is to consider that some **virtual mesh currents** are flowing through each mesh.

The **unknowns** for Mesh Analysis are these virtual mesh currents

Mesh Analysis

上海纽约大学
NYU SHANGHAI


How many loops? 6
How many meshes? 3

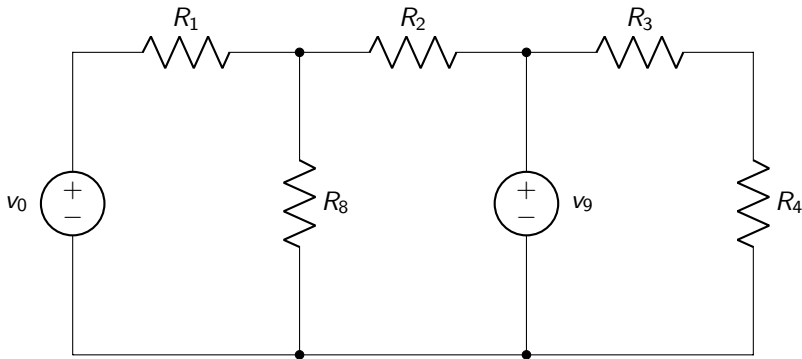

Mesh Analysis

上海纽约大学
NYU SHANGHAI*virtual currents*

Labeling the circuit with mesh currents

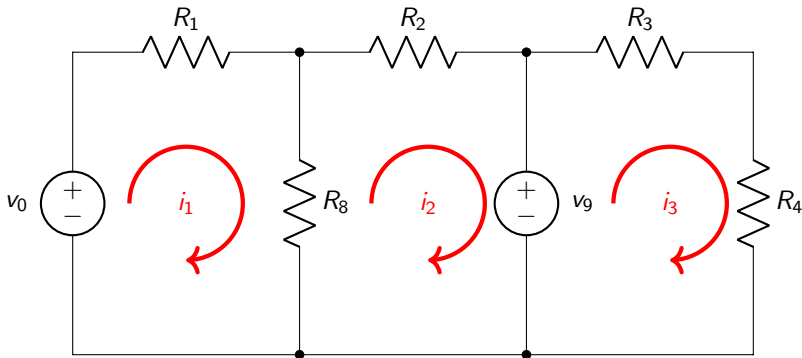meshes = min # equations of analyzing by KVL.

Mesh Analysis

上海纽约大学
NYU SHANGHAI

Applying KVL for each mesh

- $v_0 - R_1 \cdot i_1 - R_8 \cdot (i_1 - i_2) = 0$
- $R_8 \cdot (i_1 - i_2) - R_2 \cdot i_2 - v_9 = 0$
- $v_9 - (R_3 + R_4) \cdot i_3 = 0$

System of equations

- $(R_1 + R_8) \cdot i_1 - R_8 \cdot i_2 = v_0$ *the unknowns are virtual currents.*
- $R_8 \cdot i_1 - (R_2 + R_8) \cdot i_2 = v_9$
- $(R_3 + R_4) \cdot i_3 = v_9$

Mesh Analysis

上海纽约大学
NYU SHANGHAI

Summary


6 steps to follow:

- ① Check if you have a **planar circuit**
- ② Identify and label the virtual currents for each mesh
- ③ Apply KVL to these meshes
- ④ Determine the voltages as functions of mesh currents
- ⑤ Solve linear system of equations for the currents
- ⑥ Post-process any variable of interest

Mesh Analysis

上海 纽约 大学
NYU SHANGHAI

Planar

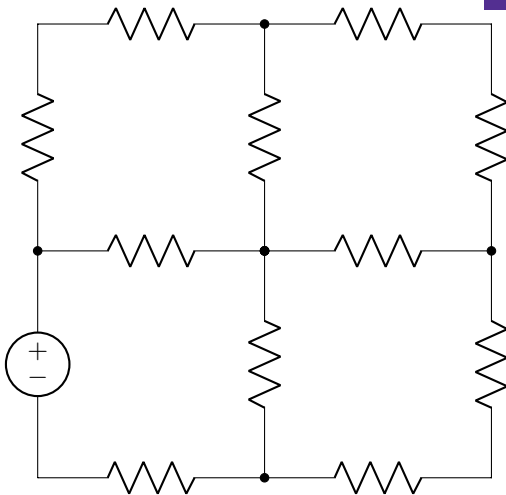


Mesh Analysis

上海纽约大学
NYU SHANGHAI

*Mesh's a property of planar circuit,
and is undefined for a non-planar circuit.*


Planar

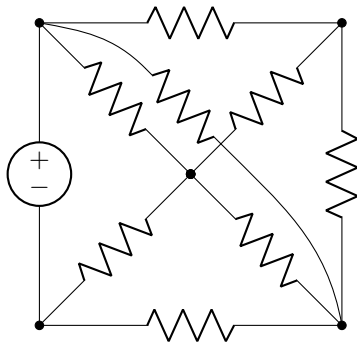

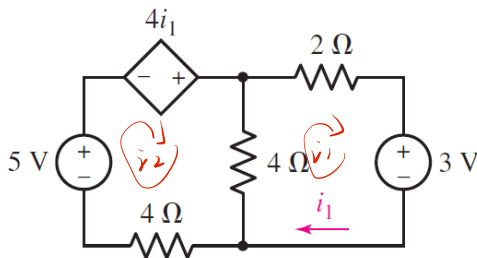Examples



Determine the current i_1 in the circuit.



$$\begin{aligned} i_1 &= -\frac{2}{8} \text{ A} \\ i_2 &= \frac{3}{8} \text{ A} \end{aligned}$$

$$\begin{cases} 3\text{V} + 4(i_1 - i_2) + 2i_1 = 0 \\ -5\text{V} - 4i_1 + 4(i_2 - i_1) + 4i_2 = 0 \end{cases}$$

Supermesh

上海 纽约 大学
NYU SHANGHAI

Problem with mesh analysis


If some mesh has some current source (dependent or independent), the voltage across the source cannot be expressed simply as a function of virtual currents.

Solution


Get rid of the voltage variable for the source by applying KVL to a **supermesh**

An extra equation is then required (source current expressed as a function of virtual currents)

Supermesh

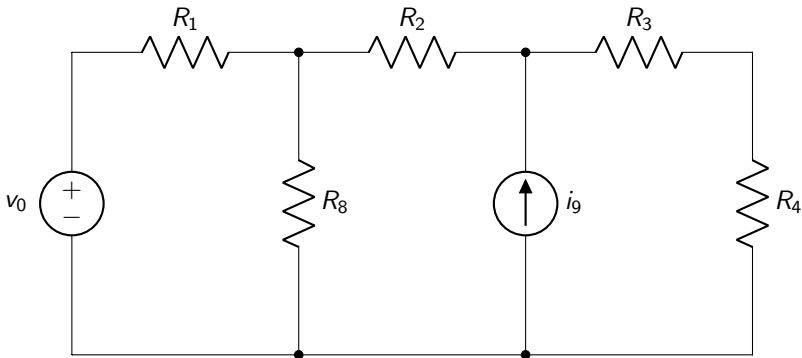上海纽约大学
NYU SHANGHAI

Supermesh

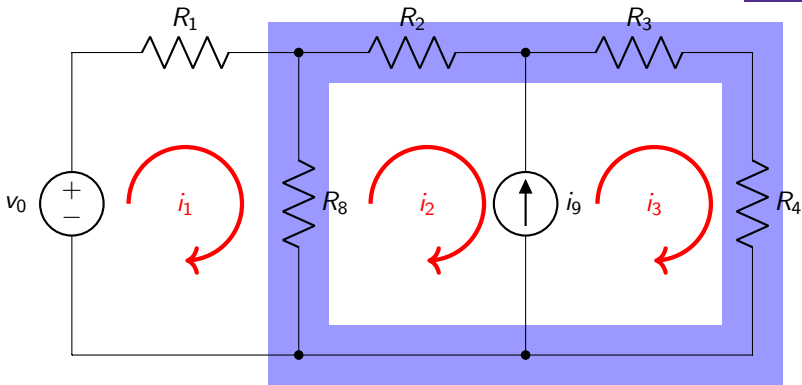
上海 纽约 大学
NYU SHANGHAI

- KVL on supermesh: $R_8 \cdot (i_1 - i_2) - R_2 \cdot i_2 - (R_3 + R_4) \cdot i_3 = 0$
- Extra equation: $i_9 = -i_2 + i_3$

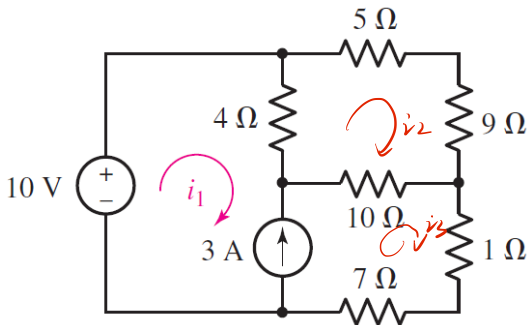Examples



Determine the current i_1 in the circuit.



$$-10 + 4\Omega \cdot i_1 + 10\Omega (i_3 - i_2) + 7\Omega \cdot i_3 = 0$$

$$14\Omega \cdot i_2 + 10\Omega (i_2 - i_3) + 4\Omega \cdot (i_2 - i_1) = 0$$

$$i_3 - i_1 = 3A$$