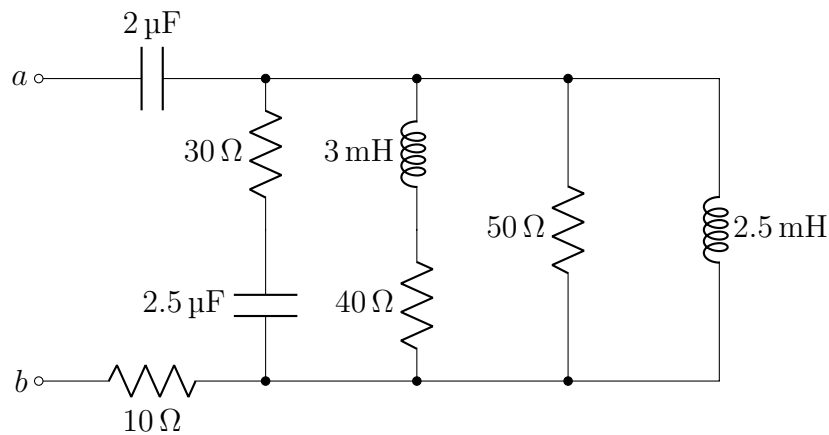


## Exercises 10

### -


## Phasors

### Exercise 1 - Equivalent impedance/admittance 1



- Determine the equivalent impedance/admittance for an angular frequency  $\omega = 10\,000$  rad/s.
- If we want the current and voltage for that equivalent impedance to be in phase for that frequency, by which value of capacitance should we change the  $2\,\mu\text{F}$  capacitor?
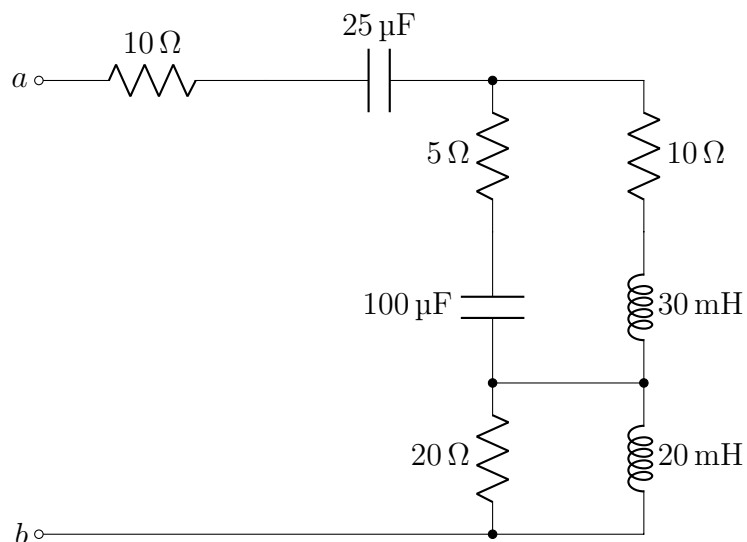
### Exercise 2 - Equivalent impedance/admittance 2




- Determine the equivalent impedance/admittance for an angular frequency  $\omega = 1000$  rad/s.

---

**Exercise 3 - Equivalent impedance/admittance 2**


---

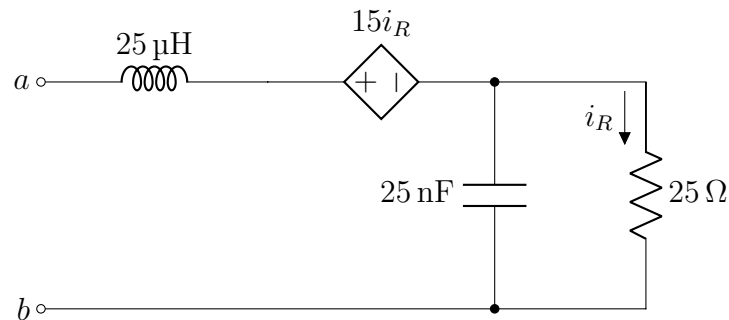


- Determine the equivalent impedance/admittance for an angular frequency  $\omega = 1.6 \text{ Mrad/s}$ .

---

**Exercise 4 - Circuit 1**


---

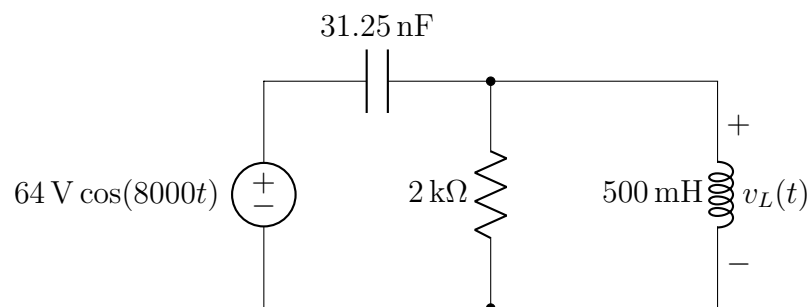


- Determine the steady-state expression for  $v_L(t)$ .

---


**Exercise 5 - Circuit 2**


---

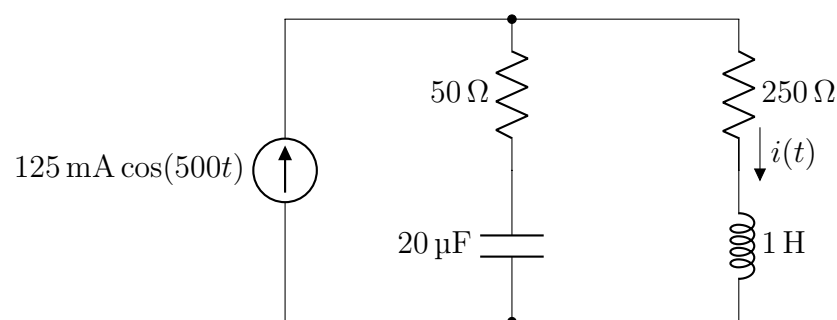


- Determine the steady-state expression for  $i(t)$ .

### Exercise 6 - Source transformation

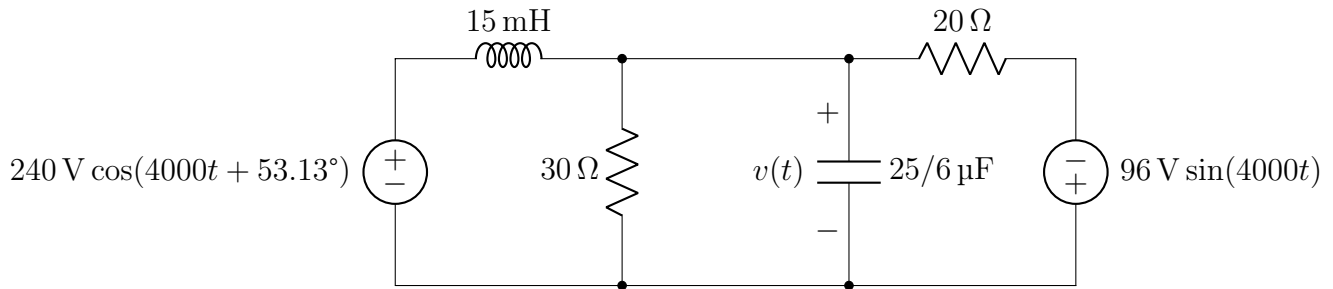


- Using source transformation, determine the steady-state expression for  $v(t)$ .

### Exercise 7 - Superposition

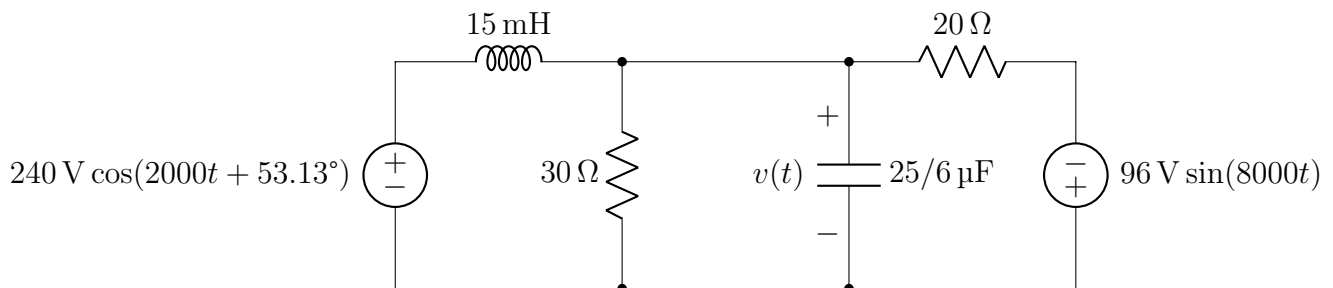

- Using superposition, determine the steady-state expression for  $v(t)$ .

### Exercise 8 - Circuit 3

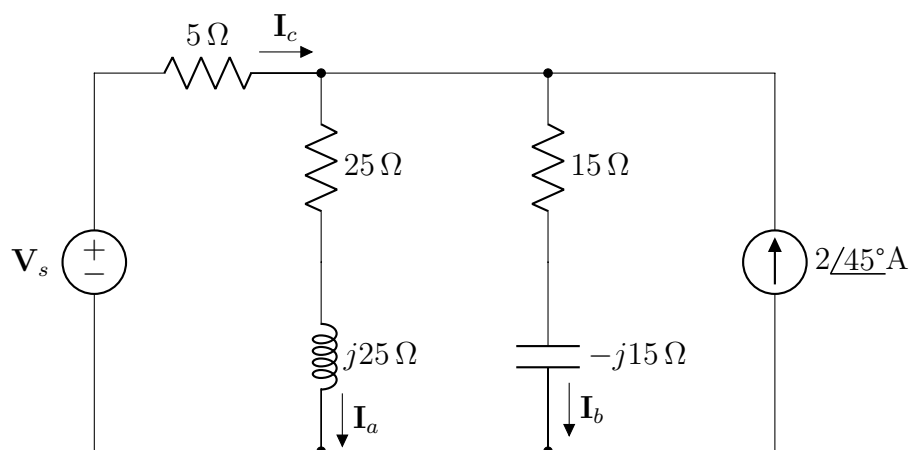


Knowing that  $\mathbf{I}_b = 5/45^\circ \text{A}$ :

- Determine  $\mathbf{I}_a$ ,  $\mathbf{I}_c$  and  $\mathbf{V}_s$
- For  $\omega = 800 \text{ rad/s}$ , give the expression for  $i_a(t)$ ,  $i_c(t)$  and  $v_s(t)$ .

---

**Exercise 9 - Circuit 4**

---

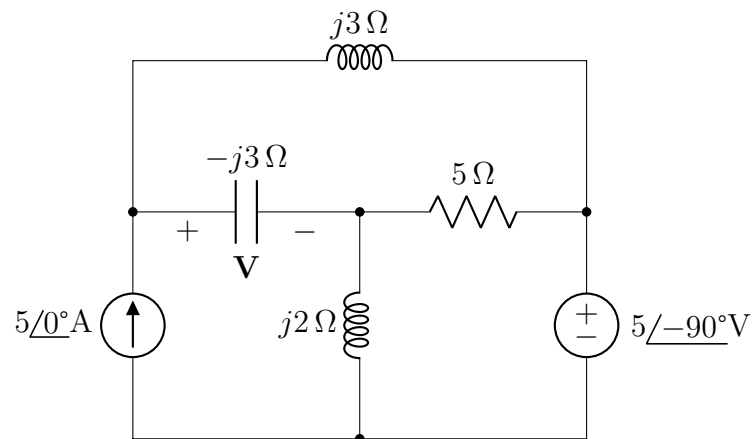

- Determine the phasor  $\mathbf{V}$ .