

# Circuits

-

## Voltage and current laws



Spring 2022

# Context

上海纽约大学  
NYU SHANGHAI

## Analyzing a circuit

- we need to determine the **voltages** and **currents** in the circuit
- for resistors: once we know the voltage, we know the current (or conversely)
- for sources: more complicated...

*Any kind of circuit can be analyzed*

## Additional rules

- Kirchhoff's current law (KCL)
- Kirchhoff's voltage law (KVL)

*charge conservation*  
*energy conservation*

# Context



## Wire

The wires connecting the different elements of a circuit will be considered to be **zero-resistance conductors**

*ideal.*

It means that there is **no voltage drop** on a wire (whatever the current value)

## Node

Definition: **a point** at which 2 or more elements are connected to

*they share the same voltage.*

## Path/Branch/Loop

- Path: starting at a node, going through different connected elements and stopping at another node *can be multiple elements*
- Branch: single path, composed of one element *only one path & one element*
- Loop: path that stops at the starting node (closed path)

## Context

上海纽约大学  
NYU SHANGHAI


The # elements should equal the # of branches

How many nodes and branches?

5 elements



5 branches

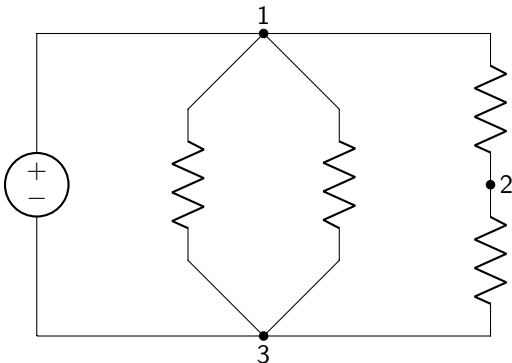

6 loops

3 nodes

from 1 to 3. 4 paths

# Kirchhoff's current law

上海纽约大学  
NYU SHANGHAI

*a restatement of charge conservation.*

## KCL


The algebraic sum of the currents **entering a node** (or a closed boundary) is **zero**

## Interpretation

Conservation of charge:

- all the electrons have to go somewhere
- the current that goes in, has to come out

# Kirchhoff's current law

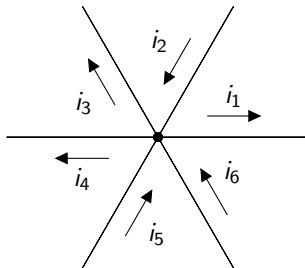上海纽约大学  
NYU SHANGHAI

## KCL formula

$$-i_1 + i_2 - i_3 - i_4 + i_5 + i_6 = 0$$


or

$$i_2 + i_5 + i_6 = i_1 + i_3 + i_4$$

上海纽约大学  
NYU SHANGHAI
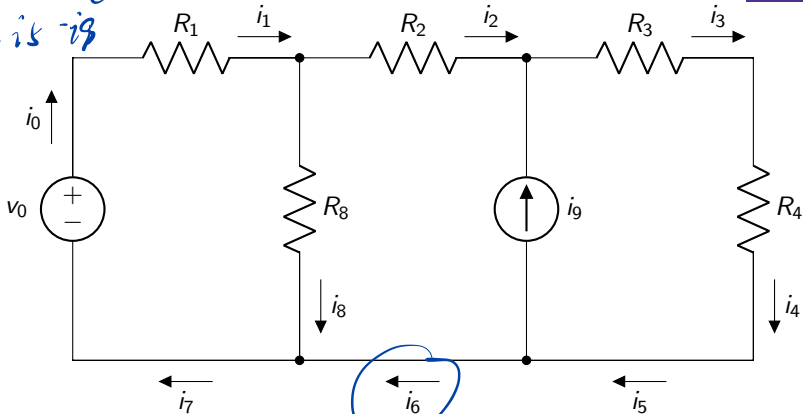
# Kirchhoff's current law

$\begin{cases} i_b = i_7 - i_8 \\ i_b = i_5 - i_9 \end{cases}$   $i_b$  is not necessary



How many nodes? How many branches?

Apply KCL to each node

$$i_b + i_9 = i_5$$

$$i_b + i_8 = i_7$$

5 nodes.  
7 branches

# Kirchhoff's current law

上海纽约大学  
NYU SHANGHAI

- $i_0 = i_1$
- $i_1 = i_2 + i_8$
- $i_2 + i_9 = i_3$
- $i_3 = i_4$
- $i_4 = i_5$
- $i_5 = i_6 + i_9$
- $i_6 + i_8 = i_7$
- $i_7 = i_0$

Are there some redundant variables?


How about  $i_6$ ?



# Kirchhoff's current law

上海纽约大学  
NYU SHANGHAI

Better annotation

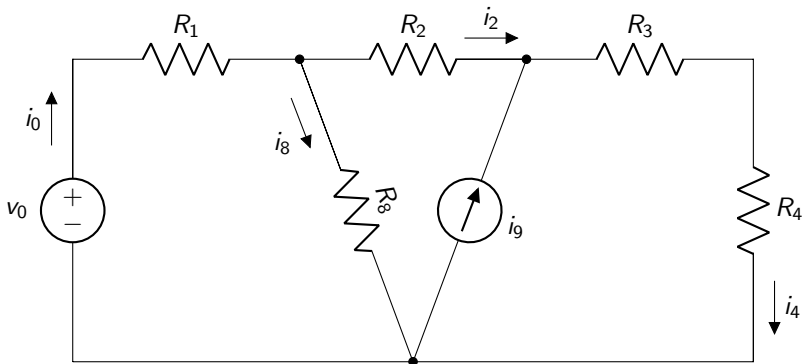


# Kirchhoff's current law

上海纽约大学  
NYU SHANGHAI

- $i_0 = i_2 + i_8$
- $i_2 + i_9 = i_4$
- $i_4 + i_8 = i_0 + i_9$

Actually, only 2 equations are necessary. The third one can be obtained from the other two.

# Kirchhoff's current law

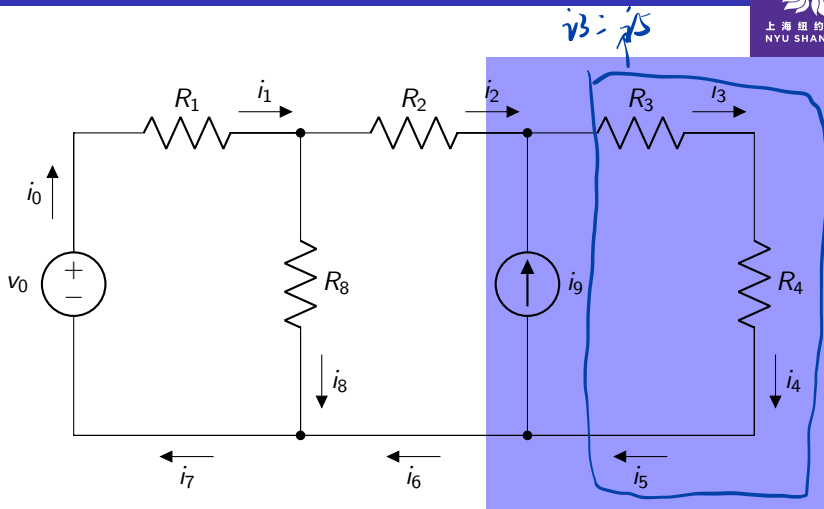上海纽约大学  
NYU SHANGHAI

KCL on closed boundaries:  $i_2 = i_6$

# Kirchhoff's voltage law

上海纽约大学  
NYU SHANGHAI

$$\oint \vec{E} \cdot d\vec{l} = 0$$

## KVL

The algebraic sum of **voltages** around a **loop** are **zero**

## Interpretation


### Conservation of energy:

- voltages are differences of electric potentials
- around a loop, the difference in electrical potential is zero



# Kirchhoff's voltage law

Better follow  
the PSC

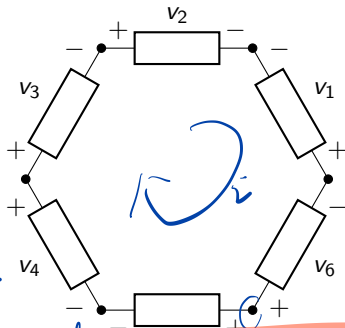

PSC  
allowed:  
 $-v_1 - v_4 - v_6$   
 $+v_5 + v_3 + v_2 = 0$

we can only  
assume one direction of the current.


KVL formula

$$-v_1 + v_2 + v_3 - v_4 + v_5 - v_6 = 0$$

or

$$v_1 + v_4 + v_6 = v_2 + v_3 + v_5$$


# Kirchhoff's voltage law

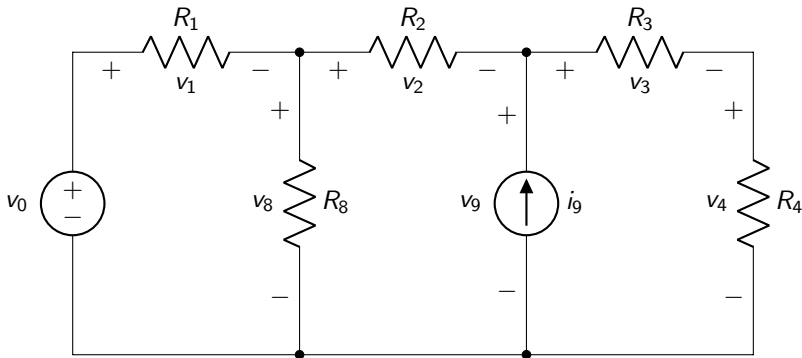上海纽约大学  
NYU SHANGHAI

6 Loops


How many loops?  
Apply KVL to each loop

# Kirchhoff's voltage law

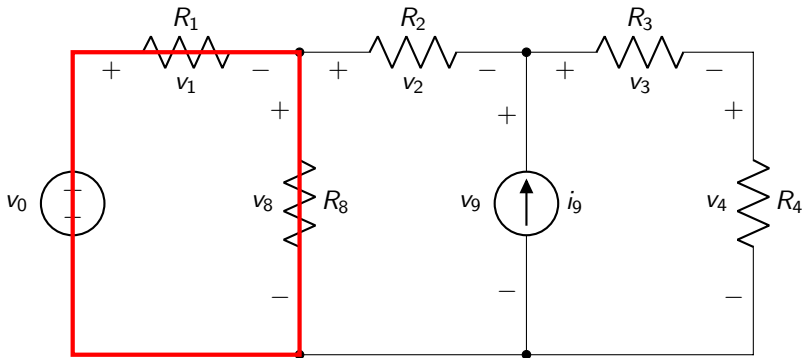上海纽约大学  
NYU SHANGHAI

How many loops?  
Apply KVL to each loop


# Kirchhoff's voltage law

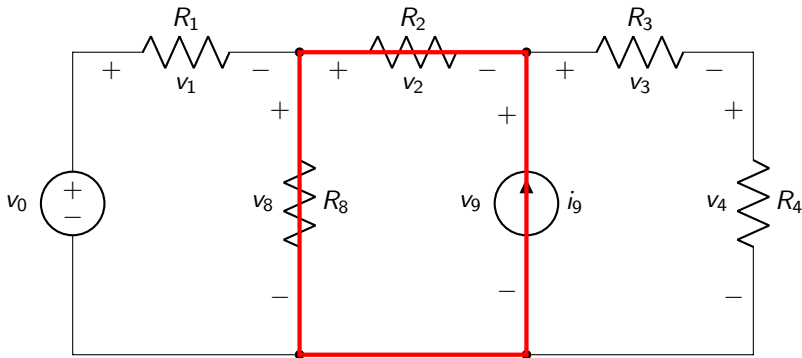上海纽约大学  
NYU SHANGHAI

How many loops?  
Apply KVL to each loop




# Kirchhoff's voltage law

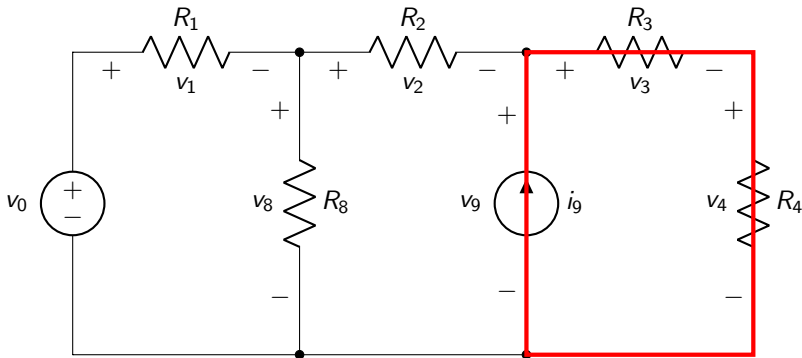上海纽约大学  
NYU SHANGHAI


How many loops?  
Apply KVL to each loop

# Kirchhoff's voltage law

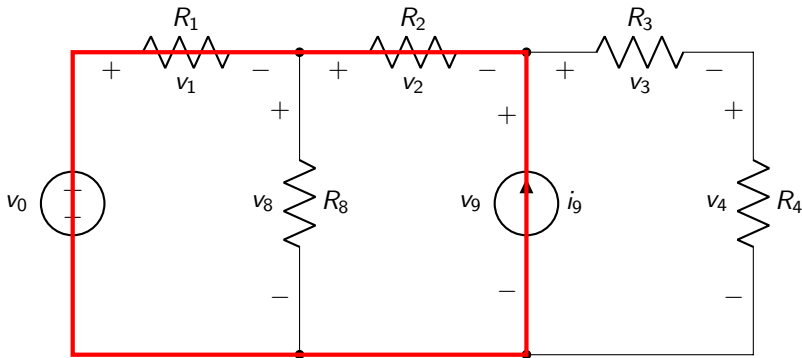上海纽约大学  
NYU SHANGHAI


How many loops?  
Apply KVL to each loop

# Kirchhoff's voltage law

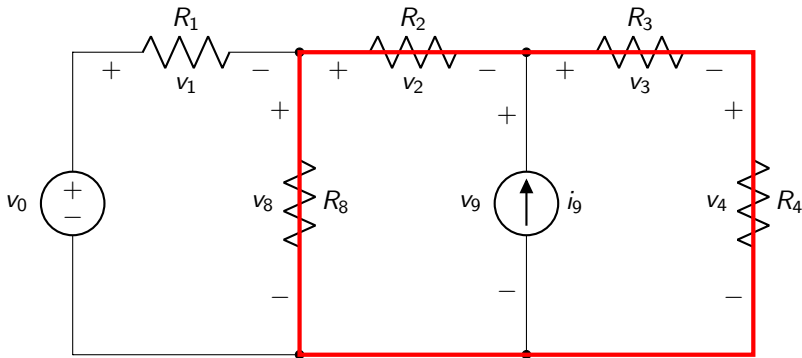上海纽约大学  
NYU SHANGHAI

How many loops?  
Apply KVL to each loop

# Kirchhoff's voltage law

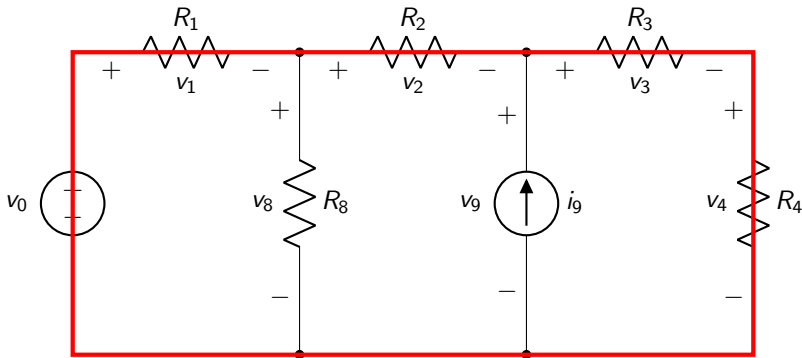上海纽约大学  
NYU SHANGHAI

How many loops?  
Apply KVL to each loop

# Kirchhoff's voltage law

上海 纽约 大学  
NYU SHANGHAI

- $v_0 = v_1 + v_8$
- $v_8 = v_2 + v_9$
- $v_9 = v_3 + v_4$
- $v_0 = v_1 + v_2 + v_9$
- $v_8 = v_2 + v_3 + v_4$
- $v_0 = v_1 + v_2 + v_3 + v_4$

Actually, only 3 equations are necessary. The three others can be deduced from the other ones.




上海纽约大学  
NYU SHANGHAI
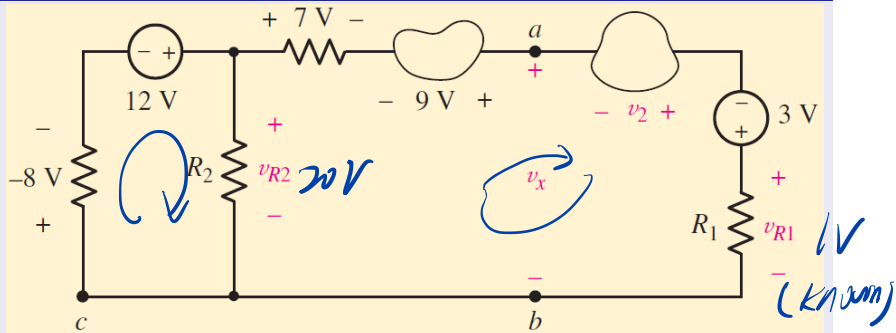
## Examples I

$-24V$

When  $v_{R1} = 1V$ , determine  $v_{R2}$  and  $v_2$ .




$$-1 + V_{R_2} - 7V + 9V + V_2 + 3kV$$

## Examples II

✱ combine ohm's Law. KVL & KCL.

Determine  $v_x$  in the circuit.

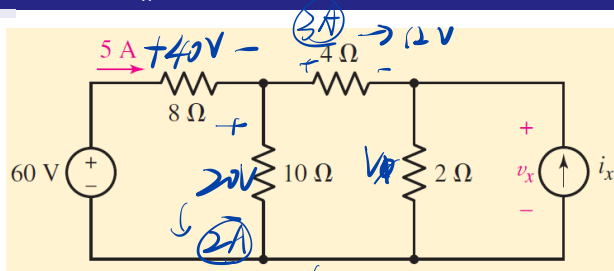

we're actually calculating voltage  
across the  $2\Omega$  resistor

$$\therefore \text{finally } v_x = 8V$$

# How to analyze circuits by KCL and KVL?

上海纽约大学  
NYU SHANGHAI

- ① Identify the goal of the problem.  
Label  $i$  or  $v$  on the circuit diagram.
- ② Collect the known information.  
The nodes, branches, ...
- ③ Devise a plan  
KCL and KVL and Ohm's law
- ④ Construct an appropriate set of equations.  
Summing the currents flowing into the node.
- ⑤ Determine if additional information is required.
- ⑥ Attempt a solution
- ⑦ Verify the solution. Is it reasonable or expected?  
It is always worth the effort to recheck our work.