

Circuits

-

First-order circuits

NYU
上海



SHANGHAI
纽约大学

Spring 2022

First order circuits

上海纽约大学
NYU SHANGHAI

Definition

Circuits that contain a single capacitor or inductor (and resistors, sources and switches).

It can contain multiple capacitors or inductors as long as we can combine them into a single equivalent capacitor/inductor.

Analysis

We will use KCL and KVL for the analysis of such circuits.


2 kinds of response

- **Natural response:** when the circuit does not contain any source (also called source-free)
- **Forced response:** when the circuit contains a source

Switches


上海纽约大学
NYU SHANGHAI

Opening switch

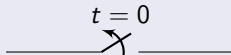

- $t < 0$: equivalent to a short-circuit
- $t > 0$: equivalent to an open-circuit

Closing switch

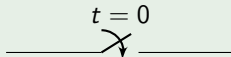


- $t < 0$: equivalent to an open-circuit
- $t > 0$: equivalent to a short-circuit

RC circuits (Natural response)

上海纽约大学
NYU SHANGHAI

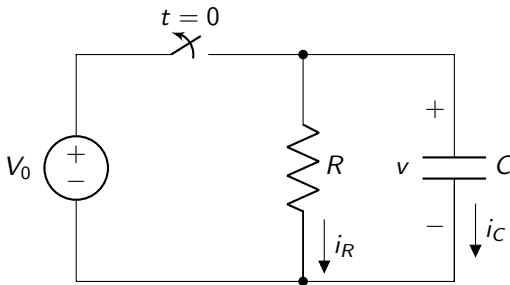
The switch, initially closed, opens at $t = 0$



RC circuits (Natural response)

上海纽约大学
NYU SHANGHAI

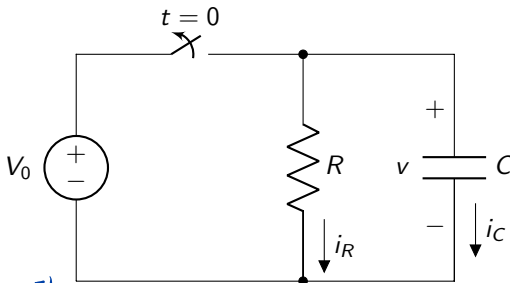The switch, initially closed, opens at $t = 0$



$$W(t=0^-) = \frac{1}{2} C V_0^2$$

$t < 0$

For $t < 0$, we suppose that the switch has been closed for a *long* time


- Capacitor voltage $v(t=0^-)$? V_0
- Capacitor current $i_C(t=0^-)$? 0
- Stored energy in the capacitor $w(t=0^-)$?

the response is
very stable now
the energy is already
stored

RC circuits (Natural response)

上海纽约大学
NYU SHANGHAI

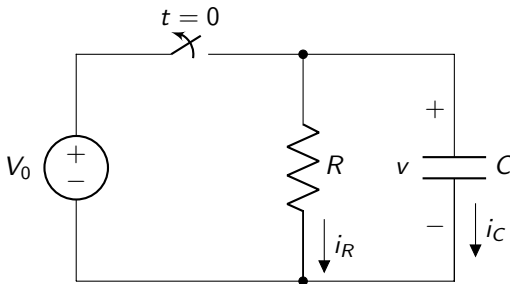The switch, initially closed, opens at $t = 0$



$t < 0$


For $t < 0$, we suppose that the switch has been closed for a *long* time

- Capacitor voltage $v(t = 0^-)$? $v(t = 0^-) = V_0$
- Capacitor current $i_C(t = 0^-)$?
- Stored energy in the capacitor $w(t = 0^-)$?

RC circuits (Natural response)

上海纽约大学
NYU SHANGHAI

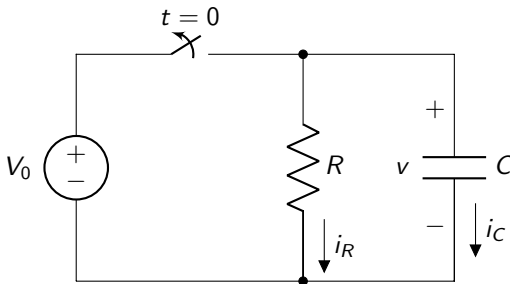The switch, initially closed, opens at $t = 0$



$t < 0$


For $t < 0$, we suppose that the switch has been closed for a *long* time

- Capacitor voltage $v(t = 0^-)$? $v(t = 0^-) = V_0$
- Capacitor current $i_C(t = 0^-)$? $i_C(t = 0^-) = 0$
- Stored energy in the capacitor $w(t = 0^-)$?

RC circuits (Natural response)

上海纽约大学
NYU SHANGHAI

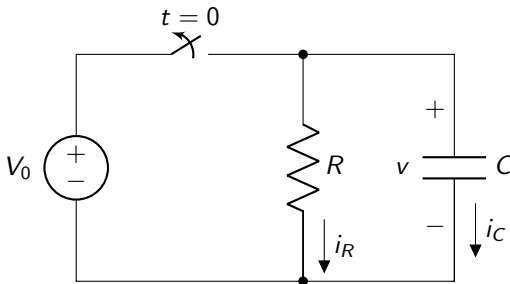The switch, initially closed, opens at $t = 0$



$t < 0$


For $t < 0$, we suppose that the switch has been closed for a *long* time

- Capacitor voltage $v(t = 0^-)$? $v(t = 0^-) = V_0$
- Capacitor current $i_C(t = 0^-)$? $i_C(t = 0^-) = 0$
- Stored energy in the capacitor $w(t = 0^-)$? $w(t = 0^-) = \frac{1}{2} C \cdot V_0^2$

RC circuits (Natural response)

上海纽约大学
NYU SHANGHAI

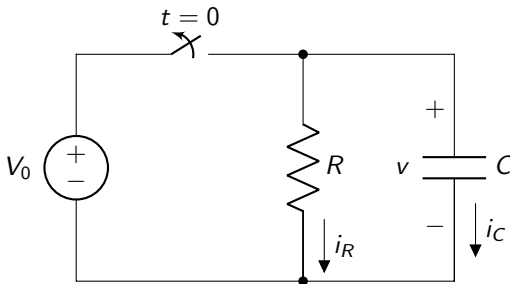The switch, initially closed, opens at $t = 0$



$t > 0$


The switch has just been opened ($t = 0^+$)

- Capacitor voltage $v(t = 0^+)$ V_0
- Capacitor current $i_C(t = 0^+)$
- Stored energy in the capacitor $w(t = 0^+)$

RC circuits (Natural response)



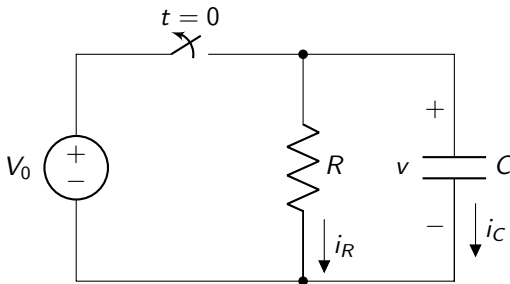The switch, initially closed, opens at $t = 0$



$t > 0$


The switch has just been opened ($t = 0^+$)

- Capacitor voltage $v(t = 0^+)$? $v(t = 0^+) = V_0$
- Capacitor current $i_C(t = 0^+)$?
- Stored energy in the capacitor $w(t = 0^+)$?

RC circuits (Natural response)

上海纽约大学
NYU SHANGHAI

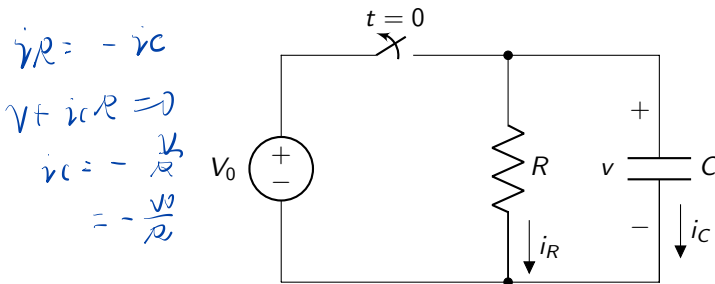The switch, initially closed, opens at $t = 0$



$t > 0$


The switch has just been opened ($t = 0^+$)

- Capacitor voltage $v(t = 0^+)$? $v(t = 0^+) = V_0$
- Capacitor current $i_C(t = 0^+)$? $i_C(t = 0^+) = -\frac{V_0}{R}$
- Stored energy in the capacitor $w(t = 0^+)$?

RC circuits (Natural response)

上海纽约大学
NYU SHANGHAI

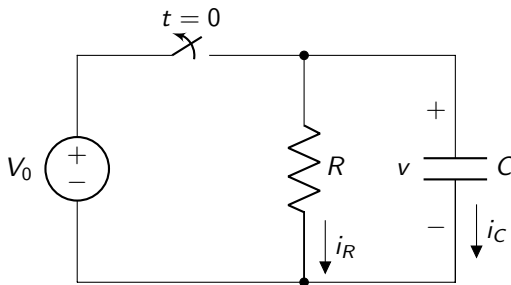The switch, initially closed, opens at $t = 0$



$t > 0$


The switch has just been opened ($t = 0^+$)

- Capacitor voltage $v(t = 0^+)$? $v(t = 0^+) = V_0$
- Capacitor current $i_C(t = 0^+)$? $i_C(t = 0^+) = -\frac{V_0}{R}$
- Stored energy in the capacitor $w(t = 0^+)$? $w(t = 0^+) = \frac{1}{2} C \cdot V_0^2$

RC circuits (Natural response)

上海纽约大学
NYU SHANGHAI

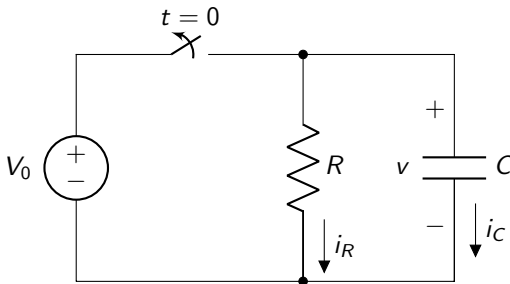The switch, initially closed, opens at $t = 0$



$t \rightarrow \infty$


The switch has been opened for a *long* time

- Capacitor voltage $v(t \rightarrow \infty)$?
- Capacitor current $i_C(t \rightarrow \infty)$?
- Stored energy in the capacitor $w(t \rightarrow \infty)$?

RC circuits (Natural response)

上海纽约大学
NYU SHANGHAI

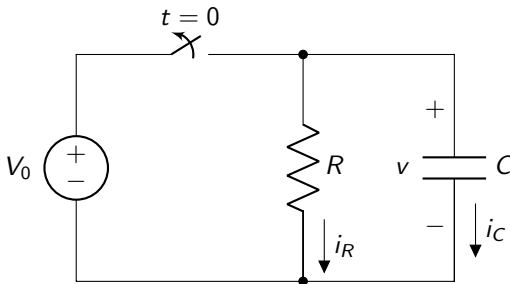The switch, initially closed, opens at $t = 0$



$t \rightarrow \infty$


The switch has been opened for a *long* time

- Capacitor voltage $v(t \rightarrow \infty)$? $v(t \rightarrow \infty) = 0$
- Capacitor current $i_C(t \rightarrow \infty)$?
- Stored energy in the capacitor $w(t \rightarrow \infty)$?

RC circuits (Natural response)

上海纽约大学
NYU SHANGHAI

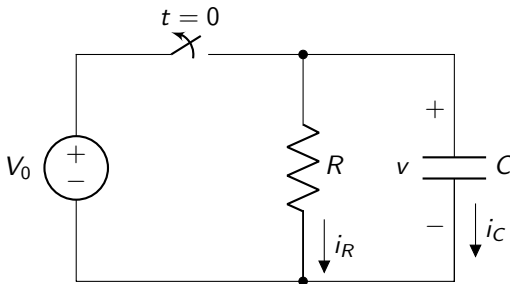The switch, initially closed, opens at $t = 0$



$t \rightarrow \infty$


The switch has been opened for a *long* time

- Capacitor voltage $v(t \rightarrow \infty)$? $v(t \rightarrow \infty) = 0$
- Capacitor current $i_C(t \rightarrow \infty)$? $i_C(t \rightarrow \infty) = 0$
- Stored energy in the capacitor $w(t \rightarrow \infty)$?

RC circuits (Natural response)

上海纽约大学
NYU SHANGHAI

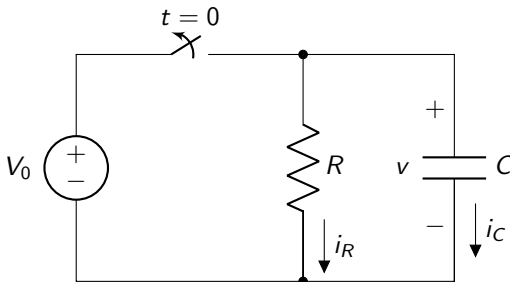The switch, initially closed, opens at $t = 0$



All the electrons have met their protons

$t \rightarrow \infty$

The switch has been opened for a *long* time

- Capacitor voltage $v(t \rightarrow \infty)$? $v(t \rightarrow \infty) = 0$
- Capacitor current $i_C(t \rightarrow \infty)$? $i_C(t \rightarrow \infty) = 0$
- Stored energy in the capacitor $w(t \rightarrow \infty)$? $w(t \rightarrow \infty) = 0$

RC circuits (Natural response)

上海纽约大学
NYU SHANGHAI

Determination of $v(t)$

For $t \geq 0$, we can write:

- $i_C(t) + i_R(t) = 0$
- $C \frac{dv(t)}{dt} + \frac{v(t)}{R} = 0$
- $\frac{dv(t)}{dt} + \frac{v(t)}{\tau} = 0$

Time constant τ

The unit of the product RC is proportional to **time** (usually in s, or ms, or μs ...).

This product RC is called the **time constant** τ with $\tau = RC$.

RC circuits (Natural response)



Determination of $v(t)$

For $t \geq 0$, we have:

$$\frac{dv(t)}{dt} + \frac{v(t)}{\tau} = 0$$

Solution (for $t \geq 0$)


- $\frac{dv(t)}{dt} = -\frac{v(t)}{\tau}$
- $\frac{1}{v(t)} \cdot \frac{dv(t)}{dt} = -\frac{1}{\tau}$
- $\int_0^t \frac{1}{v(t')} \cdot \frac{dv(t')}{dt'} dt' = -\frac{1}{\tau} \int_0^t dt'$
- $\int_{v(0)=V_0}^{v(t)} \frac{1}{v'} \cdot dv' = -\frac{t}{\tau} \implies \ln\left(\frac{v(t)}{V_0}\right) = -\frac{t}{\tau}$

RC circuits (Natural response)




RC circuit natural response
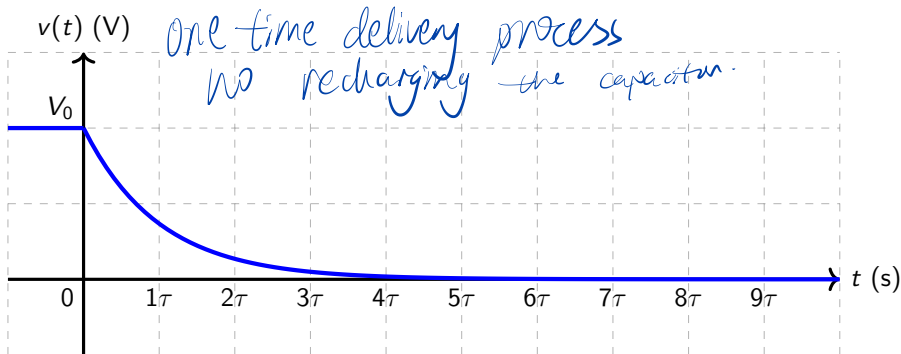
$$v(t) = \begin{cases} V_s, & \text{if } t \leq 0 \\ V_0 e^{-\frac{t}{\tau}}, & \text{if } t \geq 0 \end{cases}$$




RC circuits (Natural response)

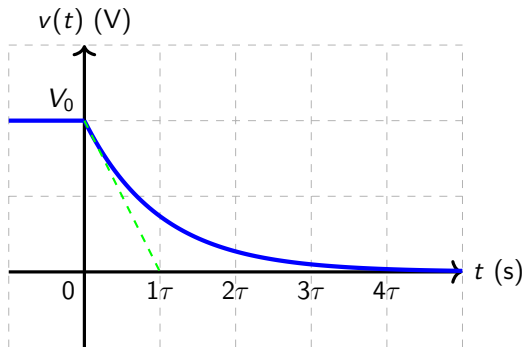


Exponential values

t	$v(t)$
τ	$0.37V_s$
2τ	$0.14V_s$
3τ	$0.05V_s$
5τ	$0.01V_s$


RC circuits (Natural response)

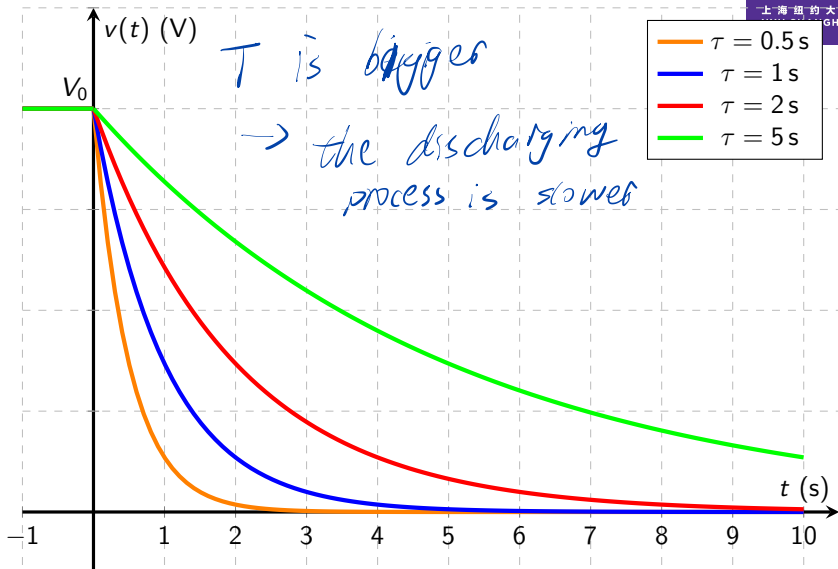上海纽约大学
SHANGHAI


RC circuits (Natural response)

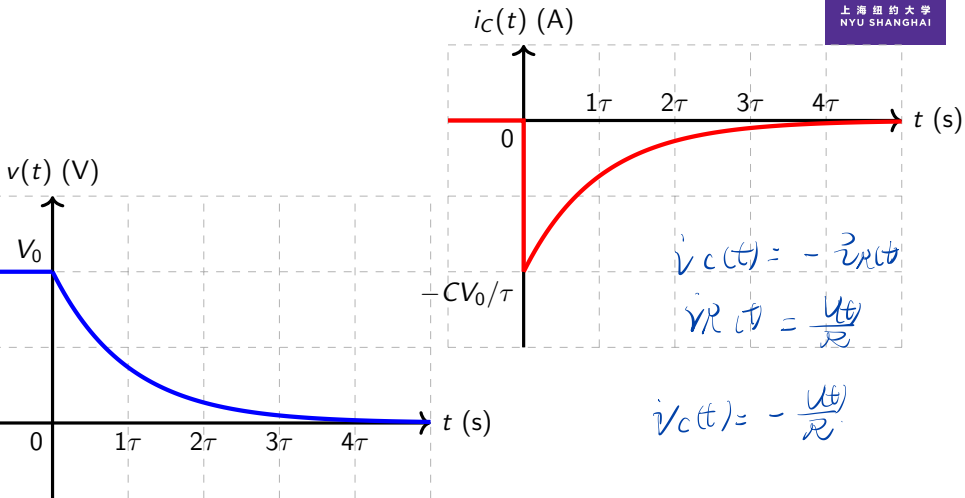上海纽约大学
NYU SHANGHAI

RC circuits (Forced response)

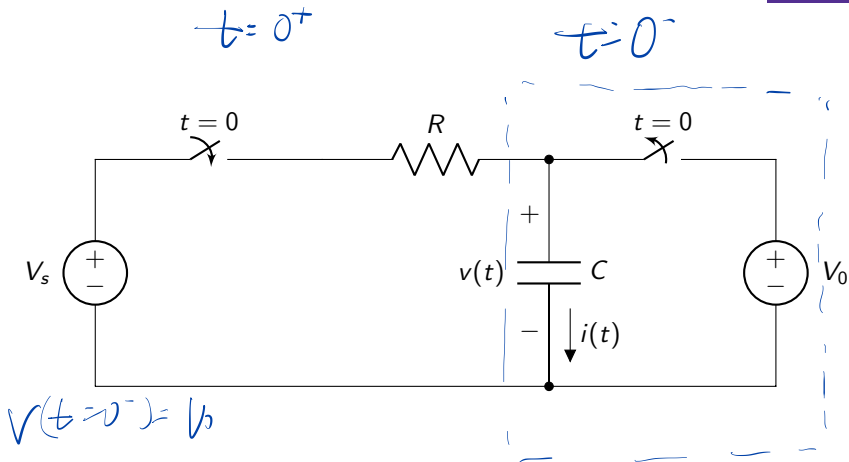上海纽约大学
NYU SHANGHAI


RC circuits (Forced response)

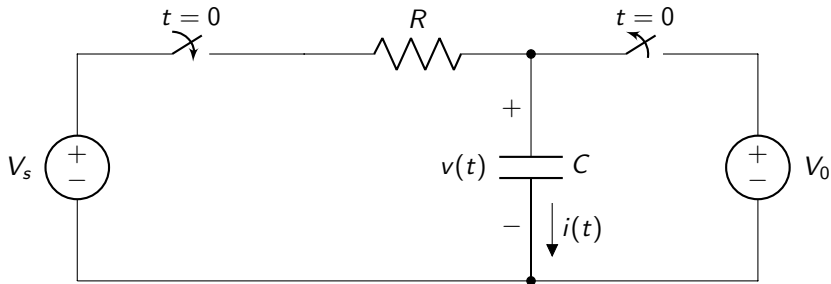上海纽约大学
NYU SHANGHAI $t < 0$

For $t < 0$, we suppose that the circuit was in that state for a *long* time

- Capacitor voltage $v(t = 0^-)$?
- Capacitor current $i(t = 0^-)$?
- Stored energy in the capacitor $w(t = 0^-)$?


RC circuits (Forced response)

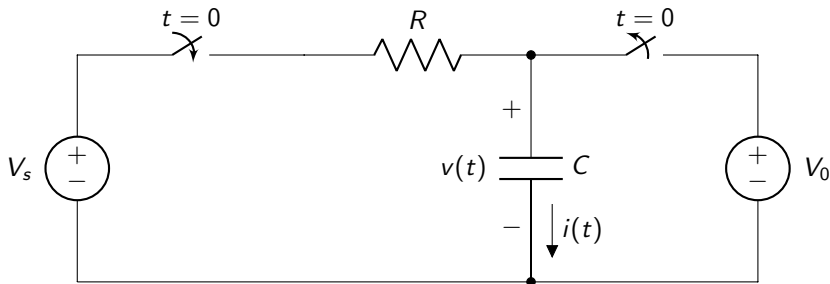上海纽约大学
NYU SHANGHAI $t < 0$

For $t < 0$, we suppose that the circuit was in that state for a *long* time

- Capacitor voltage $v(t = 0^-)$? $v(t = 0^-) = V_0$
- Capacitor current $i(t = 0^-)$?
- Stored energy in the capacitor $w(t = 0^-)$?


RC circuits (Forced response)

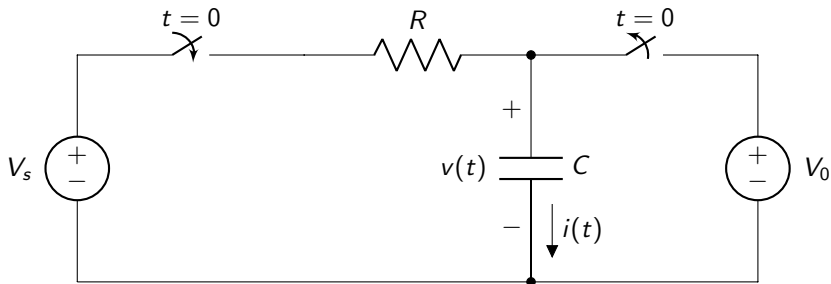上海纽约大学
NYU SHANGHAI $t < 0$

For $t < 0$, we suppose that the circuit was in that state for a *long* time

- Capacitor voltage $v(t = 0^-)$? $v(t = 0^-) = V_0$
- Capacitor current $i(t = 0^-)$? $i(t = 0^-) = 0$
- Stored energy in the capacitor $w(t = 0^-)$?


RC circuits (Forced response)

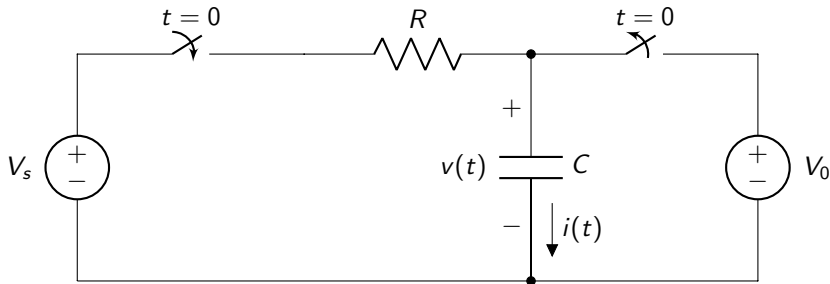上海纽约大学
NYU SHANGHAI $t < 0$

For $t < 0$, we suppose that the circuit was in that state for a *long* time

- Capacitor voltage $v(t = 0^-)$? $v(t = 0^-) = V_0$
- Capacitor current $i(t = 0^-)$? $i(t = 0^-) = 0$
- Stored energy in the capacitor $w(t = 0^-)$? $w(t = 0^-) = \frac{1}{2} C \cdot V_0^2$

RC circuits (Forced response)

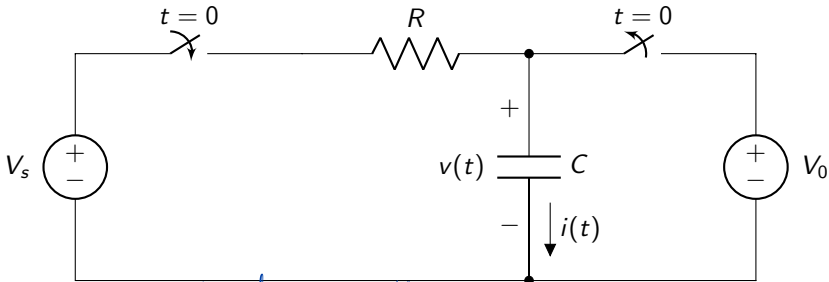
上海纽约大学
NYU SHANGHAI

should be continuous all the time.

$t > 0$

- Capacitor voltage $v(t = 0^+)$?
- Capacitor current $i(t = 0^+)$?
- Stored energy in the capacitor $w(t = 0^+)$?

RC circuits (Forced response)

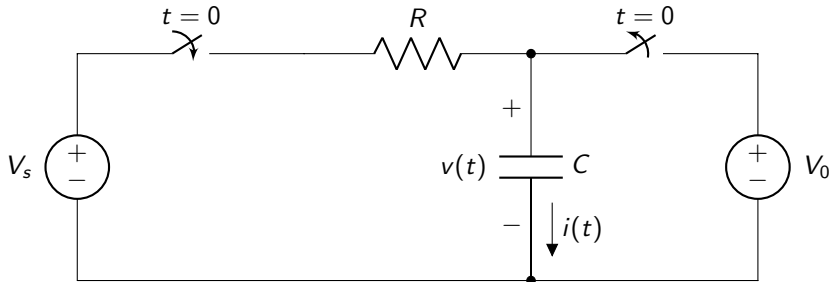上海 纽约 大学
NYU SHANGHAI $t > 0$


- Capacitor voltage $v(t = 0^+)$? $v(t = 0^+) = V_0$

- Capacitor current $i(t = 0^+)$? $-V_s + R i(t = 0^+) + V_0 = 0$

- Stored energy in the capacitor $w(t = 0^+)$?


$$v(t) = \frac{V_s - V_0}{R}$$

RC circuits (Forced response)

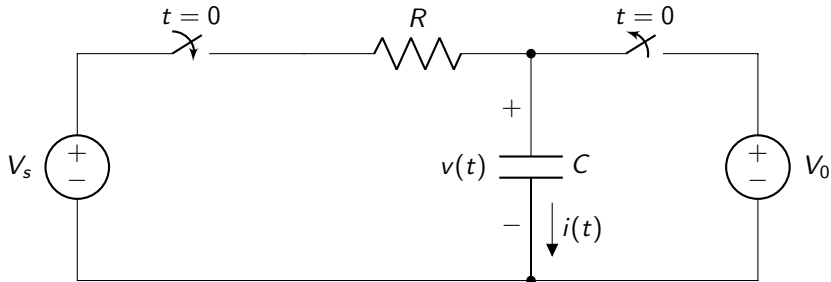上海 纽约 大学
NYU SHANGHAI $t > 0$


- Capacitor voltage $v(t = 0^+)$? $v(t = 0^+) = V_0$
- Capacitor current $i(t = 0^+)$? $i(t = 0^+) = \frac{V_s - V_0}{R}$
- Stored energy in the capacitor $w(t = 0^+)$?

RC circuits (Forced response)

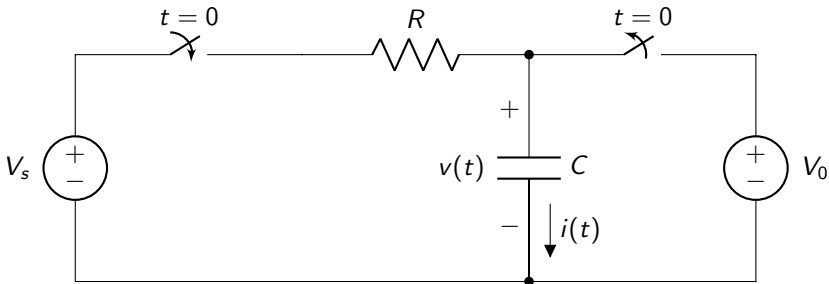上海纽约大学
NYU SHANGHAI $t > 0$

- Capacitor voltage $v(t = 0^+)$? $v(t = 0^+) = V_0$
- Capacitor current $i(t = 0^+)$? $i(t = 0^+) = \frac{V_s - V_0}{R}$
- Stored energy in the capacitor $w(t = 0^+)$? $w(t = 0^+) = \frac{1}{2} C \cdot V_0^2$


RC circuits (Forced response)

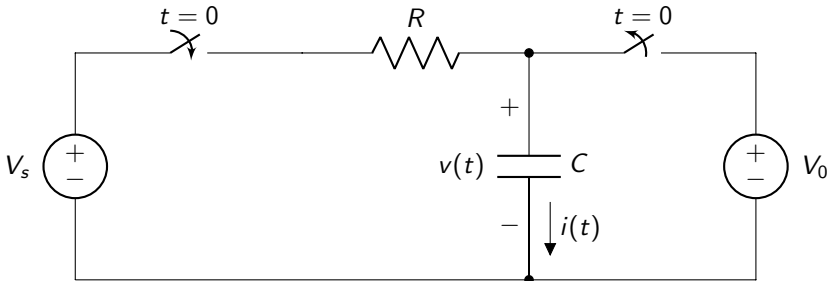上海纽约大学
NYU SHANGHAI

very stable: capacitor as open circuit now
 $t \rightarrow \infty$


- Capacitor voltage $v(t \rightarrow \infty)$? V_s
- Capacitor current $i(t \rightarrow \infty)$? 0
- Stored energy in the capacitor $w(t \rightarrow \infty)$?

RC circuits (Forced response)

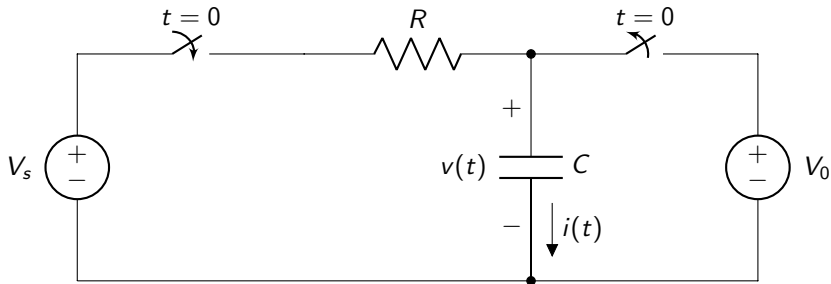上海纽约大学
NYU SHANGHAI $t \rightarrow \infty$


- Capacitor voltage $v(t \rightarrow \infty)$? $v(t \rightarrow \infty) = V_s$
- Capacitor current $i(t \rightarrow \infty)$?
- Stored energy in the capacitor $w(t \rightarrow \infty)$?

RC circuits (Forced response)

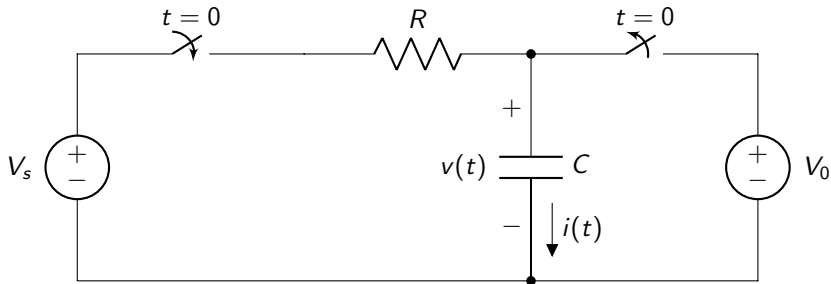上海纽约大学
NYU SHANGHAI $t \rightarrow \infty$

- Capacitor voltage $v(t \rightarrow \infty)$? $v(t \rightarrow \infty) = V_s$
- Capacitor current $i(t \rightarrow \infty)$? $i(t \rightarrow \infty) = 0$
- Stored energy in the capacitor $w(t \rightarrow \infty)$?

RC circuits (Forced response)

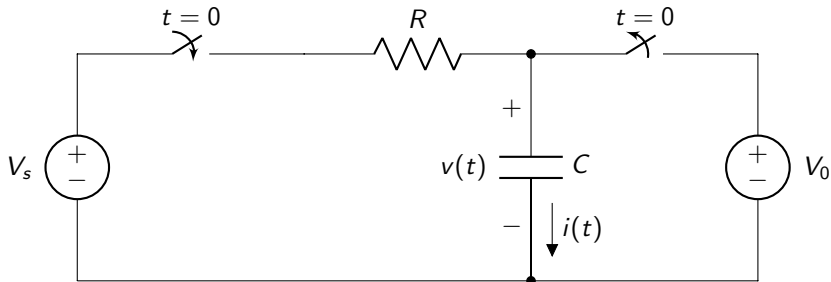上海纽约大学
NYU SHANGHAI $t \rightarrow \infty$

- Capacitor voltage $v(t \rightarrow \infty)$? $v(t \rightarrow \infty) = V_s$
- Capacitor current $i(t \rightarrow \infty)$? $i(t \rightarrow \infty) = 0$
- Stored energy in the capacitor $w(t \rightarrow \infty)$? $w(t \rightarrow \infty) = \frac{1}{2} C \cdot V_s^2$

RC circuits (Forced response)

上海纽约大学
NYU SHANGHAI

natural response
↓

Determination of $v(t)$

For $t \geq 0$, we can write:

$$\blacksquare i(t) = C \frac{dv(t)}{dt}$$

$$\blacksquare V_s = R \cdot i(t) + v(t) \quad \Rightarrow \quad \tau \frac{dv(t)}{dt} + v(t) = V_s$$

$$\frac{dv(t)}{dt} + \frac{v(t)}{\tau} \Rightarrow$$

Solution

Solution similar to natural response.

By setting $v_2(t) = v(t) - V_s$, we get: $\tau \frac{dv_2(t)}{dt} + v_2(t) = 0$



RC circuit forced response

$$v(t) = \begin{cases} V_0, & \text{if } t \leq 0 \\ (V_0 - V_s)e^{-\frac{t}{\tau}} + V_s, & \text{if } t \geq 0 \end{cases}$$




$V_s > V_0$. charging process


$V_s < V_0$ discharging process

RC circuits (Forced response)

上海交通大学
SJTU

RC circuit forced response

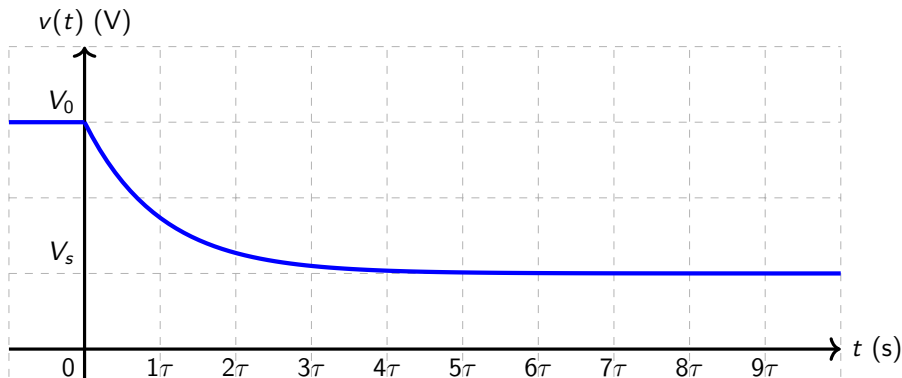
$$v(t) = \begin{cases} V_0, & \text{if } t \leq 0 \\ (V_0 - V_s)e^{-\frac{t}{\tau}} + V_s, & \text{if } t \geq 0 \end{cases}$$



RC circuits

上海纽约大学
NYU SHANGHAI

Natural Response

$$\begin{cases} v_0 & t \leq 0 \\ v_0 e^{-\frac{t}{\tau}} & t > 0 \end{cases}$$

Generic method

- 1 Zero-out all the independent sources, and determine R_{eq} , C_{eq} and the time constant $\tau = R_{eq}C_{eq}$
- 2 Determine the capacitor voltage $v(0^-)$ before the change ($t \leq 0$) by DC analysis, meaning considering the capacitor is **equivalent to an open-circuit**
- 3 Find the steady-state capacitor voltage $v(t \rightarrow \infty)$ by using DC analysis, still considering the capacitor is **equivalent to an open-circuit**
- 4 The response (for $t \geq 0$) is then:

$$v(t) = v(t \rightarrow \infty) + (v(0^-) - v(t \rightarrow \infty))e^{-t/\tau}$$


Forced Response.

$$v(t) = \begin{cases} v_0 & t \leq 0 \\ (v_0 - V_s)e^{-\frac{t}{\tau}} + V_s & t > 0 \end{cases}$$


RL circuits (Natural response)

上海纽约大学
NYU SHANGHAI

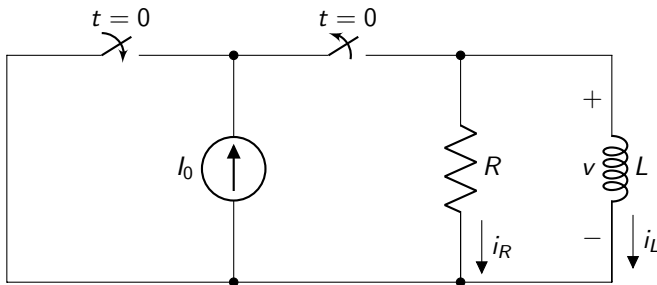Why choose voltage as the response?
Voltage is the consequence. current is the premise.



RL circuits (Natural response)

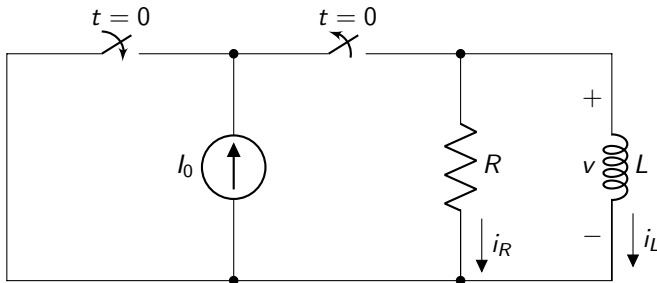
上海纽约大学
NYU SHANGHAI

$t < 0$

For $t < 0$, we suppose that the circuit was in that state for a *long* time

- Inductor current $i_L(t = 0^-)$?
- Inductor voltage $v(t = 0^-)$?
- Stored energy in the inductor $w(t = 0^-)$?


RL circuits (Natural response)

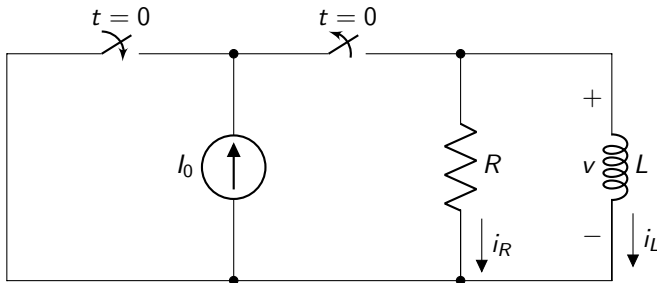上海纽约大学
NYU SHANGHAI $t < 0$

For $t < 0$, we suppose that the circuit was in that state for a *long* time

- Inductor current $i_L(t = 0^-)$? $i_L(t = 0^-) = I_0$
- Inductor voltage $v(t = 0^-)$?
- Stored energy in the inductor $w(t = 0^-)$?


RL circuits (Natural response)

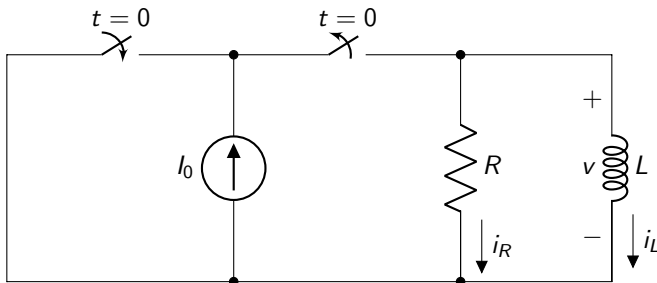上海纽约大学
NYU SHANGHAI $t < 0$

For $t < 0$, we suppose that the circuit was in that state for a *long* time

- Inductor current $i_L(t = 0^-)$? $i_L(t = 0^-) = I_0$
- Inductor voltage $v(t = 0^-)$? $v(t = 0^-) = 0$
- Stored energy in the inductor $w(t = 0^-)$?


RL circuits (Natural response)

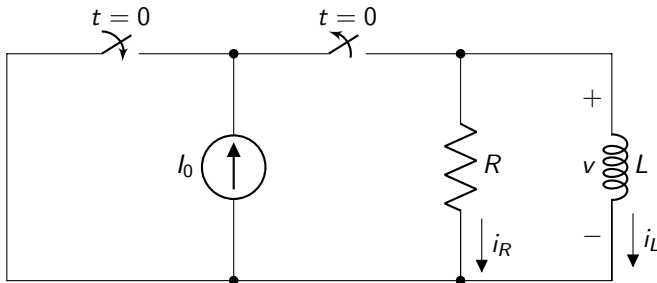上海纽约大学
NYU SHANGHAI $t < 0$

For $t < 0$, we suppose that the circuit was in that state for a *long* time


- Inductor current $i_L(t = 0^-)$? $i_L(t = 0^-) = I_0$
- Inductor voltage $v(t = 0^-)$? $v(t = 0^-) = 0$
- Stored energy in the inductor $w(t = 0^-)$? $w(t = 0^-) = \frac{1}{2} L \cdot I_0^2$

RL circuits (Natural response)

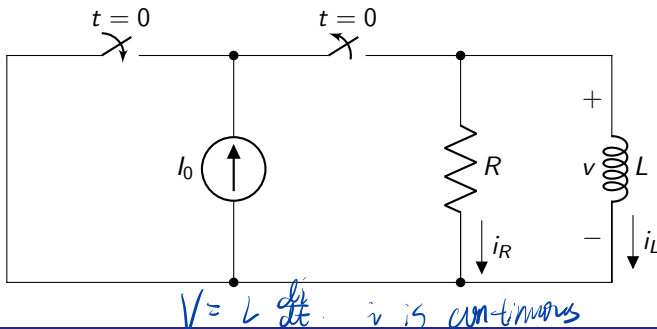上海纽约大学
NYU SHANGHAI $t > 0$


- Inductor current $i_L(t = 0^+)$?
- Inductor voltage $v(t = 0^+)$?
- Stored energy in the inductor $w(t = 0^-)$?

RL circuits (Natural response)

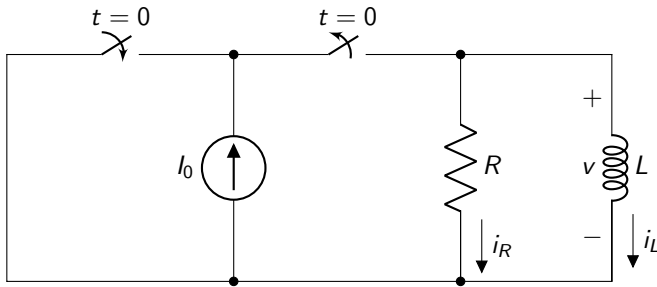上海 纽约 大学
NYU SHANGHAI $t > 0$


- Inductor current $i_L(t = 0^+)$? $i_L(t = 0^+) = I_0$
- Inductor voltage $v(t = 0^+)$?
- Stored energy in the inductor $w(t = 0^-)$?

RL circuits (Natural response)

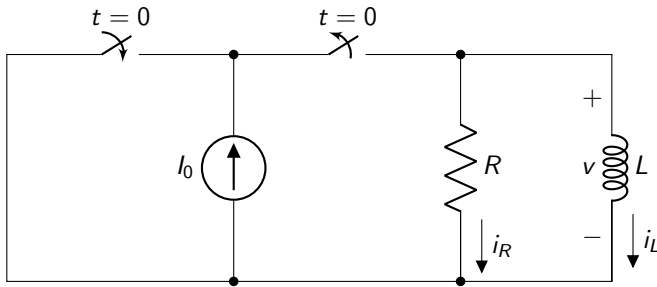上海纽约大学
NYU SHANGHAI $t > 0$


- Inductor current $i_L(t = 0^+)$? $i_L(t = 0^+) = I_0$
- Inductor voltage $v(t = 0^+)$? $v(t = 0^+) = -RI_0$
- Stored energy in the inductor $w(t = 0^-)$?

RL circuits (Natural response)

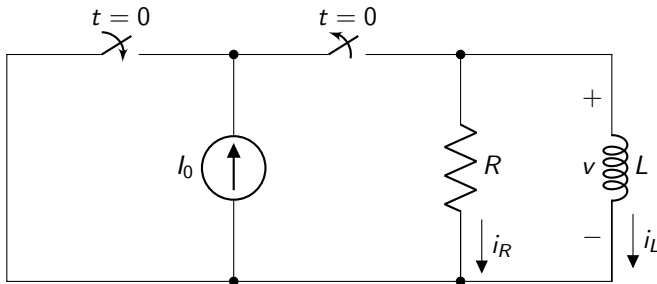上海纽约大学
NYU SHANGHAI $t > 0$


- Inductor current $i_L(t = 0^+)$? $i_L(t = 0^+) = I_0$
- Inductor voltage $v(t = 0^+)$? $v(t = 0^+) = -RI_0$
- Stored energy in the inductor $w(t = 0^+)$? $w(t = 0^+) = \frac{1}{2}L \cdot I_0^2$

RL circuits (Natural response)

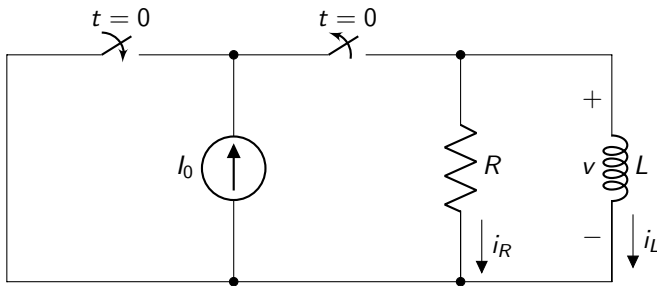上海纽约大学
NYU SHANGHAI $t \rightarrow \infty$


- Inductor current $i_L(t \rightarrow \infty)$?
- Inductor voltage $v(t \rightarrow \infty)$?
- Stored energy in the inductor $w(t \rightarrow \infty)$?

RL circuits (Natural response)

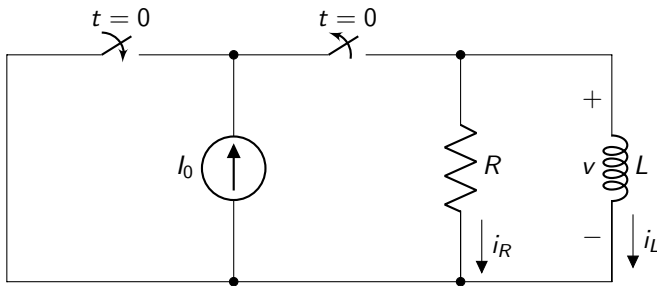上海纽约大学
NYU SHANGHAI $t \rightarrow \infty$


- Inductor current $i_L(t \rightarrow \infty)$? $i_L(t \rightarrow \infty) = 0$
- Inductor voltage $v(t \rightarrow \infty)$?
- Stored energy in the inductor $w(t \rightarrow \infty)$?

RL circuits (Natural response)

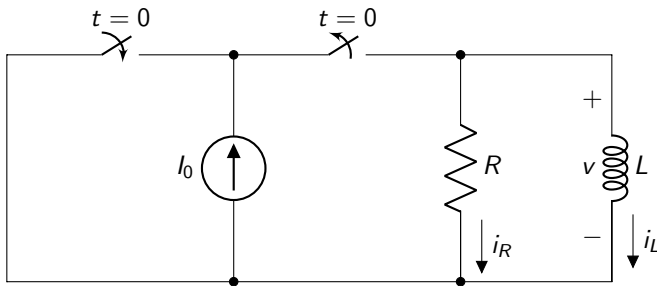上海纽约大学
NYU SHANGHAI $t \rightarrow \infty$

- Inductor current $i_L(t \rightarrow \infty)$? $i_L(t \rightarrow \infty) = 0$
- Inductor voltage $v(t \rightarrow \infty)$? $v(t \rightarrow \infty) = 0$
- Stored energy in the inductor $w(t \rightarrow \infty)$?

RL circuits (Natural response)

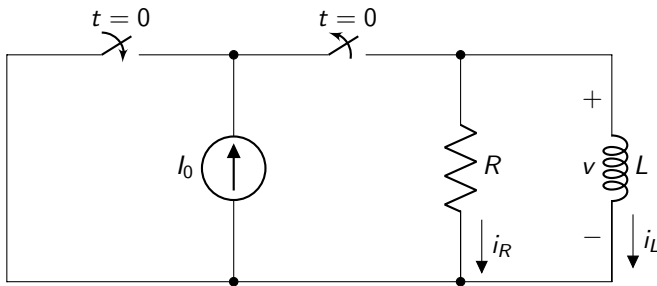上海纽约大学
NYU SHANGHAI $t \rightarrow \infty$

- Inductor current $i_L(t \rightarrow \infty)$? $i_L(t \rightarrow \infty) = 0$
- Inductor voltage $v(t \rightarrow \infty)$? $v(t \rightarrow \infty) = 0$
- Stored energy in the inductor $w(t \rightarrow \infty)$? $w(t \rightarrow \infty) = 0$

RL circuits (Natural response)



上海纽约大学
NYU SHANGHAI

Determination of $i_L(t)$

For $t \geq 0$, we can write:

- $i_L(t) + i_R(t) = 0$
- $v(t) = L \frac{di_L(t)}{dt} = Ri_R(t)$
- $L \frac{di_L(t)}{dt} + Ri_L(t) = 0$
- $\tau \frac{di_L(t)}{dt} + i_L(t) = 0$

My derivation:

$$\tau \frac{di}{dt} + i = 0$$

$$\int_{i_0}^{i(t)} \frac{di}{-i} = \int_0^t \frac{-1}{\tau} dt$$

$$\ln \frac{i(t)}{i_0} = -\frac{t}{\tau}$$

$$\frac{i(t)}{i_0} = e^{-\frac{t}{\tau}}$$

Time constant τ

The unit of the ratio $\frac{L}{R}$ is proportional to **time** (usually in s, or ms, or μ s...).

$$\tau = \frac{L}{R} \quad T = RC$$


This ratio $\frac{L}{R}$ is called the **time constant** τ with $\tau = \frac{L}{R}$.

RL circuits (Natural response)




RL circuit natural response

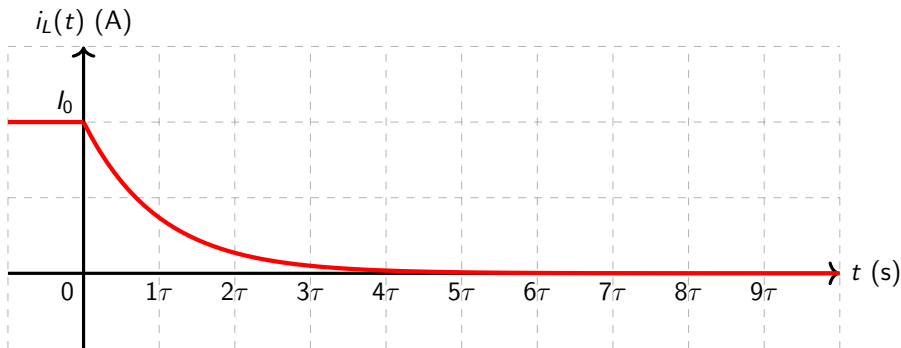
$$i_L(t) = \begin{cases} I_0, & \text{if } t \leq 0 \\ I_0 e^{-\frac{t}{\tau}}, & \text{if } t \geq 0 \end{cases}$$




RL circuits (Natural response)

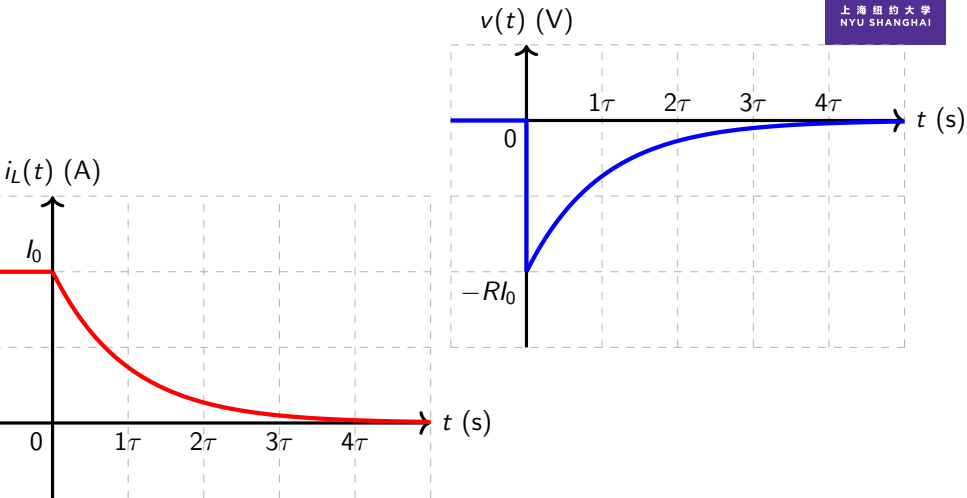上海纽约大学
NYU SHANGHAI

RL circuits (Forced response)

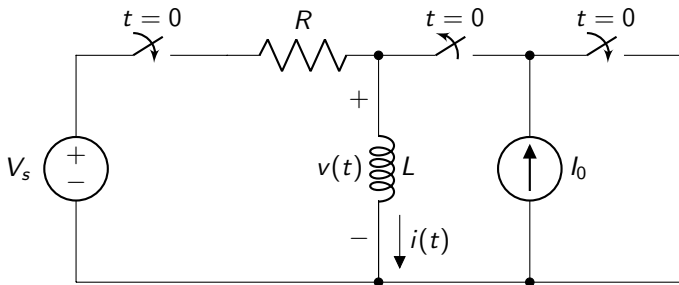上海纽约大学
NYU SHANGHAI

RL circuits (Forced response)

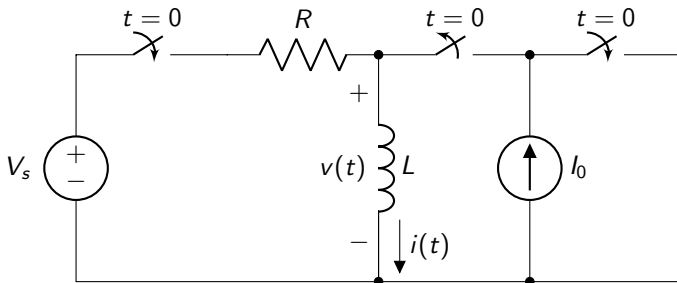
上海 纽约 大学
NYU SHANGHAI

$t < 0$

For $t < 0$, we suppose that the circuit was in that state for a *long* time

- Inductor current $i(t = 0^-)$?
- Inductor voltage $v(t = 0^-)$?
- Stored energy in the inductor $w(t = 0^-)$?


RL circuits (Forced response)

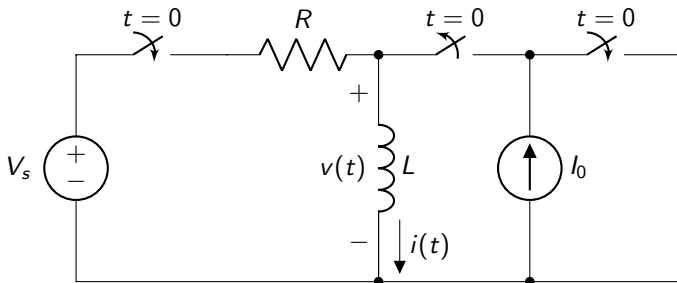上海 纽约 大学
NYU SHANGHAI $t < 0$

For $t < 0$, we suppose that the circuit was in that state for a *long* time

- Inductor current $i(t = 0^-)$? $i(t = 0^-) = I_0$
- Inductor voltage $v(t = 0^-)$?
- Stored energy in the inductor $w(t = 0^-)$?


RL circuits (Forced response)

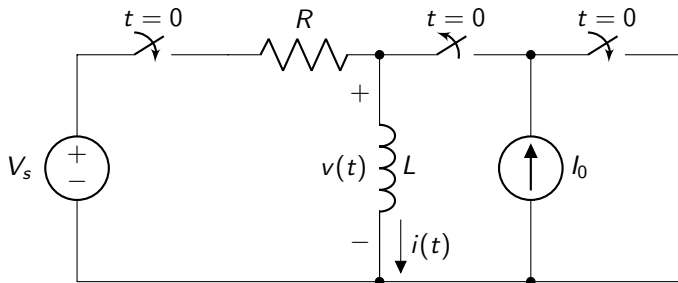上海纽约大学
NYU SHANGHAI $t < 0$

For $t < 0$, we suppose that the circuit was in that state for a *long* time

- Inductor current $i(t = 0^-)$? $i(t = 0^-) = I_0$
- Inductor voltage $v(t = 0^-)$? $v(t = 0^-) = 0$
- Stored energy in the inductor $w(t = 0^-)$?


RL circuits (Forced response)

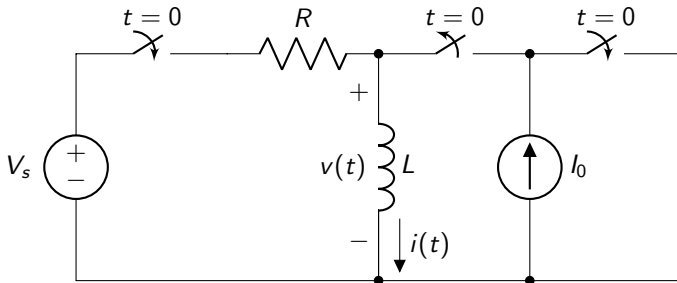上海 纽约 大学
NYU SHANGHAI $t < 0$

For $t < 0$, we suppose that the circuit was in that state for a *long* time


- Inductor current $i(t = 0^-)$? $i(t = 0^-) = I_0$
- Inductor voltage $v(t = 0^-)$? $v(t = 0^-) = 0$
- Stored energy in the inductor $w(t = 0^-)$? $w(t = 0^-) = \frac{1}{2} L \cdot I_0^2$

RL circuits (Forced response)

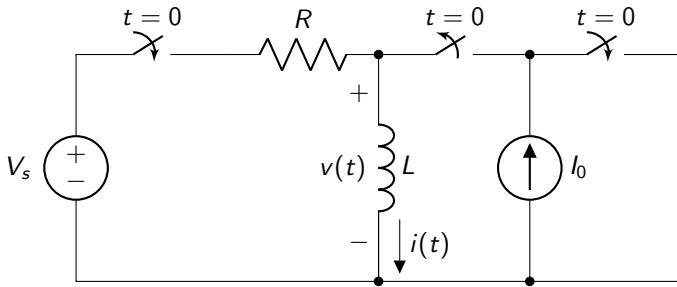上海 纽约 大学
NYU SHANGHAI $t > 0$


- Inductor current $i(t = 0^+)$?
- Inductor voltage $v(t = 0^+)$?
- Stored energy in the inductor $w(t = 0^+)$?

RL circuits (Forced response)

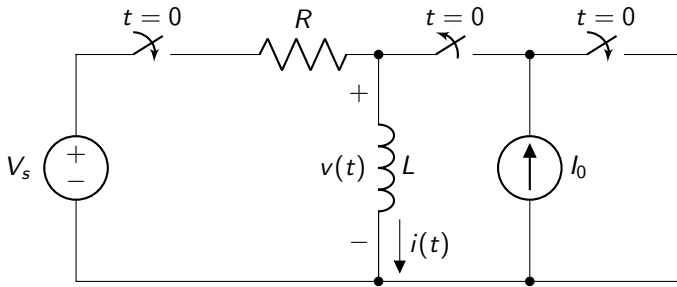上海 纽约 大学
NYU SHANGHAI $t > 0$


- Inductor current $i(t = 0^+)$? $i(t = 0^+) = I_0$
- Inductor voltage $v(t = 0^+)$?
- Stored energy in the inductor $w(t = 0^+)$?

RL circuits (Forced response)

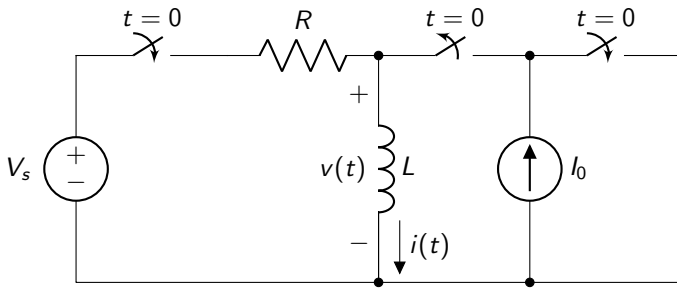上海 纽约 大学
NYU SHANGHAI $t > 0$


- Inductor current $i(t = 0^+)$? $i(t = 0^+) = I_0$
- Inductor voltage $v(t = 0^+)$? $v(t = 0^+) = V_s - RI_0$
- Stored energy in the inductor $w(t = 0^+)$?

RL circuits (Forced response)

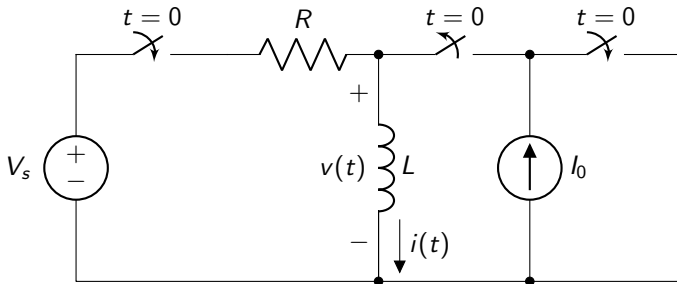上海纽约大学
NYU SHANGHAI $t > 0$


- Inductor current $i(t = 0^+)$? $i(t = 0^+) = I_0$
- Inductor voltage $v(t = 0^+)$? $v(t = 0^+) = V_s - RI_0$
- Stored energy in the inductor $w(t = 0^+)$? $w(t = 0^+) = \frac{1}{2}L \cdot I_0^2$

RL circuits (Forced response)

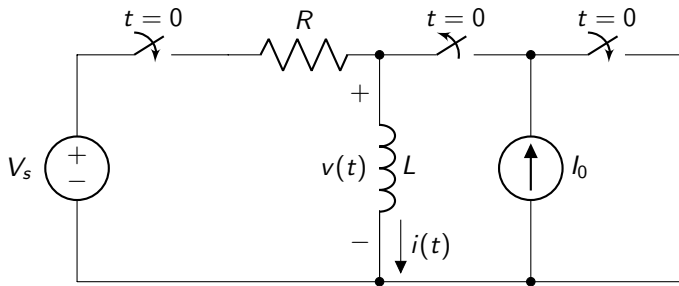上海 纽约 大学
NYU SHANGHAI $t \rightarrow \infty$


- Inductor current $i(t \rightarrow \infty)$?
- Inductor voltage $v(t \rightarrow \infty)$?
- Stored energy in the inductor $w(t \rightarrow \infty)$?

RL circuits (Forced response)

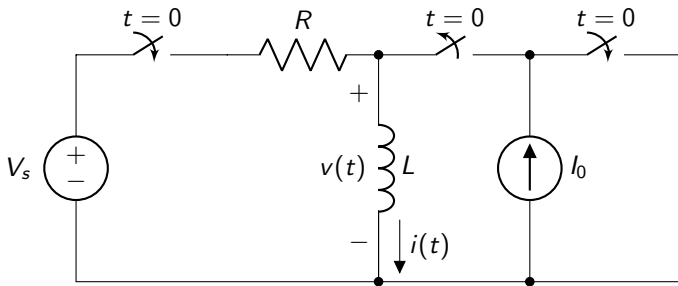上海 纽约 大学
NYU SHANGHAI $t \rightarrow \infty$


- Inductor current $i(t \rightarrow \infty)$? $i(t \rightarrow \infty) = \frac{V_s}{R}$
- Inductor voltage $v(t \rightarrow \infty)$?
- Stored energy in the inductor $w(t \rightarrow \infty)$?

RL circuits (Forced response)

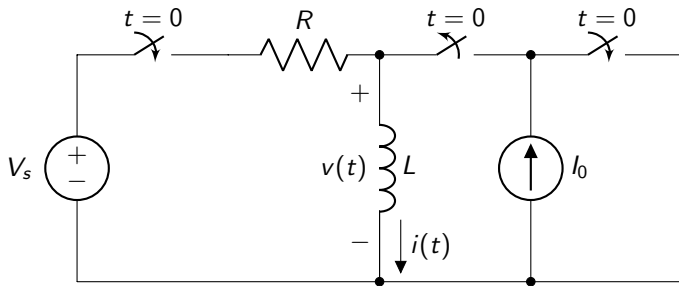上海 纽约 大学
NYU SHANGHAI $t \rightarrow \infty$

- Inductor current $i(t \rightarrow \infty)$? $i(t \rightarrow \infty) = \frac{V_s}{R}$
- Inductor voltage $v(t \rightarrow \infty)$? $v(t \rightarrow \infty) = 0$
- Stored energy in the inductor $w(t \rightarrow \infty)$?

RL circuits (Forced response)

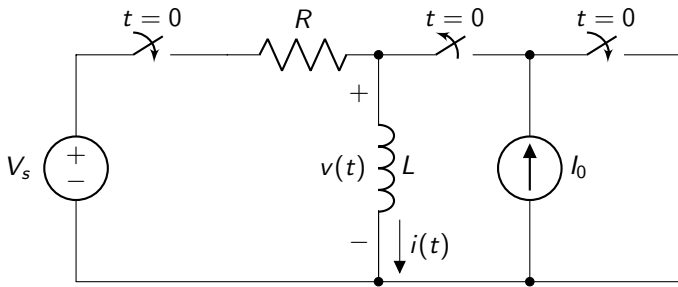上海 纽约 大学
NYU SHANGHAI $t \rightarrow \infty$

- Inductor current $i(t \rightarrow \infty)$? $i(t \rightarrow \infty) = \frac{V_s}{R}$
- Inductor voltage $v(t \rightarrow \infty)$? $v(t \rightarrow \infty) = 0$
- Stored energy in the inductor $w(t \rightarrow \infty)$? $w(t \rightarrow \infty) = \frac{1}{2} \frac{L}{R^2} V_s^2$

RL circuits (Forced response)



Determination of $i(t)$

For $t \geq 0$, we can write:

$$\blacksquare v(t) = L \frac{di(t)}{dt}$$

$$\blacksquare V_s = R \cdot i(t) + v(t) \quad \Rightarrow \quad \tau \frac{di(t)}{dt} + i(t) = \frac{V_s}{R}$$

Solution

Solution similar to natural response.


By setting $i_2(t) = i(t) - \frac{V_s}{R}$, we get: $\tau \frac{di_2(t)}{dt} + i_2(t) = 0$

RL circuits (Forced response)

上海交通大学
SJTU

RL circuit forced response
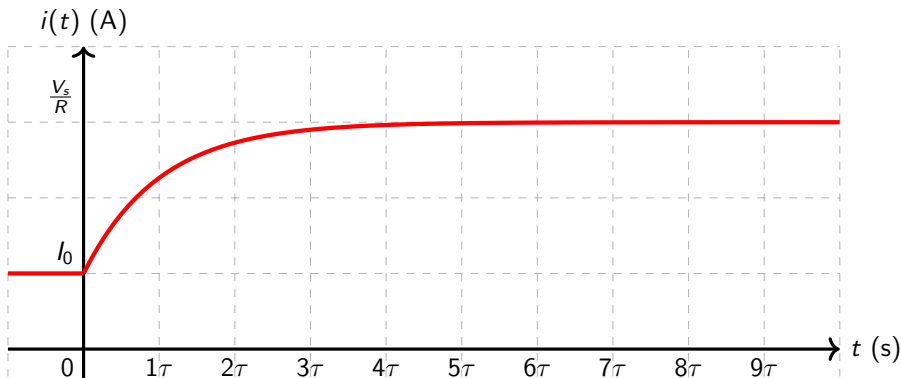
$$i(t) = \begin{cases} I_0, & \text{if } t \leq 0 \\ (I_0 - \frac{V_s}{R})e^{-\frac{t}{\tau}} + \frac{V_s}{R}, & \text{if } t \geq 0 \end{cases}$$




RL circuits (Forced response)

上海交通大学
SHANGHAI JIAO TONG UNIVERSITY

RL circuit forced response
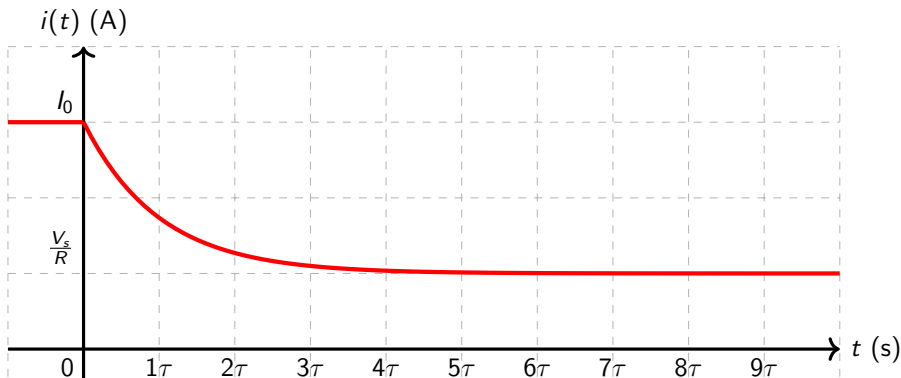
$$v(t) = \begin{cases} V_0, & \text{if } t \leq 0 \\ (V_0 - V_s)e^{-\frac{t}{\tau}} + V_s, & \text{if } t \geq 0 \end{cases}$$



RL circuits



Generic method

- ① Zero-out all the independent sources, and determine R_{eq} , L_{eq} and the time constant $\tau = \frac{L_{eq}}{R_{eq}}$
- ② Determine the inductor current $i(0^-)$ before the change ($t \leq 0$) by DC analysis, meaning considering the inductor is **equivalent to a short-circuit**
- ③ Find the steady-state inductor current $i(t \rightarrow \infty)$ by using DC analysis, still considering the inductor is **equivalent to a short-circuit**
- ④ The response (for $t \geq 0$) is then:
$$i(t) = i(t \rightarrow \infty) + (i(0^-) - i(t \rightarrow \infty))e^{-t/\tau}$$