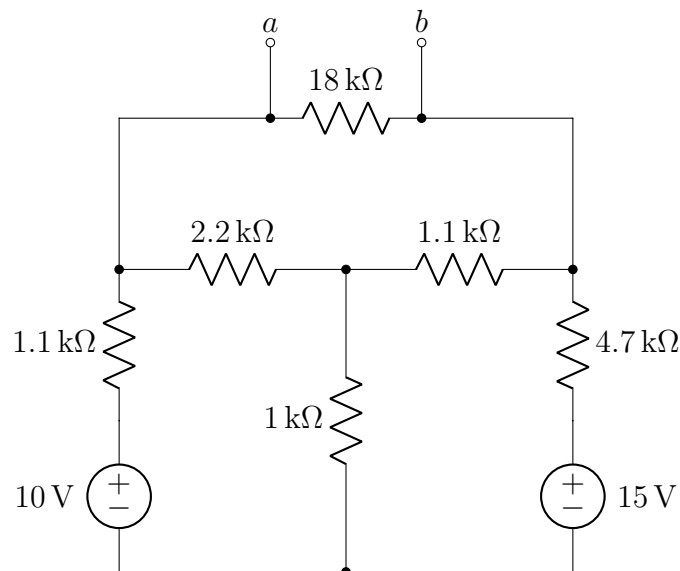


## Lab assignment 05

### -

## Thevenin/Norton

### Exercise 1 - Thevenin and Norton equivalence



#### Pre-lab:

- Analytically determine the **Thevenin equivalent circuit** for terminals  $ab$
- Analytically determine the **Norton equivalent circuit** for terminals  $ab$
- Predict the theoretical voltages  $V_{ab}$  across terminals  $ab$  when a load resistor  $R_L$  is connected to the terminals  
Consider the following values for  $R_L$ :  $100\Omega$ ,  $1\text{ k}\Omega$ ,  $10\text{ k}\Omega$ , and  $100\text{ k}\Omega$

#### During the lab:

- Experimentally measure the open-circuit voltage  $V_{oc}$  across terminals  $ab$
- Experimentally measure the short-circuit current  $I_{sc}$  through terminals  $ab$
- Experimentally measure the equivalent resistor of terminals  $ab$  while zeroing-out all the sources
- Determine the **experimental Thevenin and Norton equivalent circuits**
- Connect different load resistors  $R_L$  to terminals  $ab$  and measure  $V_{ab}$  for each resistance value
- Wire the equivalent Thevenin circuit

- Connect different load resistors  $R_L$  to the equivalent circuit and measure  $V'_{ab}$  for each resistance value
- Discuss about your findings with the instructor