

Circuits

-

Superposition & Thévenin/Norton equivalence

NYU
上海



SHANGHAI
纽约大学

Spring 2022

Superposition



上海 纽约 大学
NYU SHANGHAI

Linear circuits

We will analyze linear circuits.

One of the most interesting consequence of linearity is **superposition**

Superposition

The response of a circuit having more than one independent source can be obtained by **adding the responses** caused by the **independent sources acting alone**


Superposition

上海交通大学
SHANGHAI JIAO TONG UNIVERSITY
GHAI

Turning off sources

Since the response of the circuit can be obtained by superposition, **all the independent sources but one have to be turned off** at a time


Voltage source turned off (zeroed out)

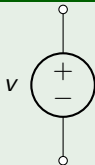

When turned off \Rightarrow



Current source turned off (zeroed out)

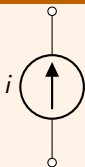


When turned off \Rightarrow



Superposition



Determine the voltage v

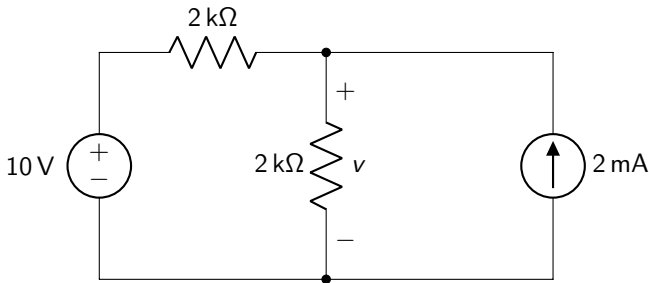

Nodal analysis (for example):


$$\blacksquare 2\text{ mA} + \frac{10\text{ V} - v}{2\text{ k}\Omega} = \frac{v}{2\text{ k}\Omega}$$

$$\blacksquare v = 7\text{ V}$$

Superposition




Analysis 1

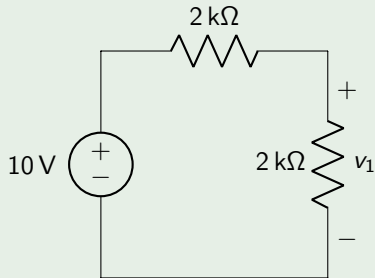

■ $v_1 = 5\text{ V}$

Analysis 2

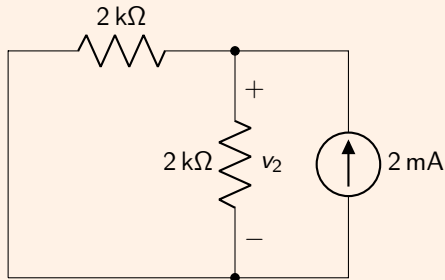

■ $v_2 = 2\text{ V}$


Superposition

■ $v = v_1 + v_2 = 7\text{ V}$

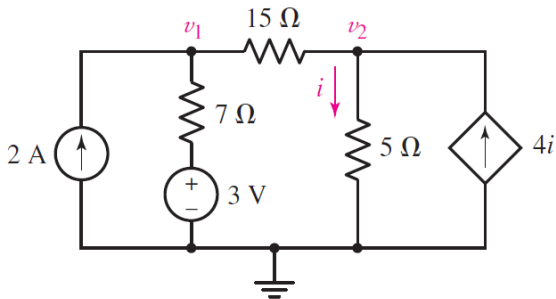Examples



Determine the voltage across each current source.



Superposition



上海纽约大学
NYU SHANGHAI

Summary

- Superposition relies on linearity
- Analyze as many circuits as there are **independent sources**
- Dependent sources are never zeroed out
- More circuits to analyze, sometimes leading to more equations. . .
- But the different circuits are also simpler to analyze, with simpler equations


Source transformation



Concept

A voltage source with a resistor in series is **equivalent** to a current source with a resistor in parallel



Equivalence

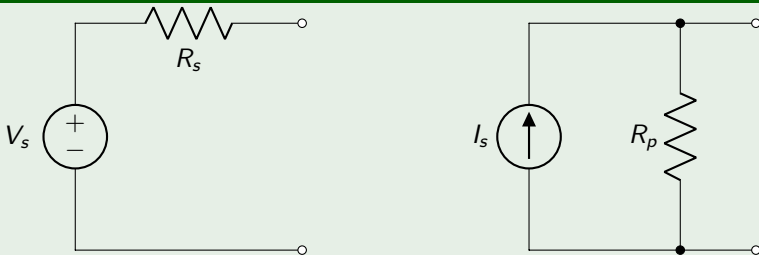

Validity

The equivalence holds if both circuits have the **same voltage-current relationship** at their terminals

Source transformation

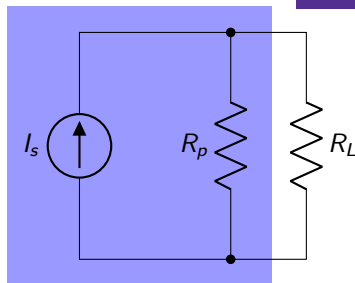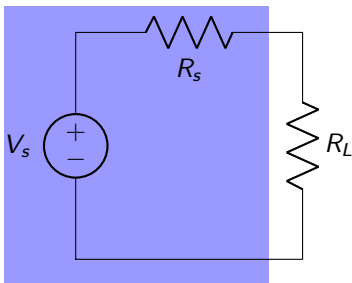上海纽约大学
NYU SHANGHAI

Terminal

$$\blacksquare V = \frac{R_L}{R_s + R_L} V_s$$

$$\blacksquare I = \frac{V_s}{R_s + R_L}$$

Terminal



$$\blacksquare V = \frac{R_L}{R_p + R_L} R_p I_s$$

$$\blacksquare I = \frac{R_p I_s}{R_p + R_L}$$

Source transformation



Equivalence

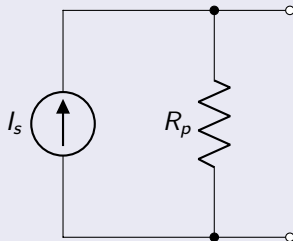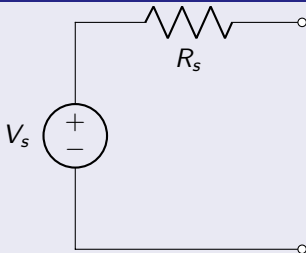


Equivalent when:

- $R_s = R_p = R$
- $V_s = RI_s$

Source transformation

上海纽约大学
NYU SHANGHAI

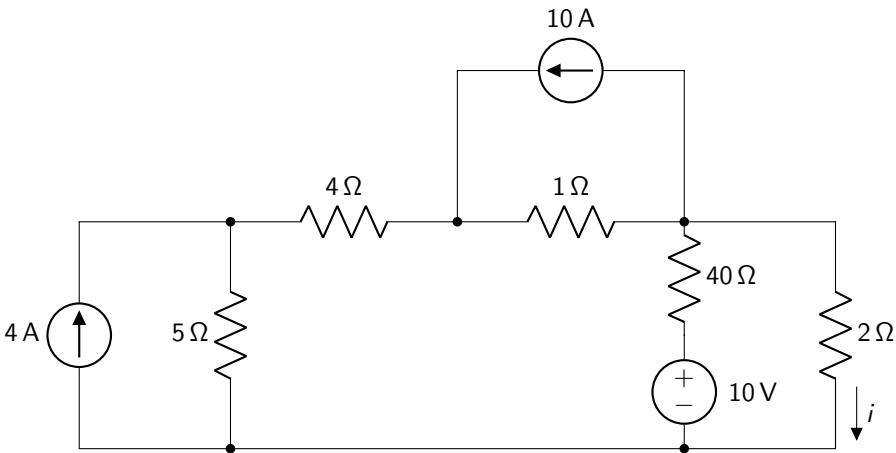Apply multiple source transformation to determine i




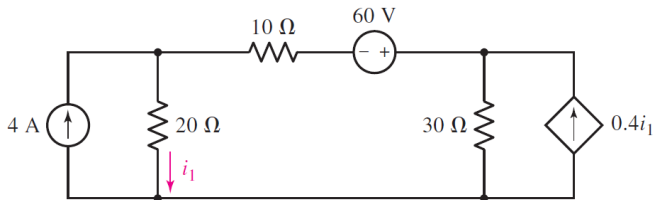Examples



上海纽约大学
NYU SHANGHAI

Determine the source transformation should be performed or not.



Thévenin equivalent circuit



上海 纽约 大学
NYU SHANGHAI

Theorem

A **two-terminal linear circuit**, constituted of sources and resistors, is equivalent to a **voltage source in series with a resistor**

Application



Usually, it allows us to simplify the analysis of a circuit when only a few values need to be determined

for example, previous example. . .

Thévenin equivalent circuit

上海交通大学
SJTU

Equivalence

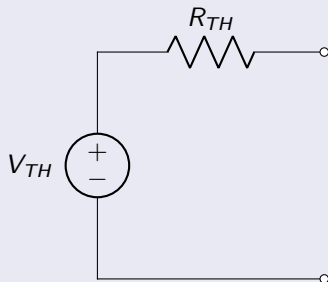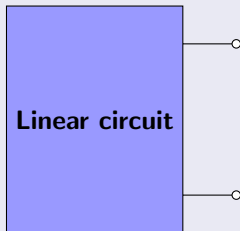

How to determine the Thévenin equivalence?


Several methods:

- 1 Evaluate the **open-circuit voltage**
- 2 Evaluate the **short-circuit current**
- 3 Evaluate the **resistor value** by turning off every independent source

Thévenin equivalent circuit

上海纽约大学
NYU SHANGHAI

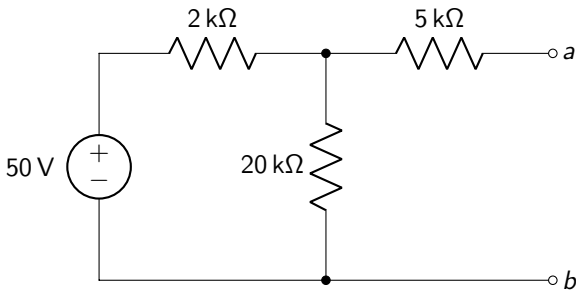
Find the Thévenin equivalence (terminal ab)



Thévenin equivalent circuit

上海纽约大学
NYU SHANGHAI

① Evaluate the **open-circuit voltage**

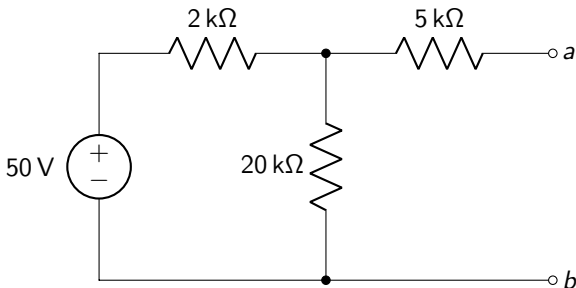


(no current in 5 k Ω resistor)

$$V_{OC} = \frac{20}{22} 50 \text{ V} = 45.45 \text{ V}$$

Thévenin equivalent circuit

上海纽约大学
NYU SHANGHAI

2 Evaluate the **short-circuit current**

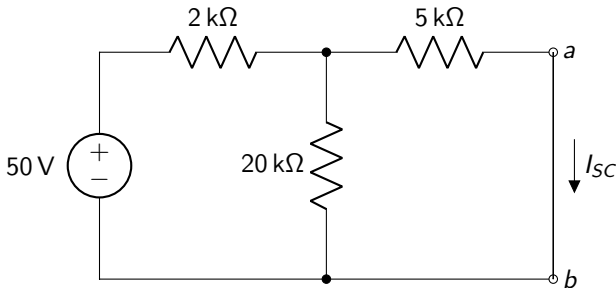


(current $I_{SC}/4$ in the $20\text{ k}\Omega$ resistor)

$$50\text{ V} = \left(\frac{5}{4} 2\text{ k}\Omega + 5\text{ k}\Omega\right) I_{SC} \quad \Rightarrow \quad I_{SC} = 6.67\text{ mA}$$

Thévenin equivalent circuit

上海纽约大学
NYU SHANGHAI

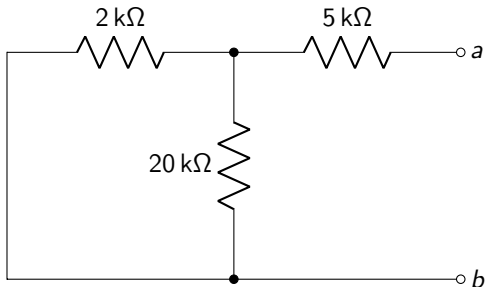- ③ Evaluate the **resistor value** by turning off every independent source





$$R_{eq} = 5 \text{ k}\Omega + \frac{2 \text{ k}\Omega \cdot 20 \text{ k}\Omega}{22 \text{ k}\Omega} = 6.82 \text{ k}\Omega$$

Thévenin equivalent circuit



Equivalence

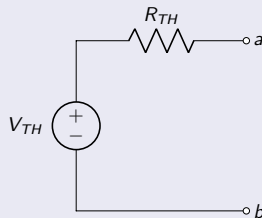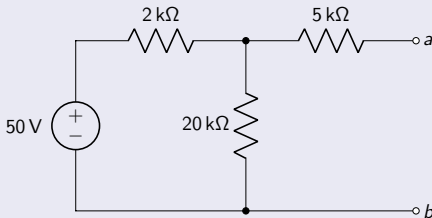

Values

Actually, only 2 experiments are necessary:

- $V_{TH} = V_{OC} = 45.45 \text{ V}$
- $R_{TH} = R_{eq} = 6.82 \text{ k}\Omega$
- $V_{TH} = R_{TH} \cdot I_{SC}$

Thévenin equivalent circuit



上海 纽约 大学
NYU SHANGHAI

Presence of dependent sources

It seems that determining the **open-circuit voltage** and the **equivalent resistance** (when independent sources are turned off) is the most straightforward technique to find Thévenin equivalence

But, what happens when we have dependent sources?

Answer: connect a source to the terminals

- connect a voltage source (or a current source) to the terminals
- the source value can be **any value**

- $R_{eq} = \frac{V}{I}$


Thévenin equivalent circuit



上海纽约大学
NYU SHANGHAI


Determining R_{eq} with dependent sources

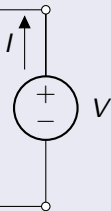Linear circuit
Independent
sources are off



or

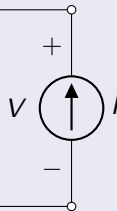Linear circuit
Independent
sources are off



R_{eq} with dependent sources


Beware!

With dependent sources, it is possible to find **negative values** for R_{eq} !!!

Thévenin equivalent circuit

上海纽约大学
NYU SHANGHAI

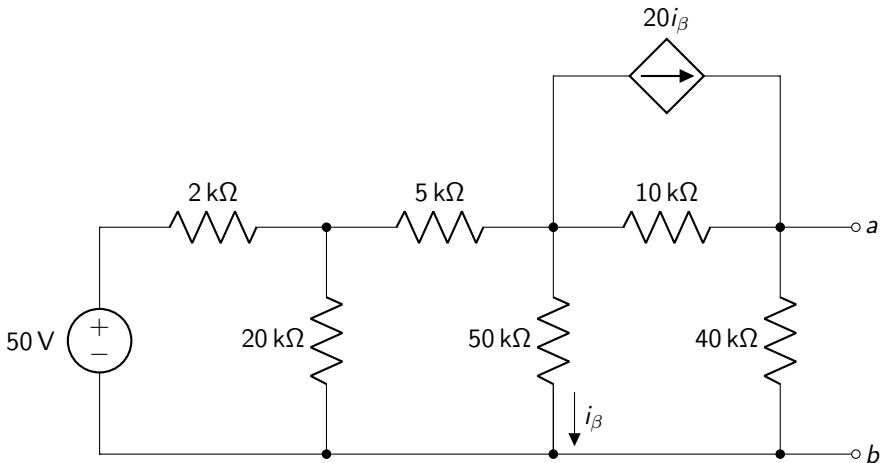Find the Thévenin equivalence (terminal ab)



Norton equivalent circuit



上海纽约大学
NYU SHANGHAI

Theorem

A **two-terminal linear circuit**, constituted of sources and resistors, is equivalent to a **current source in parallel with a resistor**



Application

Usually, it allows us to simplify the analysis of a circuit when only a few values need to be determined

for example, previous example. . .

Norton equivalent circuit

Equivalence

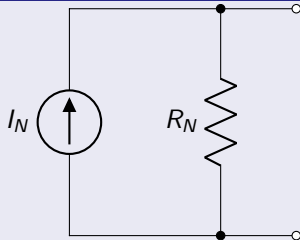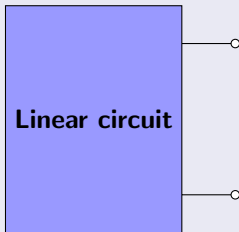

How to determine the Norton equivalence?



Several methods:

- 1 Evaluate the **open-circuit voltage**
- 2 Evaluate the **short-circuit current**
- 3 Evaluate the **resistor value** by turning off every independent source

Norton equivalent circuit



Equivalence

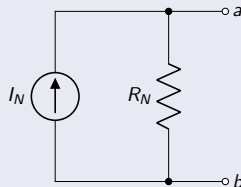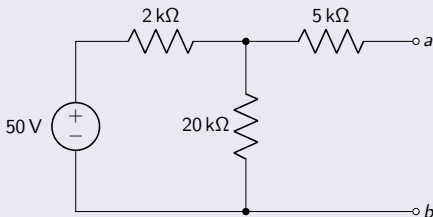

Values

Actually, only 2 experiments are necessary:

- $I_N = I_{SC} = 6.67 \text{ mA}$
- $R_N = R_{eq} = 6.82 \text{ k}\Omega$
- $I_N = \frac{V_{OC}}{R_N}$

Norton equivalent circuit

上海纽约大学
NYU SHANGHAI

Find the Norton equivalence (terminal ab)

