

Exercises 07

- First order circuits


Exercise 1 - RC circuit

① $\frac{10V - v}{20k\Omega} + 100\mu A = \frac{v}{20k\Omega}$
 $\Rightarrow v = 6V$
 $i_1(0^-) = i_2(0^-) = \frac{v}{20k\Omega} = 0.3mA$

② $i_2(0^+) = 0.3mA$
 $i_1(0^+) = -0.3mA$

• Determine $i_1(0^-)$ and $i_2(0^-)$.
 • Determine $i_1(0^+)$ and $i_2(0^+)$.
 • Determine $i_1(\infty)$ and $i_2(\infty)$.
 • Determine $i_1(t)$ and $i_2(t)$.

③ $i_1(t) \cdot 5k\Omega + i_2(t) \cdot 10k\Omega + i_1(t) \cdot 5k\Omega = 0$
 $i_1(t) \cdot 10k\Omega + i_2(t) \cdot 10k\Omega = 0$
 $i_1(t) = -i_2(t)$

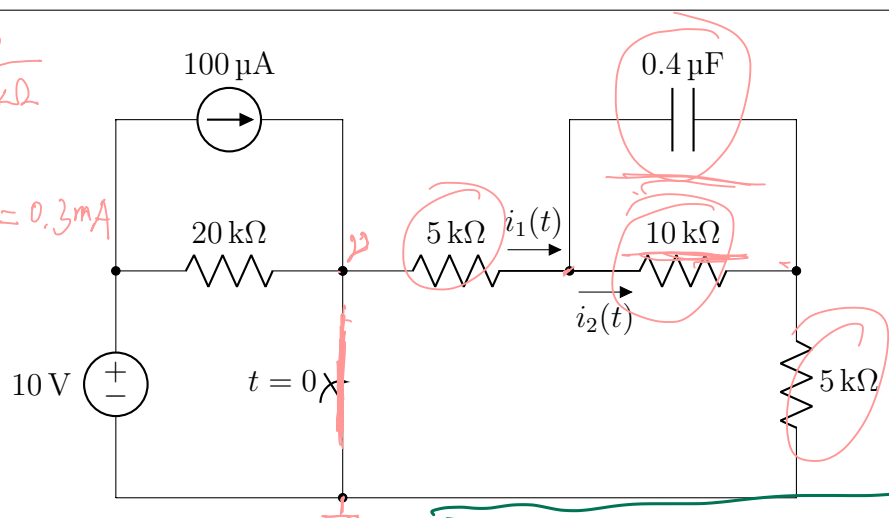


Exercise 2 - RL circuit


① $t < 0$

• Determine $v_o(t)$, $i_1(t)$ and $i_2(t)$.

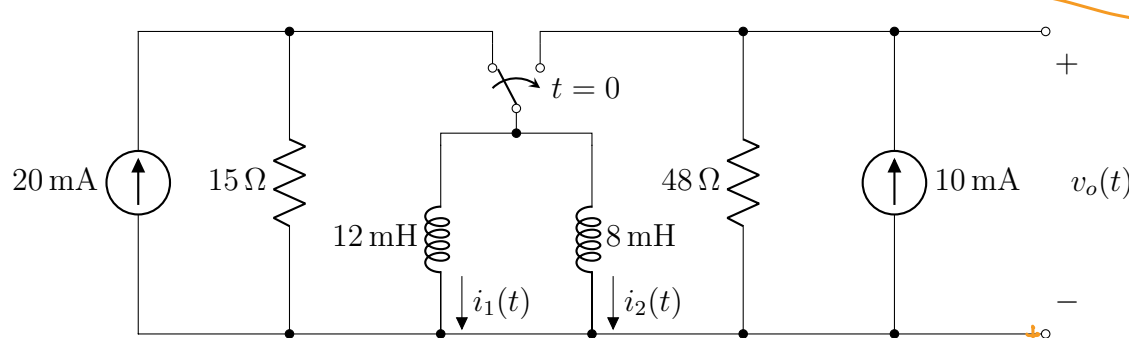② $i(t) = i(\infty) + (i(0^-) - i(\infty)) \cdot e^{-\frac{t}{\tau}}$ $\tau = \frac{L}{R}$



Exercise 2 RL circuit

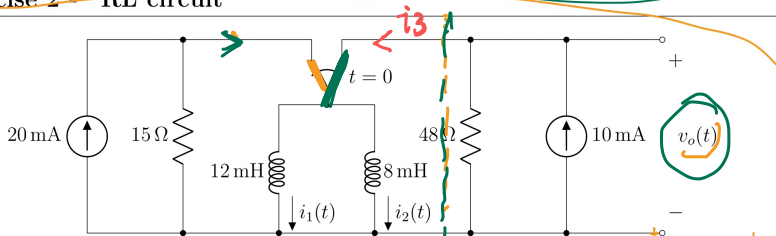

$t < 0$

• Determine $v_o(t)$, $i_1(t)$ and $i_2(t)$.

$$i(t) = i(\infty) + (i(0^-) - i(\infty)) \cdot e^{-\frac{t}{\tau}} \quad \tau = \frac{L}{R}$$

① $t < 0$

$$V_o(0^-) = 10 \text{ mA} \cdot 48 \Omega = 0.48 \text{ V}$$

$$i_1(0^-) = i_1(0^+)$$

$$i_2(0^-) = i_2(0^+)$$

$$\begin{cases} i_1(0^-) = i_1(-\infty) + \frac{1}{12 \text{ mH}} \int_{-\infty}^{0^-} v(t') dt' & i_1(-\infty) = 0 \\ i_2(0^-) = i_2(-\infty) + \frac{1}{8 \text{ mH}} \int_{-\infty}^{0^-} v(t') dt' & i_2(-\infty) = 0 \end{cases}$$

$$\Rightarrow \begin{cases} 12 \text{ mH} \cdot i_1(0^-) = 8 \text{ mH} \cdot i_2(0^-) \\ i_1(0^-) + i_2(0^-) = 20 \text{ mA} \end{cases} \Rightarrow \begin{cases} i_1(0^-) = 8 \text{ mA} \\ i_2(0^-) = 12 \text{ mA} \end{cases}$$

② $t > 0$

$$(V_o(\infty) = 48 \Omega \cdot 10 \text{ mA} = 0.48 \text{ V} \quad \text{X}) \quad V_o(\infty) = 0 \text{ V}$$

$$i_1(\infty) + i_2(\infty) = 10 \text{ mA}$$

$$\begin{cases} i_1(\infty) = i_1(0^+) + \frac{1}{12 \text{ mH}} \int_{0^+}^{\infty} v(t') dt' \\ i_2(\infty) = i_2(0^+) + \frac{1}{8 \text{ mH}} \int_{0^+}^{\infty} v(t') dt' \end{cases} \Rightarrow 12 \text{ mH} \cdot (i_1(\infty) - i_1(0^+)) = 8 \text{ mH} \cdot (i_2(\infty) - i_2(0^+))$$

$$i_1(\infty) = 4 \text{ mA} \quad i_2(\infty) = 6 \text{ mA}$$

$$\textcircled{3} \quad L_{eq} = \frac{12 \text{ mH} \cdot 8 \text{ mH}}{12 \text{ mH} + 8 \text{ mH}} = 4.8 \text{ mH} \quad \tau = \frac{L}{R} = \frac{4.8 \text{ mH}}{48 \Omega} = 0.1 \text{ ms}$$

$$i_1(t) = 4 \text{ mA} + (8 \text{ mA} - 4 \text{ mA}) \cdot e^{-t/\tau} = 4 \text{ mA} \cdot (1 + e^{-t/\tau})$$

$$i_2(t) = 6 \text{ mA} + (12 \text{ mA} - 6 \text{ mA}) \cdot e^{-t/\tau} = 6 \text{ mA} \cdot (1 + e^{-t/\tau})$$

$$v_o(t) = L_1 \cdot \frac{di_1(t)}{dt} = 12 \text{ mH} \cdot \left(4 \text{ mA} \cdot \frac{-1}{\tau} \cdot e^{-t/\tau} \right) = -0.48 \text{ V} \cdot e^{-t/\tau} \quad 0 \leq t < \infty$$

$$i_L(t) = i_L(0^-) + (i_L(0^+) - i_L(0^-)) \cdot e^{-t/\tau} \quad \text{RL}$$

$$\Rightarrow v_L(t)$$

Spring 2022

NYU
上海




SHANGHAI
纽约大学

$$v_C(0^-) = v_C(0^+) \Rightarrow i_C(0^+) \quad \left. \begin{array}{l} i_C(0^-), v_C(0^-) \end{array} \right\} \Rightarrow v_C(t) = v_C(0^-) + (v_C(0^+) - v_C(0^-)) \cdot e^{-t/\tau}$$

Exercise 3 - Natural response RL circuit 1

$$\Rightarrow i_C(t)$$

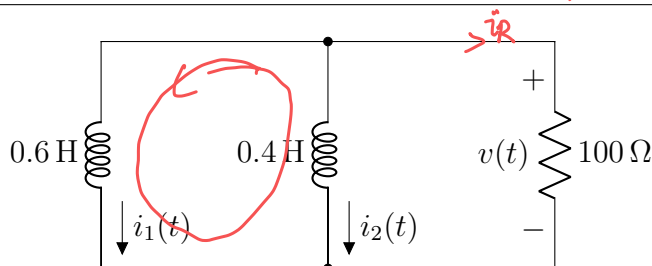

At $t = 0^-$, the inductor currents are:

- $i_1(0^-) = 1 \text{ mA}$
- $i_2(0^-) = -1 \text{ mA}$

Determine $v(t)$ for $t \geq 0$.

$i_1(0^-) + i_2(0^-) = i_3(t) = 0$ No current in the resistor.
There is no reason to have non-zero i_3 .
The current will continue flowing between the inductors.
 $v(t) = 0 \quad t \geq 0$

Exercise 4 - Natural response RL circuit 2

With the same circuit, the initial conditions are now:

- $i_1(0^-) = 2 \text{ mA}$
- $i_2(0^-) = -1 \text{ mA}$


Determine $v(t)$ for $t \geq 0$.

$$i_R(t) = -i_1(t) - i_2(t) \quad i_1(0^-) = i_1(0^+) = 2 \text{ mA} \quad i_2(0^-) = -1 \text{ mA}$$

$$i_R(0^+) = -1 \text{ mA} \Rightarrow v(0^+) = -0.1 \text{ V}$$

$$\left. \begin{array}{l} i_1(\infty) = i_1(0^+) + \frac{1}{0.6 \text{ H}} \int_0^\infty v(t) dt \\ i_2(\infty) = i_2(0^+) + \frac{1}{0.4 \text{ H}} \int_0^\infty v(t) dt \end{array} \right\} \Rightarrow 0.6 \text{ H} \cdot (i_1(\infty) - i_1(0^+)) = 0.4 \text{ H} \cdot (i_2(\infty) - i_2(0^+))$$

Exercise 5 - Complex circuit 1

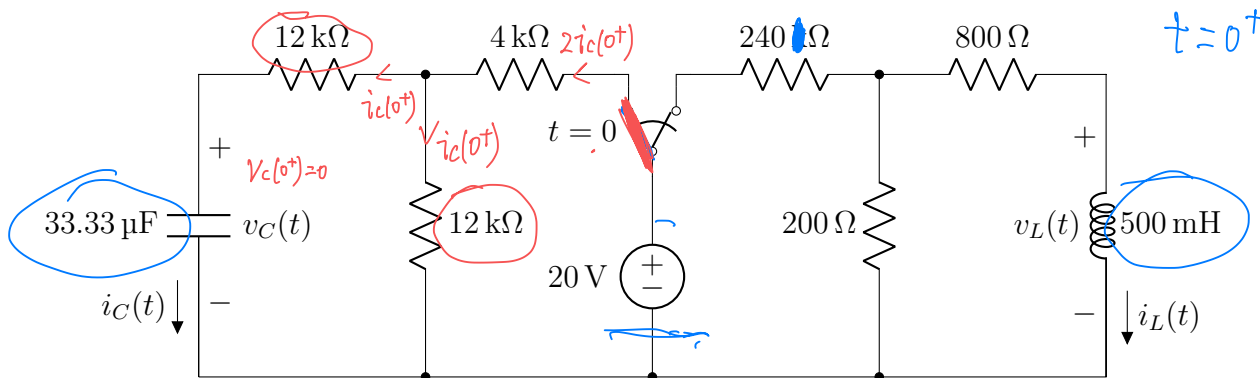

Determine $v_C(t)$, $i_C(t)$, $v_L(t)$ and $i_L(t)$ for $t \geq 0$.

$$\textcircled{1} i_L(0^-) = \frac{20 \text{ V}}{240 \Omega + 160 \Omega} \cdot \frac{200 \Omega}{200 \Omega + 800 \Omega} = 10 \text{ mA} = i_L(0^+)$$

$$v_L(0^+) = -10 \text{ mA} \cdot (200 \Omega + 800 \Omega) = -10 \text{ V}$$

$$i_L(\infty) = 0 \text{ A} \quad v_L(\infty) = 0 \text{ V} \quad R_{eq} = 1000 \Omega \quad \tau = \frac{L}{R} = \frac{0.5 \text{ H}}{1000 \Omega} = 0.5 \text{ ms}$$

$$i_L(t) = 10 \text{ mA} \cdot e^{-t/\tau} \quad v_L(t) = -10 \text{ V} \cdot e^{-t/\tau}$$

$$\textcircled{2} v_C(0^-) = 0 \text{ V} = v_C(0^+) \quad v_C(\infty) = 20 \text{ V} \cdot \frac{12 \text{ k}\Omega}{12 \text{ k}\Omega + 4 \text{ k}\Omega} = 15 \text{ V} \quad i_C(\infty) = 0$$


$$20 \text{ V} = 4 \text{ k}\Omega \cdot 2i_C(0^+) + 12 \text{ k}\Omega \cdot i_C(0^+) \Rightarrow i_C(0^+) = 1 \text{ mA}$$

$$R_{eq} = 12 \text{ k}\Omega + (12 \text{ k}\Omega \parallel 4 \text{ k}\Omega) = 15 \text{ k}\Omega \quad \tau = R \cdot C = 15 \text{ k}\Omega \cdot 33.33 \mu\text{F} = 0.5 \text{ s}$$

$$v_C(t) = 15 \text{ V} + (-15 \text{ V}) \cdot e^{-t/\tau} = 15 \text{ V} \cdot (1 - e^{-t/\tau}) \quad i_C(t) = C \cdot \frac{dv_C(t)}{dt}$$

$$= 33.33 \mu\text{F} \cdot 15 \text{ V} \cdot \frac{1}{\tau} \cdot e^{-t/\tau}$$

=

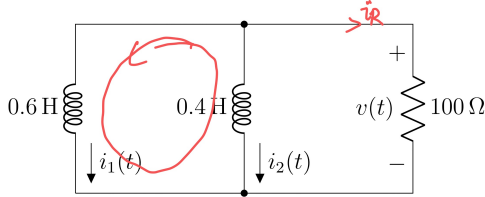

$$\begin{aligned} \dot{i}_R(\infty) &= 0 \\ \dot{i}_1(\infty) &\neq 0 \\ \dot{i}_2(\infty) &\neq 0 \end{aligned}$$

Exercise 4 - Natural response RL circuit 2

With the same circuit, the initial conditions are now:

- $i_1(0^-) = 2 \text{ mA}$
- $i_2(0^-) = -1 \text{ mA}$

Determine $v(t)$ for $t \geq 0$.

$$\begin{aligned} \dot{i}_R(t) &= -\dot{i}_1(t) - \dot{i}_2(t) & \dot{i}_1(0^+) &= \dot{i}_1(0^-) = 2 \text{ mA} & \dot{i}_2(0^+) &= -1 \text{ mA} \\ \dot{i}_R(0^+) &= -1 \text{ mA} \Rightarrow v(0^+) &= -0.1 \text{ V} \end{aligned}$$

$$\begin{aligned} \dot{i}_1(\infty) &= \dot{i}_1(0^+) + \frac{1}{0.6 \text{ H}} \int_0^\infty v(t) dt \\ \dot{i}_2(\infty) &= \dot{i}_2(0^+) + \frac{1}{0.4 \text{ H}} \int_0^\infty v(t) dt \end{aligned} \Rightarrow 0.6 \text{ H} \cdot (\dot{i}_1(\infty) - \dot{i}_1(0^+)) = 0.4 \text{ H} \cdot (\dot{i}_2(\infty) - \dot{i}_2(0^+)) \quad \textcircled{1}$$


$$\dot{i}_R(\infty) = -\dot{i}_1(\infty) - \dot{i}_2(\infty) = 0 \quad \textcircled{2} \Rightarrow \dot{i}_1(\infty) = 1.6 \text{ mA} \quad \dot{i}_2(\infty) = -1.6 \text{ mA}$$

$$L_{eq} = \frac{0.6 \text{ H} \cdot 0.4 \text{ H}}{0.6 \text{ H} + 0.4 \text{ H}} = 0.24 \text{ H} \quad \tau = \frac{L_{eq}}{R} = \frac{0.24 \text{ H}}{100 \Omega} = 2.4 \text{ ms}$$

$$\dot{i}_1(t) = 1.6 \text{ mA} + 0.4 \text{ mA} \cdot e^{-t/\tau} \quad \dot{i}_2(t) = -1.6 \text{ mA} + (-1 \text{ mA} + 1.6 \text{ mA}) \cdot e^{-t/\tau}$$

$$v(t) = (-\dot{i}_1(t) - \dot{i}_2(t)) \cdot 100 \Omega = -100 \text{ mV} \cdot e^{-t/\tau}$$

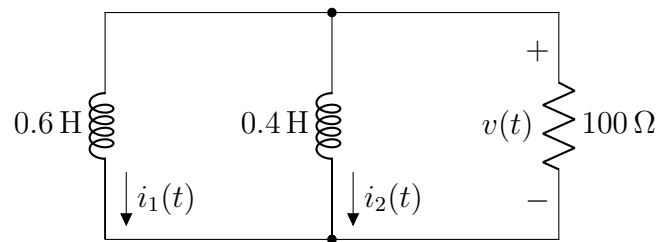Exercise 3 - Natural response RL circuit 1



At $t = 0^-$, the inductor currents are:

- $i_1(0^-) = 1 \text{ mA}$
- $i_2(0^-) = -1 \text{ mA}$

Determine $v(t)$ for $t \geq 0$.


Exercise 4 - Natural response RL circuit 2

With the same circuit, the initial conditions are now:

- $i_1(0^-) = 2 \text{ mA}$
- $i_2(0^-) = -1 \text{ mA}$


Determine $v(t)$ for $t \geq 0$.

Exercise 5 - Complex circuit 1

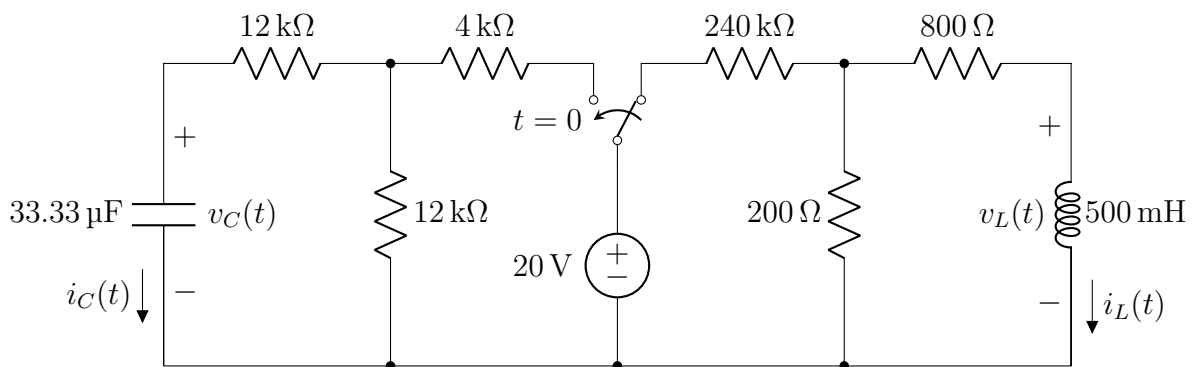

Determine $v_C(t)$, $i_C(t)$, $v_L(t)$ and $i_L(t)$ for $t \geq 0$.

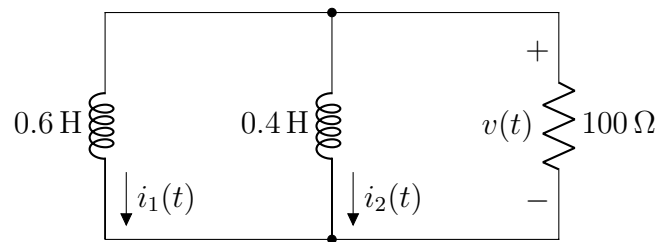Exercise 3 - Natural response RL circuit 1



At $t = 0^-$, the inductor currents are:

- $i_1(0^-) = 1 \text{ mA}$
- $i_2(0^-) = -1 \text{ mA}$

Determine $v(t)$ for $t \geq 0$.


Exercise 4 - Natural response RL circuit 2

With the same circuit, the initial conditions are now:

- $i_1(0^-) = 2 \text{ mA}$
- $i_2(0^-) = -1 \text{ mA}$

Determine $v(t)$ for $t \geq 0$.

Exercise 5 - Complex circuit 1

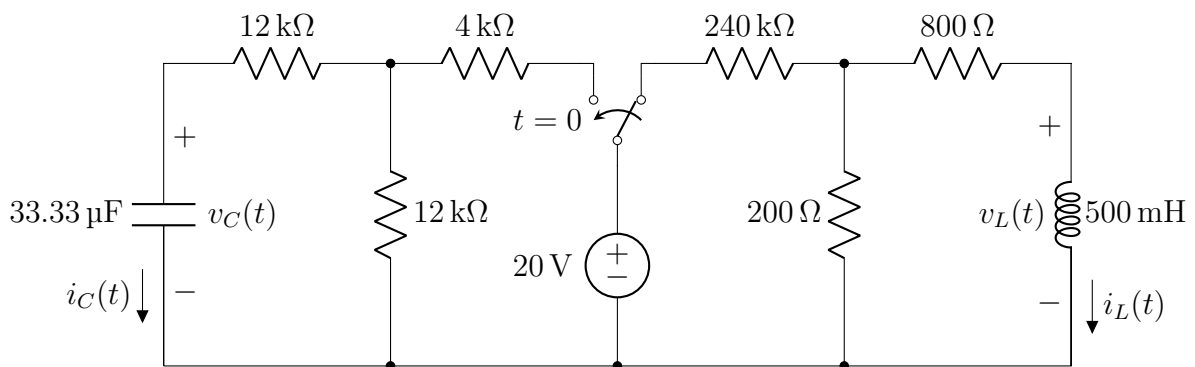

Determine $v_C(t)$, $i_C(t)$, $v_L(t)$ and $i_L(t)$ for $t \geq 0$.