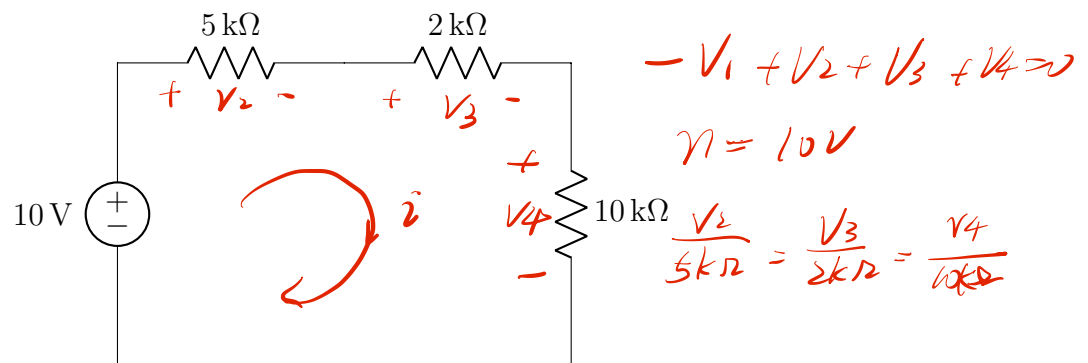


KVL \rightarrow series
KCL \rightarrow parallel.

Exercises 02


Voltage and current laws

Exercise 1 - Single current 1



Annotate the circuit with the necessary variables.
Determine the voltages for each element.

Exercise 2 - Single current 2

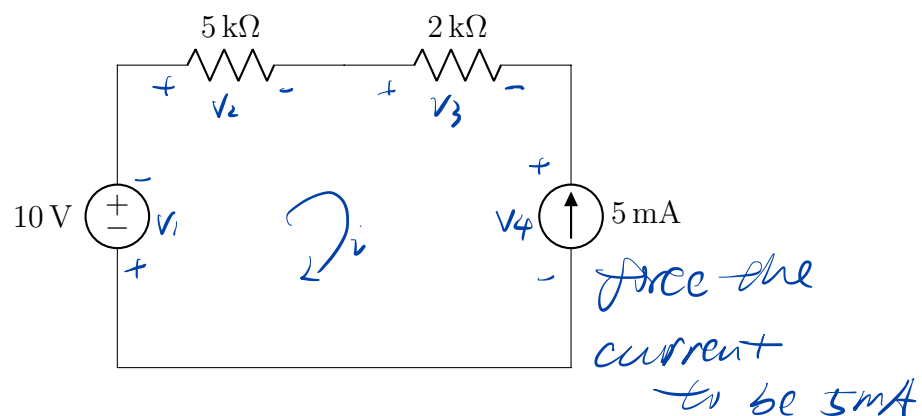


Annotate the circuit with the necessary variables.
Determine the voltages for each element.

$$V_1 = -10V$$

$$-10 + V_2 + V_3 + V_4 = 0$$


$$V_2 = 5ki \quad V_3 = 2ki$$

Exercise 3 - Single voltage 1

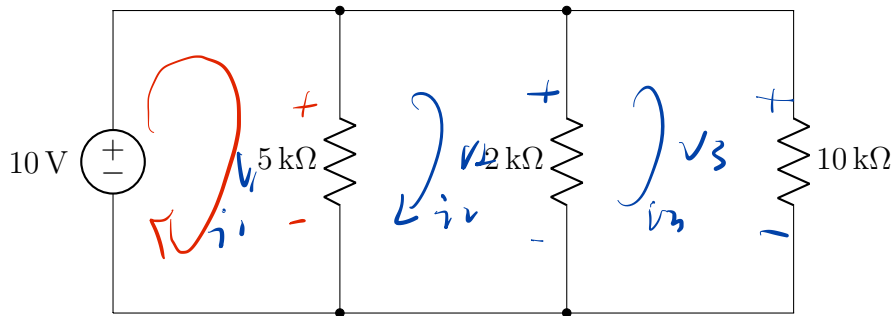


Annotate the circuit with the necessary variables.
Determine the currents for each branch.

Exercise 4 - Single voltage 2

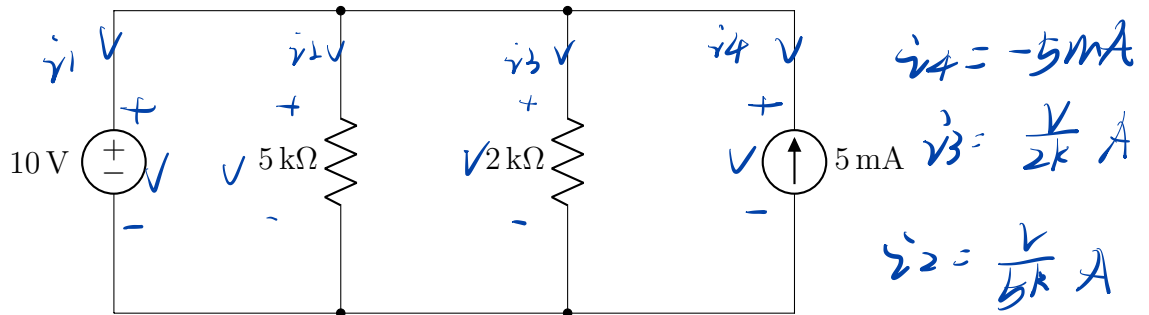

Annotate the circuit with the necessary variables.
Determine the currents for each branch.

Exercise 5 - More complex circuit

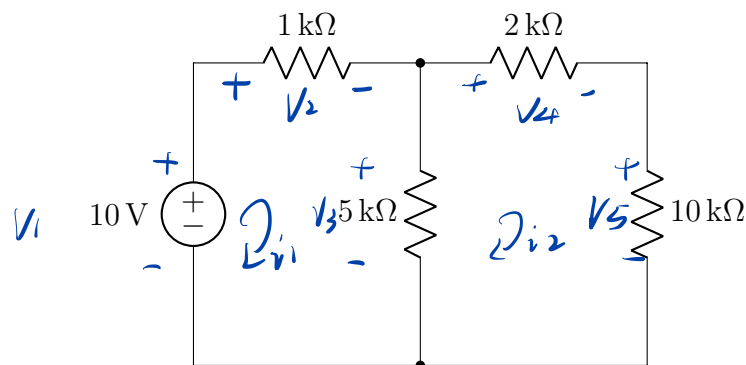


Annotate the circuit with the necessary variables.
Determine the voltages and currents for each element.

$$\begin{cases} -10 + 1k \cdot i_1 + 5k(i_1 - i_2) = 0 \\ 2k i_2 + 10k i_2 - 5k(i_2 - i_1) = 0 \end{cases}$$

$$i_1 = 1.04 \text{ mA} \quad i_2 = -0.746 \text{ mA}$$


Exercise 6 - Very complex circuit

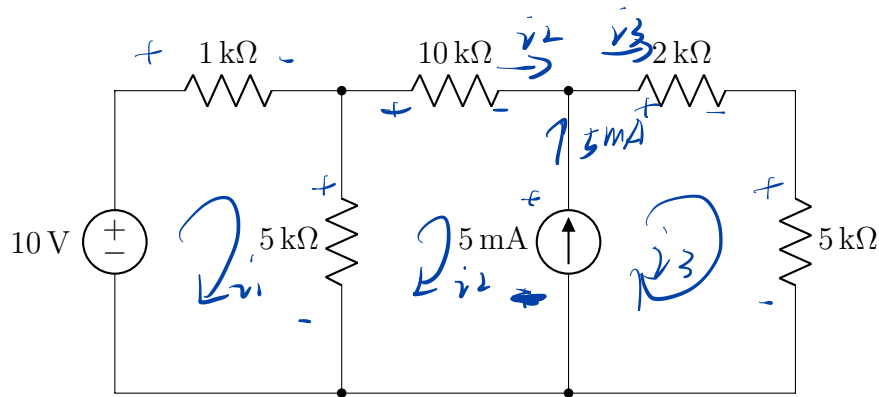

Annotate the circuit with the necessary variables.
Determine the voltages and currents for each element.

$$v_2 + 5mA = v_3$$

Exercise 7 - Very complex circuit

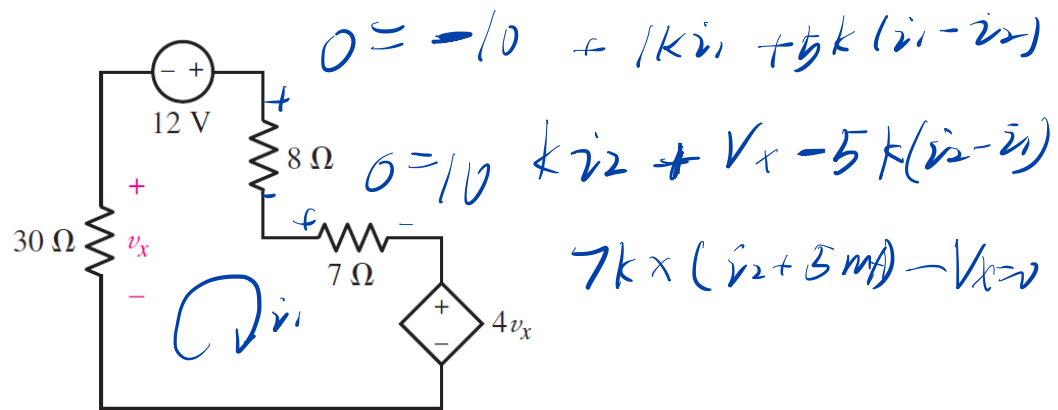

Determine the power absorbed by each of the five elements in the circuit.

$$-30 i_1 - 12 + 8 i_1 + 7 i_1 + 4 V_x = 0$$

$$V_x = -30 i_1$$