

NAME:

## Homework 3

-

## Sinusoidal analysis


**Deadline:** Wednesday, 11 May 2022, 11:55 PM

You can send your solutions in electronic version to NYU Brightspace/Assignment. **No extended deadline!**

---

**Exercise 1 - Equivalent impedance/admittance**

---

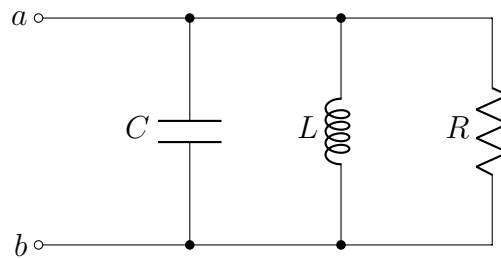


- Determine the equivalent impedance of this network, as a function of the angular frequency  $\omega$ .
- Which element is it equivalent to when  $\omega \rightarrow 0$ ?
- Which element is it equivalent to when  $\omega \rightarrow \infty$ ?
- Which element is it equivalent to when  $\omega = \frac{1}{\sqrt{LC}}$ ?

---


**Exercise 2 - Thévenin equivalence**

---

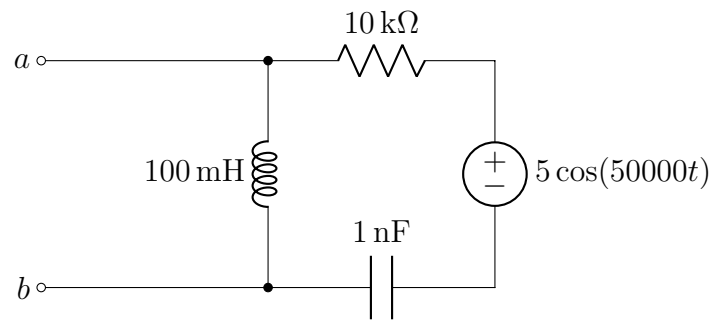

- Determine the equivalent Thévenin circuit in the phasor domain.

### Exercise 3 - Op Amp

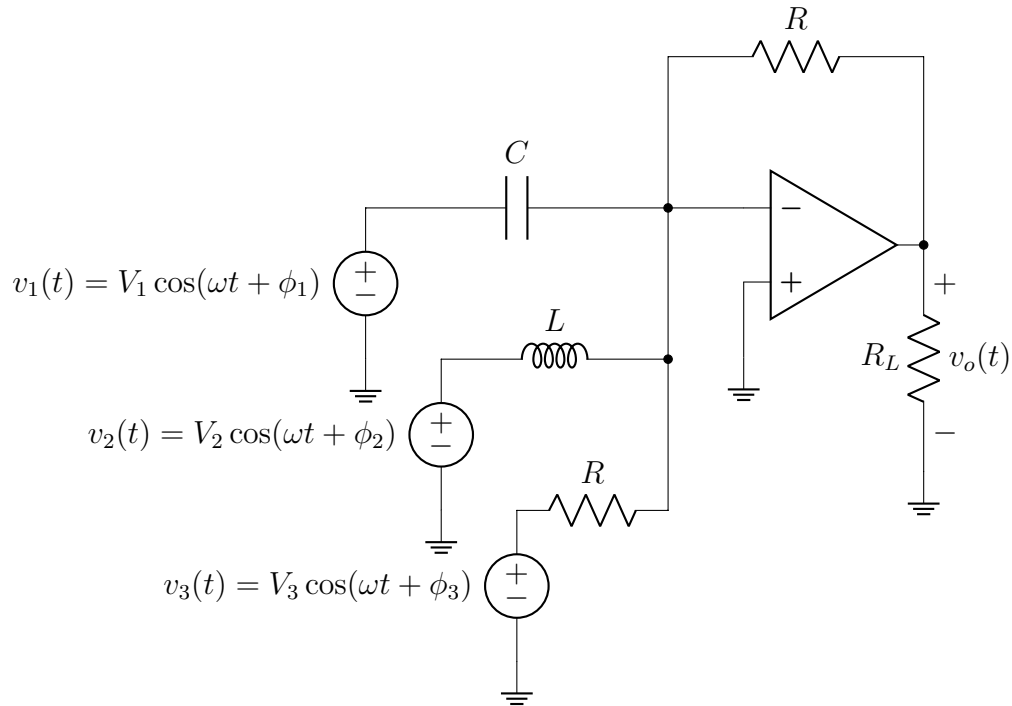

The operational amplifier is supposed to be ideal.

Questions:

1. Determine the phasor  $\mathbf{V}_o$  of  $v_o(t)$  as a function of  $R$ ,  $L$ ,  $C$ ,  $\omega$ ,  $\mathbf{V}_1$  ( $V_1/\phi_1$ ),  $\mathbf{V}_2$  ( $V_2/\phi_2$ ) and  $\mathbf{V}_3$  ( $V_3/\phi_3$ )
2. Supposing that  $v_1(t) = v_2(t)$ , which angular frequency leads to  $v_o(t) = -v_3(t)$ ?
3. Supposing that  $v_2(t) = 0$  and  $v_1(t) = v_3(t)$ , which frequency leads to

$$v_o(t) = \frac{\sqrt{2}}{2} V_1 \cos(\omega t + \phi_1 + 225^\circ)$$