

NAME:

## Homework 2

-


### DC Circuits & RC & RL

**Deadline:** Tuesday, 26 April, 2022, 11:55 PM

Please send your solutions in electronic version by NYU Brightspace.


**Exercise 1 - Maximum power**

Determine what value of resistance would absorb maximum power from the circuit when connected across terminals  $a$  and  $b$ .

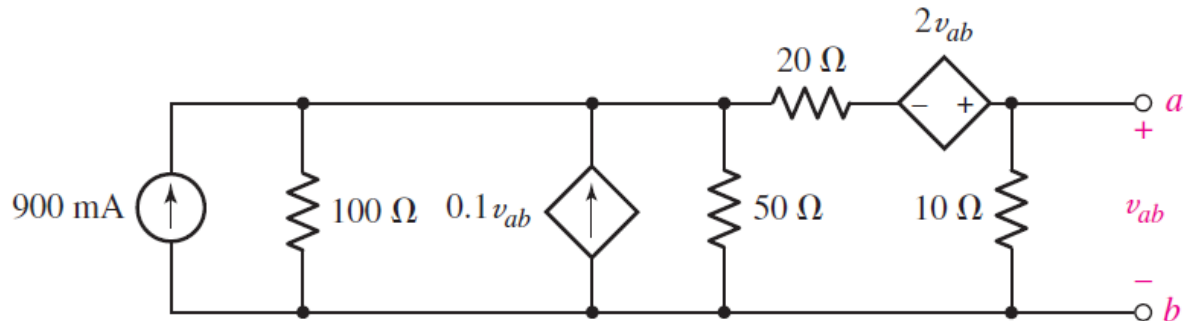

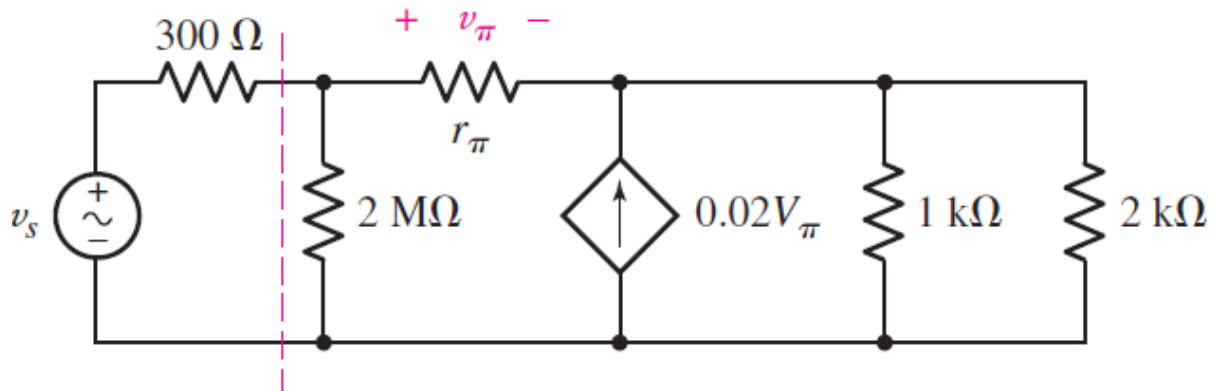**Exercise 2 - Thevenin****equivalent**

Determine the Thevenin equivalent resistance of the circuit to the right of the dashed line. This circuit is a common-collector transistor amplifier and you are calculating its input resistance.




---

**Exercise 3 - Capacitor**


---

Assuming the passive sign convention, sketch the voltage which develops across the terminals of a 2.5 F capacitor in response to the current waveforms shown below.

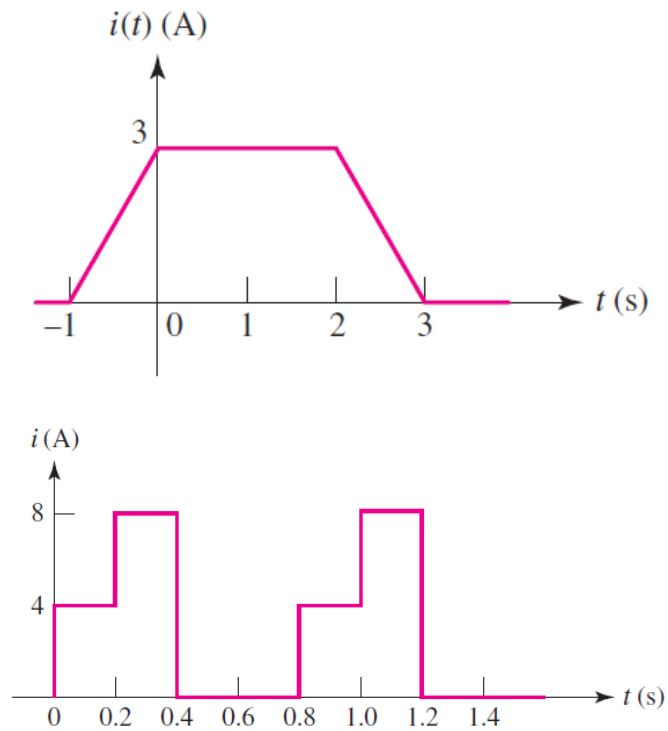

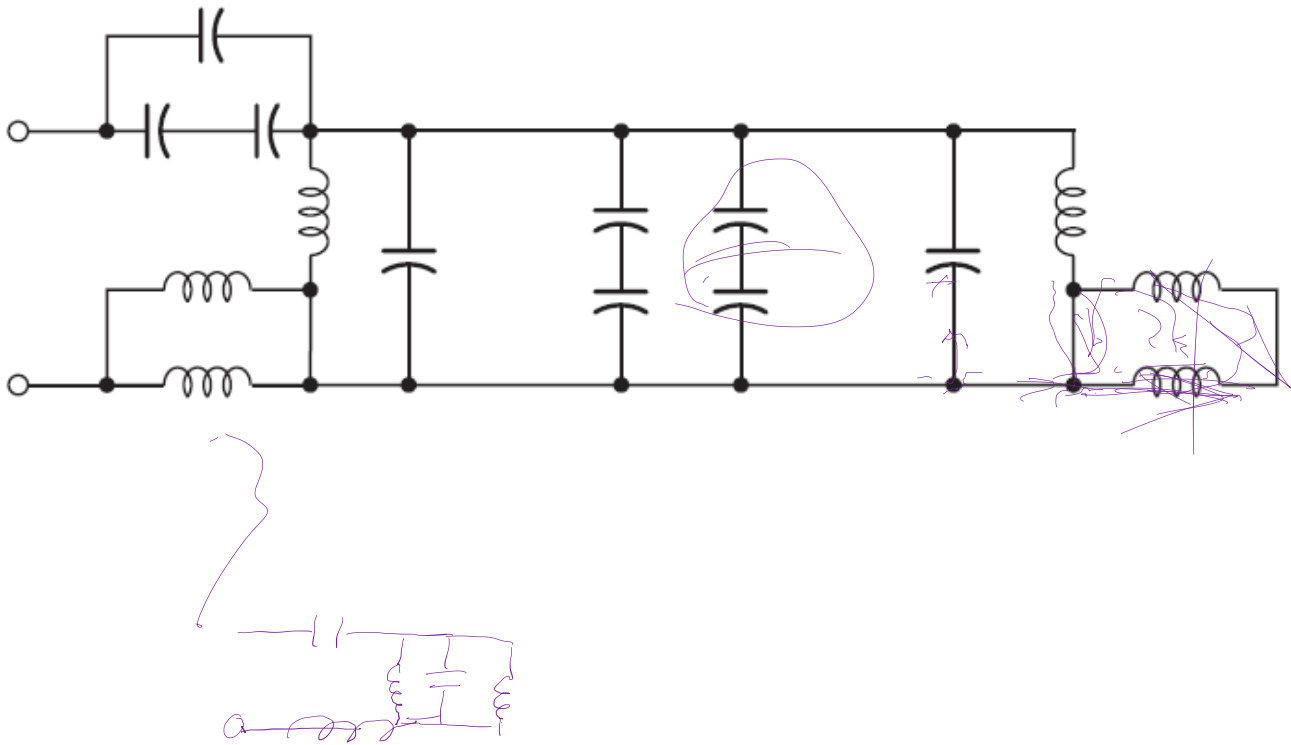
**Exercise 4 - Equivalent inductor and capacitor**

Reduce the network to the smallest possible number of components if each inductor is 1 nH and each capacitor is 1 mF.



## Exercise 5 - RC

## Circuit

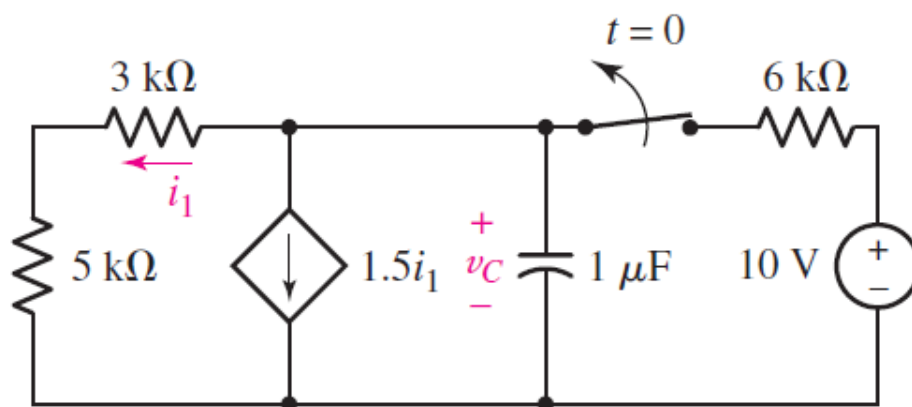Determine  $v_C(0^-)$ ,  $v_C(0^+)$ ,  $v_C(t > 0)$ 

## Exercise 6 - RL

## Circuit

Find expressions of  $i_1(t)$  and  $i_L(t)$  for  $t > 0$

