

NAME:

Homework 3


-

Sinusoidal analysis

Deadline: Wednesday, 11 May 2022, 11:55 PM

You can send your solutions in electronic version to NYU Brightspace/Assignment. **No extended deadline!**

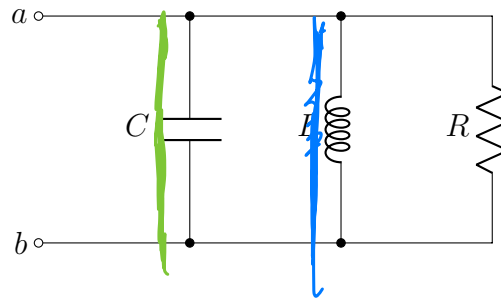Exercise 1 - Equivalent impedance/admittance



growth
of functions

$\propto 0$
 $j\omega L$, $\frac{1}{j\omega C}$, R
 $\propto \infty$ $\propto 0$
 $\omega \rightarrow 0$

- Determine the equivalent impedance of this network, as a function of the angular frequency ω .
- Which element is it equivalent to when $\omega \rightarrow 0$?
- Which element is it equivalent to when $\omega \rightarrow \infty$?
- Which element is it equivalent to when $\omega = \frac{1}{\sqrt{LC}}$?

$\omega \rightarrow \infty$


$$Z_{ab} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{R \cdot j\omega L}{\underbrace{j\omega L + R}_{\propto 0} - \underbrace{\omega^2 LC}_{\propto 0}}$$

$$\omega \rightarrow 0 \quad Z_{ab} \propto \frac{R \cdot j\omega L}{R} = j\omega L \quad \text{An inductor}$$

$$\omega \rightarrow \infty \quad \frac{1}{R} \propto 0 \quad \frac{1}{j\omega L} \propto 0 \quad \text{compared to } j\omega C \quad Z_{ab} = \frac{1}{j\omega C} \quad \text{A capacitor}$$

$$\omega = \frac{1}{\sqrt{LC}} \quad Z_{ab} = R \quad \text{A resistor}$$

Exercise 2 - Thévenin equivalence

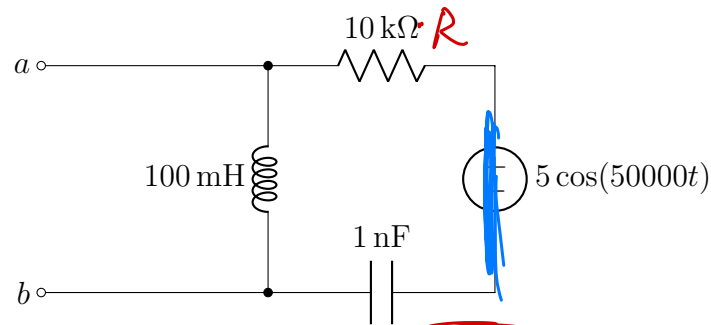


- Determine the equivalent Thévenin circuit in the phasor domain.


① $\omega = 50000 \text{ rad/s}$ $V_s = 5 \angle 0^\circ \text{ V}$ $Z_L = j\omega L = j500 \Omega$ $Z_C = \frac{1}{j\omega C} = -j200 \Omega$

$$V_{ab} = V_s \cdot \frac{Z_L}{R + Z_L + Z_C} = \frac{250}{109} j + \frac{75}{109} \text{ V} =$$

$$Z_{ab} = Z_L \parallel (R + Z_C) = 10^3 \cdot \left(\frac{25}{109} + j \frac{470}{109} \right)$$

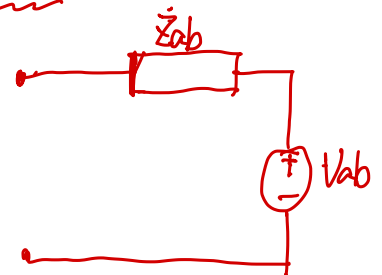

Exercise 3 - Op Amp

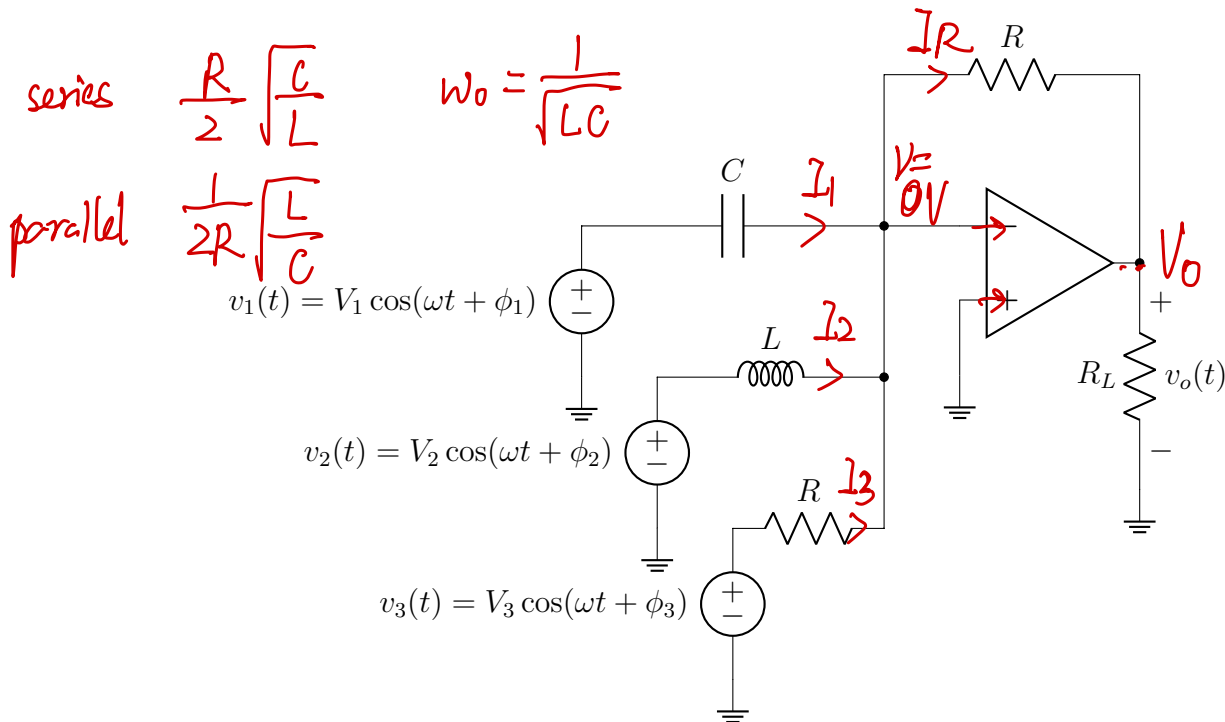

The operational amplifier is supposed to be ideal.

Questions:

1. Determine the phasor \mathbf{V}_o of $v_o(t)$ as a function of R , L , C , ω , \mathbf{V}_1 (V_1/ϕ_1), \mathbf{V}_2 (V_2/ϕ_2) and \mathbf{V}_3 (V_3/ϕ_3)
2. Supposing that $v_1(t) = v_2(t)$, which angular frequency leads to $v_o(t) = -v_3(t)$?
3. Supposing that $v_2(t) = 0$ and $v_1(t) = v_3(t)$, which frequency leads to

$$v_o(t) = \frac{\sqrt{2}}{2} V_1 \cos(\omega t + \phi_1 + 225^\circ)$$

$$V_o = \frac{\sqrt{2}}{2} V_1 \angle \phi_1 + 225^\circ$$

$$\triangleright I_R = I_1 + I_2 + I_3 = \frac{0 - V_o}{R} = \frac{V_1}{\frac{1}{j\omega C}} + \frac{V_2}{j\omega L} + \frac{V_3}{R}$$

$$\Rightarrow V_o = -R \cdot \left(j\omega C V_1 + \frac{1}{j\omega L} V_2 + \frac{1}{R} V_3 \right)$$

$$2) v_1(t) = v_2(t) \Rightarrow V_1 = V_2 \quad V_o = -R \cdot \left(j\omega C V_1 + \frac{1}{j\omega L} V_1 + \frac{1}{R} V_3 \right) = -V_3$$

$$j\omega C V_1 = -\frac{1}{j\omega L} V_1 \Rightarrow -j\omega L \cdot j\omega C = -1 \Rightarrow \omega^2 = \frac{1}{LC} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

$$3) V_2 = 0 \text{ \& } V_1 = V_3 \quad V_o = -R (j\omega C V_1 + \frac{1}{R} V_1) = V_1 (-1 - jR\omega C)$$

$$= \frac{\sqrt{2}}{2} V_1 \angle \phi_1 + 225^\circ$$

$$-\frac{1}{2}(1+j)V_1 - V_1(1+jR\omega C)$$

$$\text{Assume } \phi_1 = 0 \quad V_o = \frac{\sqrt{2}}{2} V_1 \angle 225^\circ = V_1 (-1 - jR\omega C) \Rightarrow \frac{\sqrt{2}}{2} \cdot (-\frac{\sqrt{2}}{2} - j\frac{\sqrt{2}}{2}) V_1 = -V_1 (1 + jR\omega C)$$

$$\Rightarrow R\omega C = 1 \Rightarrow \omega = \frac{1}{RC}$$