

Circuits

-

Basic concepts

NYU
上海



SHANGHAI
纽约大学

Spring 2022

Value of quantity



上海纽约大学
NYU SHANGHAI

Measurable quantity

Both:

- a number
- a unit

Examples

- 12 kilograms
- 81.3 kilometers
- 11.5 degree celsius
- 22 minutes
- ...

System of Units

上海纽约大学
NYU SHANGHAI

International System of Units (**SI**)

Base quantity	Name	Symbol
length	meter	m
mass	kilogram	kg
time	second	s
electric current	ampere	A
temperature	kelvin	K
amount of substance	mole	mol
luminosity	candela	cd

System of Units



No other units?

How about **joules** (energy), **watts** (power), **newtons** (force), **volts** (voltage), ...?

Every other unit can be derived from the 7 base units.

Examples

- $1 \text{ joule} = 1 \text{ J} = 1 \text{ kg.m}^2.\text{s}^{-2}$
- $1 \text{ watt} = 1 \text{ W} = 1 \text{ J.s}^{-1} = 1 \text{ kg.m}^2.\text{s}^{-3}$
- $1 \text{ newton} = 1 \text{ N} = 1 \text{ kg.m.s}^{-2}$
- $1 \text{ volt} = 1 \text{ V} = 1 \text{ kg.m}^2.\text{s}^{-3}.\text{A}^{-1}$

Scales



Decimal system for larger and smaller units

Factor	Name	Symbol	Factor	Name	Symbol
10^{-24}	yocto	y	10^{24}	yotta	Y
10^{-21}	zepto	z	10^{21}	zetta	Z
10^{-18}	atto	a	10^{18}	exa	E
10^{-15}	femto	f	10^{15}	peta	P
10^{-12}	pico	p	10^{12}	tera	T
10^{-9}	nano	n	10^9	giga	G
10^{-6}	micro	μ	10^6	mega	M
10^{-3}	milli	m	10^3	kilo	k
10^{-2}	centi	c	10^2	hecto	h
10^{-1}	deci	d	10^1	deca	da
10^0					

Charge



Charge conservation

Physics law of conservation of charge: charge cannot be created or destroyed, only transferred

We will consider the **flow of charges** instead (referred to the **current**)

Unit of charge

- 1 coulomb = 1 C (= 1 A.s)

2 types of charge

- positive: 1 proton = 1.602×10^{-19} C
- negative: 1 electron = -1.602×10^{-19} C

Current



Electric current

It is the **rate of change of charge**, measured in amperes (A)

Two main types of current

- **Direct Current (DC)**: current remains constant
- **Alternating Current (AC)**: current varies sinusoidally with time

Formula

$$i = \frac{dq}{dt}$$

i : current in amperes


q : charge in coulombs

t : time in seconds

Current



上海纽约大学
NYU SHANGHAI

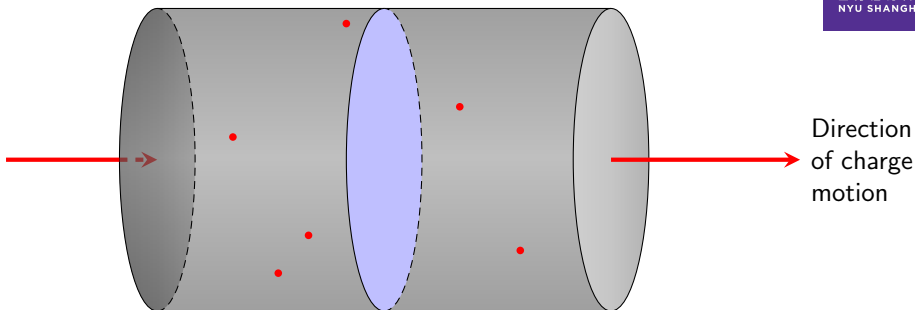

• individual charges

Definition of current: 1 ampere corresponds to 1 coulomb of (positive) charges passing through the cross section in 1 second

Current



Current: proton or electron movement?

Physically, current in circuits are obtained from the movement of electrons.

Protons are not moving.


Representation

Direction of current must be specified by an **arrow**

Current/electron directions

Electrons move in the opposite direction of current

Current

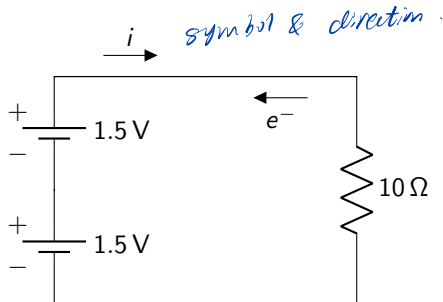


i is defined positively in the opposite direction to electron movement

Current

上海纽约大学
NYU SHANGHAI

Propagation rate

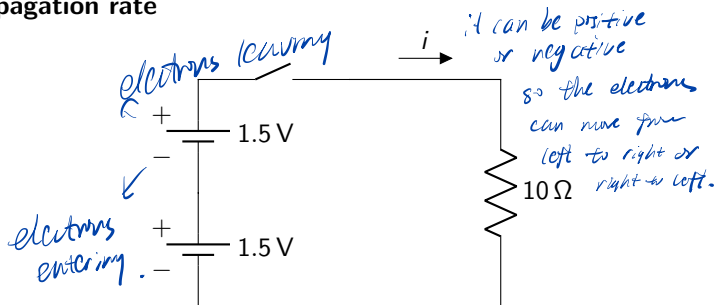

- Propagation is close to speed of light
- Effects are supposed instantaneous

Current



Assumptions for this course

- Lumped-parameter system (propagation is instantaneous)
- **No charge** can be stored
(every circuit element has a net charge of **zero**)
- No magnetic effect

Voltage



Definition

It is the **difference in electric potential** between **two points**

Other names: electric potential difference, electric pressure or electric tension


Physical interpretation

- Quantity of energy needed per unit of charge to move a test charge between the two points
- Voltage can push charges in one direction

Representation

We use polarity (+ and – on batteries for example) to indicate the direction of voltage

Voltage

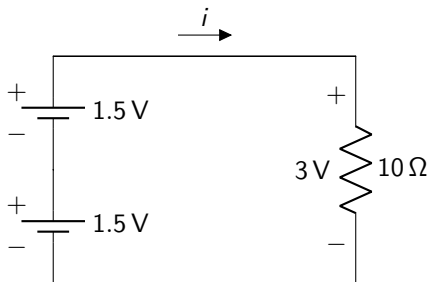上海纽约大学
NYU SHANGHAI

- the voltage sources push current through the circuit
- the resistor resists the flow of charge

Power

上海 纽约 大学
GHAI

Power

It is the **time rate of energy transfer** p , measured in watts (W)

Convention

- Circuit elements that **absorb power** have a **positive** value of p
- Circuit elements that **produce power** have a **negative** value of p

Formula

$$p = \frac{dw}{dt} = \pm v \cdot i$$

p : power in watts

w : energy in joules

t : time in seconds

v : voltage in volts

i : current in amperes

Power

上海纽约大学
NYU SHANGHAI

Conservation of energy

The **net power** absorbed by a **circuit** is equal to **0**

Interpretation

$$\sum_n p_n = 0$$

The watts absorbed by some circuit elements have been produced by some other elements

Power



上海纽约大学
NYU SHANGHAI

if it's negative, then this element is producing power.

Passive sign convention (PSC)

Current enters the positive terminal of an element

but what about a battery?


Sign in power formula

- PSC satisfied: $p = v \cdot i \rightarrow$ we are calculating the absorbed power
 - PSC not satisfied: $p = -v \cdot i \rightarrow$ current doesn't enter the positive terminal
- always the absorbing power of one element the positive polarity.*

IMPORTANT!!! *it will never be the producing power*

PSC rule is very important and should be examined very carefully!!!
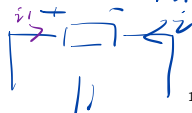
$$\begin{aligned} P &= -vi \\ &= v(-i) \\ &= v i' \end{aligned}$$



Independent voltage source



上海纽约大学
NYU SHANGHAI


*When is the voltage ever dependent on current?
正常不是V固定，I根据负载来变化吗？*

Definition (ideal)




An independent voltage source is characterized by a terminal voltage which is completely independent of the current through it

this is never the real case. the energy will be infinite.

Symbols

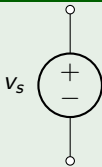

Usual

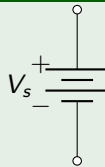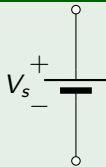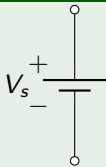

Batteries *100 voltage sources*

$P = I V$ may be infinite.


Independent current source

上海纽约大学
NYU SHANGHAI

Definition (ideal)

An independent current source is characterized by a current which is completely independent of the voltage across it

Symbols

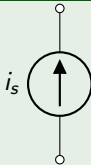

What is a current source? isn't current a product of potential difference?

Ideal sources

上海纽约大学
NYU SHANGHAI

lights dim when the AC is turned on for seconds

Model

Be careful! The independent sources are **models** for real sources.

These models do not represent exactly the real physical devices. The idealized sources could theoretically deliver infinite power, which is not possible in real life.

But, for example, 12V batteries in cars really maintain a constant 12V terminal voltage as long as the current does not exceed several amperes.

Dependent voltage sources



Definition



A dependent voltage source is characterized by a terminal voltage which depends on a quantity (voltage or current) existing somewhere else in the circuit.

analyzing complex & integrated circuits

Purpose

The models of dependent voltage sources usually appear in equivalent electrical models for some electronic devices (transistors, operational amplifiers, ...).

Symbol

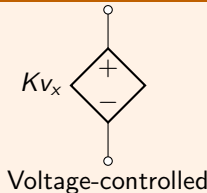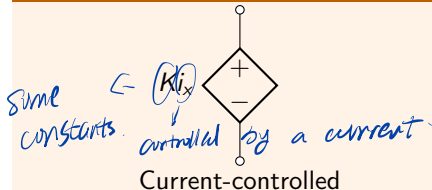

Dependent current sources

上海纽约大学
GHAI

Definition


A dependent current source is characterized by a current which depends on a quantity (voltage or current) existing somewhere else in the circuit.

Purpose


The models of dependent current sources usually appear in equivalent electrical models for some electronic devices (transistors, operational amplifiers, ...).

sources are called active elements in circuits.

Symbol

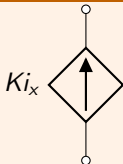

Current-controlled

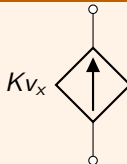

Voltage-controlled



Ohm's law

Simplest passive element: resistor

The voltage across a conductive material is **directly proportional** to the current flowing through it

Ohm's law

$$v = R \cdot i$$

R is called the **resistance**

The unit of resistance is **ohm** (Ω , equivalent to 1 V/A)

☆
here the v & i
should follow the PSC

otherwise R
will be a negative #

Symbol

resistor is a passive
element. they
absorb power.



no matter PSC is satisfied or not
the power for all resistors is positive

Ohm's law

上海纽约大学
NYU SHANGHAI

Precautions

Be careful with Ohm's law and the **directions** of current and voltage

Similarly to the definition of power absorbed, a more accurate formula should be $v = \pm R \cdot i$

Passive sign convention (again)

Current enters the **positive** terminal of an element


- PSC satisfied: $v = R \cdot i$
- PSC not satisfied: $v = -R \cdot i$

Ohm's law



上海纽约大学
NYU SHANGHAI


Compute the power absorbed by each part.

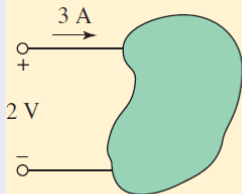

(a)


6 W

absorbing power.

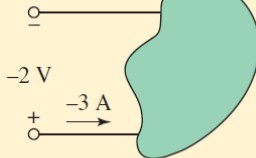

(b)

6 W

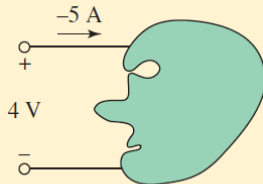

(c)

-20 W.
which means
some part here
is producing power

Ohm's law



上海 纽约 大学
NYU SHANGHAI

Power absorbed

A resistor **Joule effect** power (check exercise)

The absorbed power is dissipated into **heat**.

This phenomena is called **Joule effect**