

$$V = V_1 + V_2$$

$$V = \frac{V}{R_1 + R_2}$$

$$V_1 = iR_1 = V \cdot \frac{R_1}{R_1 + R_2}$$

$$V_2 = iR_2 = V \cdot \frac{R_2}{R_1 + R_2}$$

now expand this case  
to n resistors.

$$V_k = \frac{R_k}{R_1 + R_2 + \dots + R_n} V$$


Current Division

## Exercises 03

### Series and parallel equivalences Voltage and current division


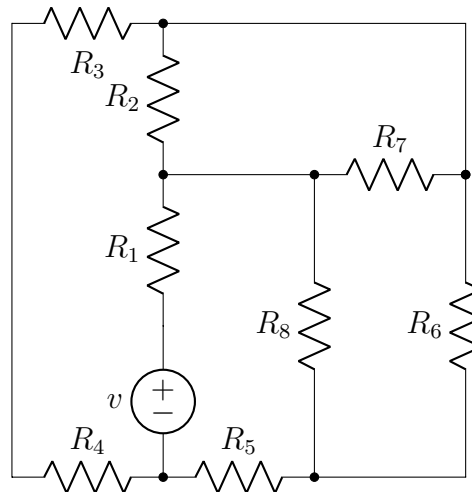
#### Exercise 1 - Series and parallel connections




- Which elements are connected in series?  $R_3, R_4$  ✓
- Which elements are connected in parallel?  $R_2, R_7$  ✓

#### Exercise 2 - Voltage division

$$V_1 = \frac{R_1}{R_1 + R_2} V$$

$$V_2 = \frac{R_2}{R_1 + R_2} V$$

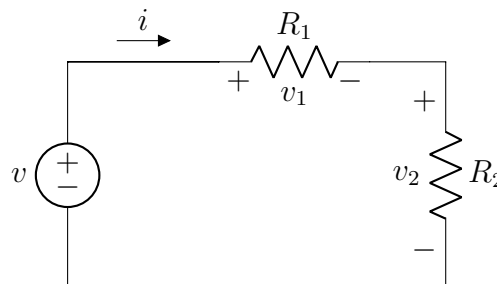

- Determine  $v_1$  and  $v_2$  as a function of  $v$  and the resistances.
- The voltage divided over the resistors. Which resistor exhibits the highest voltage knowing that  $R_1 > R_2$ ?

$$V_1 > V_2$$

# Current Division

$$i_1 + i_2 = \frac{V}{R_1} + \frac{V}{R_2} = i$$

unknown  $i_1$   $i_2$

known  $V$   $R_1$   $R_2$

$$i_1 = \frac{V}{R_1} = \frac{i (R_1 || R_2)}{R_1}$$

$$= \frac{i \frac{R_1 R_2}{R_1 + R_2}}{R_1} = i \frac{R_2}{R_1 + R_2}$$


$$\left[ R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}} \right]$$

$$i_2 = i \frac{R_1}{R_1 + R_2} \quad (\text{when there's only two parallel resistors})$$
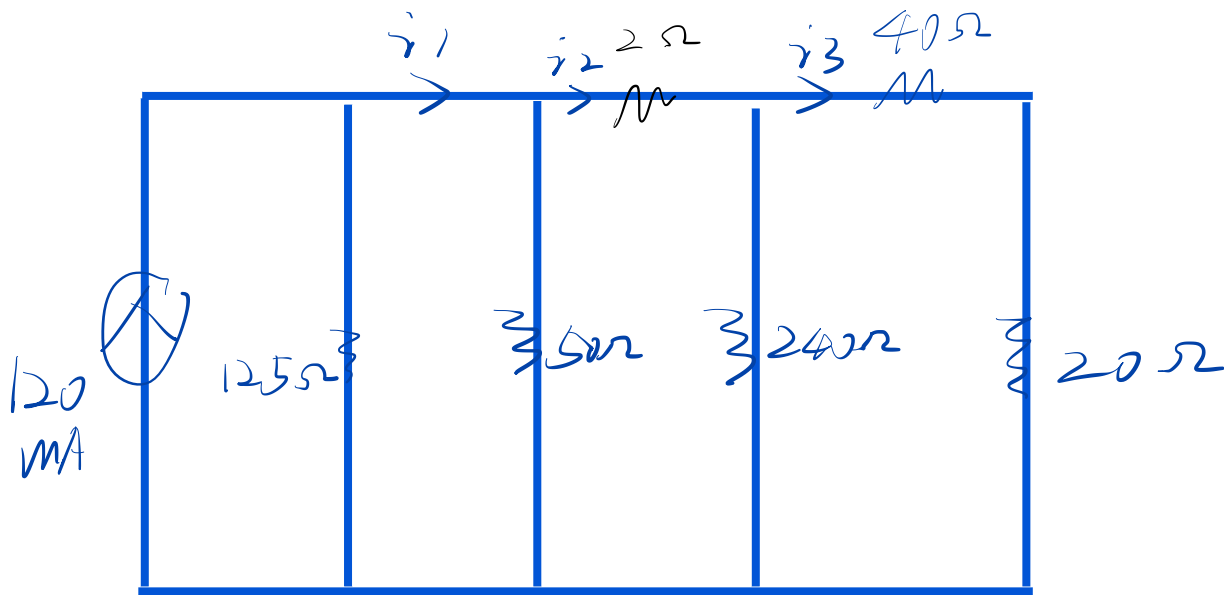
## n-Parallel Resistors

$$i_k = \frac{V}{R_k} = \frac{i \cdot \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}}{R_k}$$

$$= i \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$



Sometime

Current Division  
simplify the  
analysis.

$$240 \Omega \quad 60 \Omega$$

$$i_2 \cdot \frac{240}{300} = i_3 = 40 \text{ mA}$$

$$i_3 = i_2 \times \frac{240}{300}$$

$$i_2 = i_1 \cdot \frac{50}{50+50} = \frac{i_1}{2} = 50 \text{ mA}$$

$$i_1 = 120 \text{ mA} \cdot \frac{125 \Omega}{150 \Omega} = 100 \text{ mA}$$

not  $\frac{25 \Omega}{150 \Omega}$  but  $\frac{125 \Omega}{150 \Omega}$

it's current Division.




$$\dot{v}_1 = \dot{v} \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} = \dot{v} \frac{R_2}{R_1 + R_2}$$
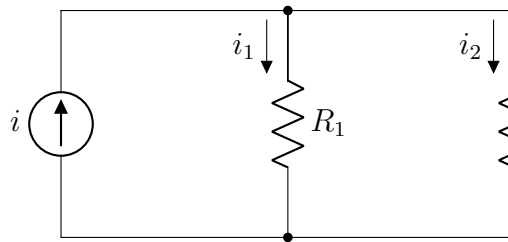
### Exercise 3 - Current division

$$\dot{v}_1 = \frac{R_2}{R_1 + R_2} \cdot \dot{v}$$

$$\dot{v}_2 = \frac{R_1}{R_1 + R_2} \cdot \dot{v}$$



$$(4\Omega + 4\Omega) \parallel 4\Omega = \frac{32}{12} = \frac{8}{3}\Omega$$

$$2\Omega \parallel (5\Omega + \frac{8}{3}\Omega) = 2\Omega$$

- Determine  $i_1$  and  $i_2$  as a function of  $i$  and the resistances.
- The current divided over the resistors. Which resistor exhibits the highest current knowing that  $R_1 > R_2$ ?


$$\dot{v}_1 < \dot{v}_2$$

$$\dot{v}_1 \cdot R_1 = \dot{v}_2 \cdot R_2$$

$$R_1 > R_2 \Rightarrow \dot{v}_1 < \dot{v}_2$$

$$\dot{v}_1 = 5A \cdot \frac{1\Omega}{1\Omega + R_1} = 5A \frac{1}{\frac{1}{R_1} + 1}$$
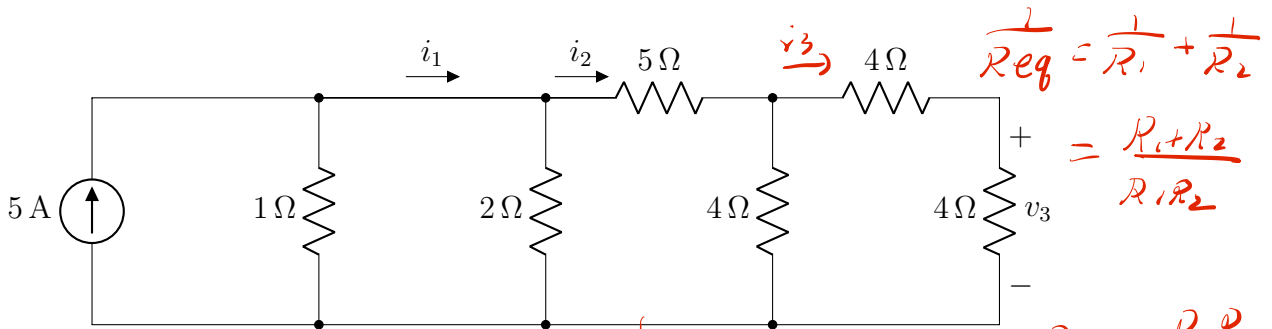
### Exercise 4 - Current and voltage division - Resistor equivalence



- Determine values for  $i_1$ ,  $i_2$  and  $v_3$ . Give the equivalent circuit for each case.

$$\frac{8\Omega}{4\Omega}$$

$$\dot{v}_3 = \frac{4}{12} \dot{v}_2 = \frac{\dot{v}_2}{3}$$

$$\frac{46\Omega}{28}$$

$$\frac{4+8}{4 \times 8} = \frac{3}{8}\Omega$$

$$\frac{3}{8}\Omega + 5\Omega = \frac{43}{8}\Omega$$

$$\dot{v}_2 = \frac{2}{\frac{23}{3} + 2} \dot{v}_1$$

Wrong

$$\dot{v}_2 = \frac{2}{2 + \frac{43}{8}} \dot{v}_1 = \frac{16}{59} \dot{v}_1$$

$$\dot{v}_1 = \frac{28}{15} A$$

$$\frac{\frac{43}{8} + 2}{\frac{43}{8} \times 2} = \frac{59}{86}\Omega$$

$$\dot{v}_2 = \frac{2}{5} A$$

$$\dot{v}_1 = \frac{1}{1 + \frac{59}{86}} \times 5 = \frac{86}{29} A$$

$$\dot{v}_3 = \frac{2}{15} A$$

$$\dot{v}_2 = \frac{1376}{1711} A$$

$$\dot{v}_3 = \frac{1376}{5133} A$$

$$v_3 = \dot{v}_3 \times 4\Omega = 1.07V$$

$$v_3 = \frac{8}{15} V$$