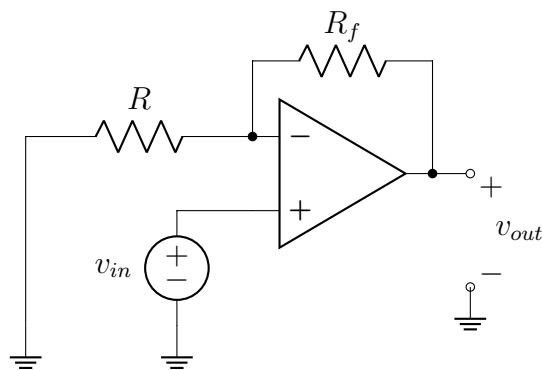


Exercises 09

-


Operational Amplifiers

Exercise 1 - Circuit 1




- Determine v_{out} . What is the name of that circuit?

Exercise 2 - Circuit 2

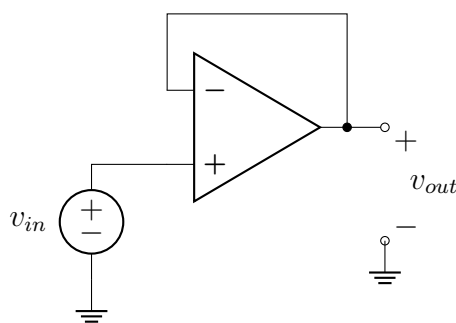


- Determine v_{out} . What is the name of that circuit?

Exercise 3 - Circuit 3

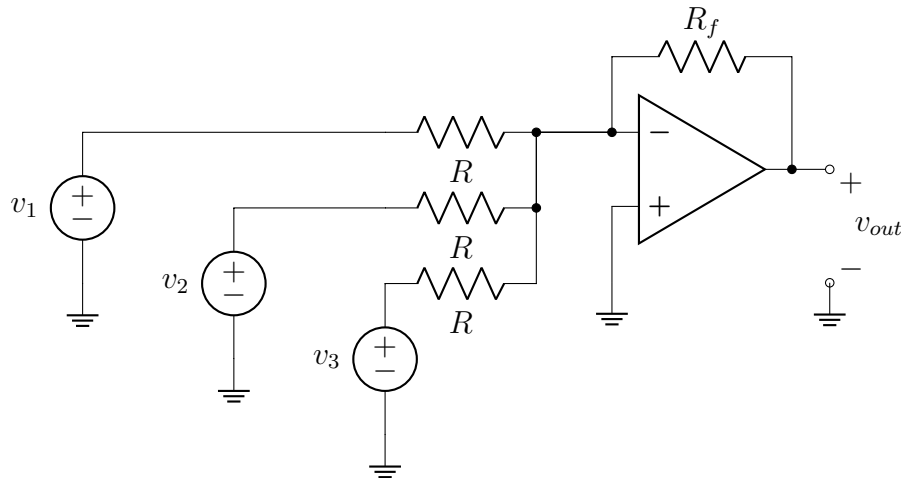


- Determine v_{out} . What is the name of that circuit?

Exercise 4 - Circuit 4

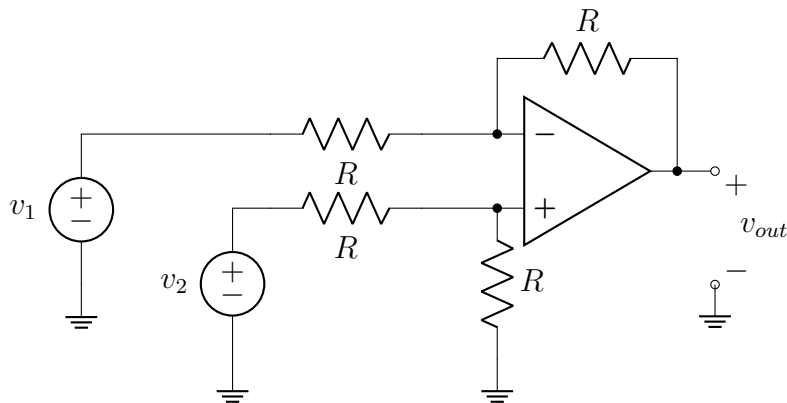


- Determine v_{out} . What is the name of that circuit?

Exercise 5 - Circuit 5

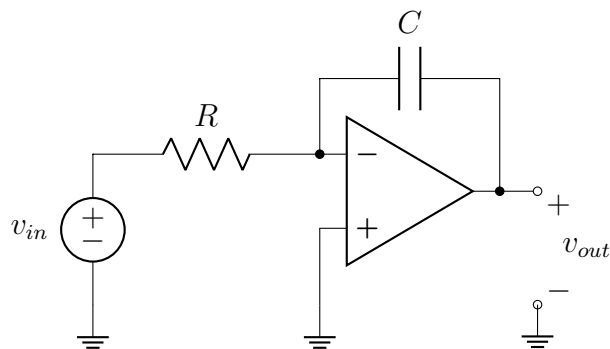

- Determine v_{out} . What is the name of that circuit?

Exercise 6 - Circuit 6

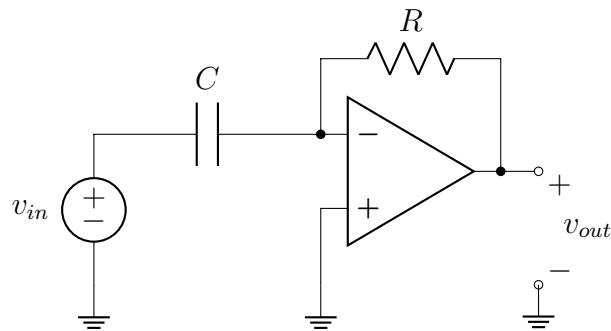

- Determine v_{out} . What is the name of that circuit?