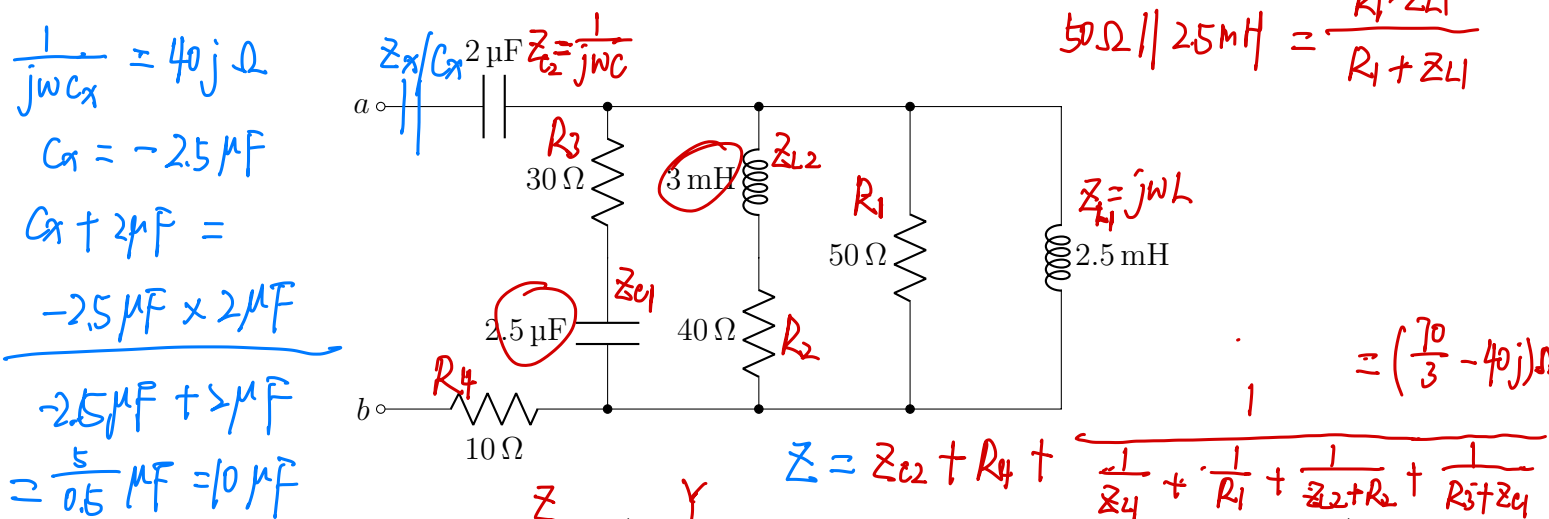


Exercises 10


- Phasors

Exercise 1 - Equivalent impedance/admittance 1




- Determine the equivalent impedance/admittance for an angular frequency $\omega = 10\,000$ rad/s.
- If we want the current and voltage for that equivalent impedance to be in phase for that frequency, by which value of capacitance should we change the $2 \mu F$ capacitor?

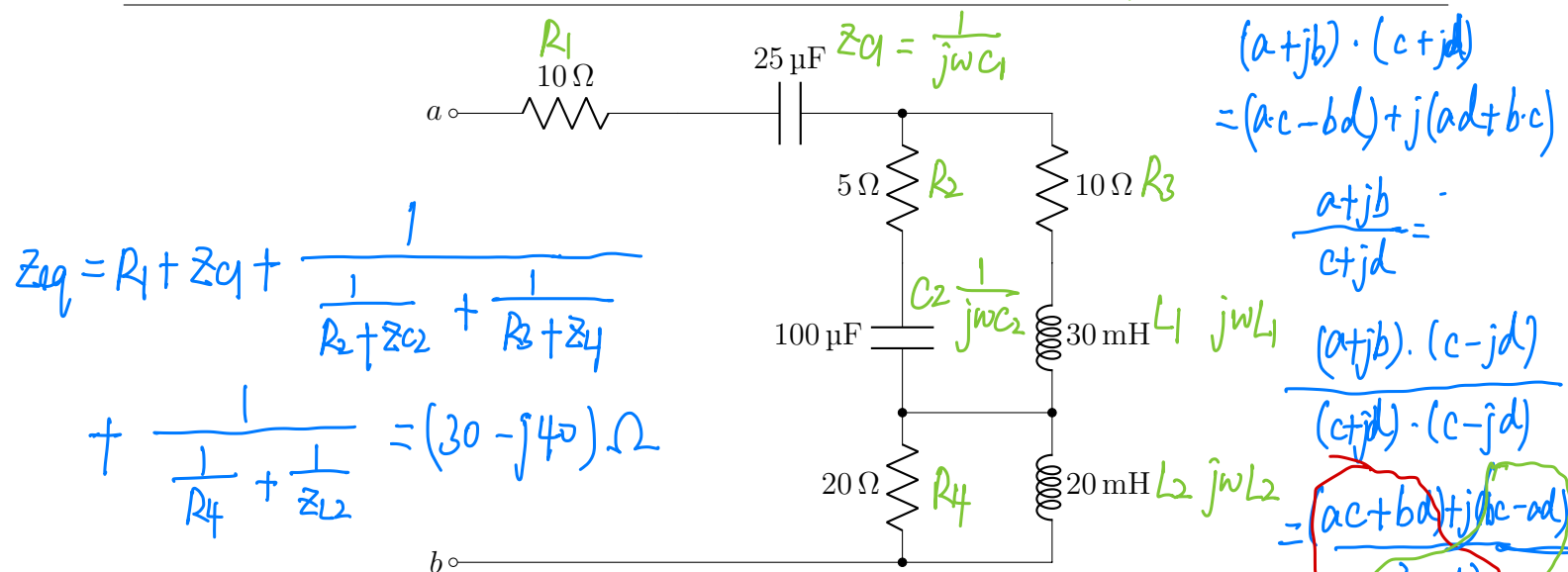Exercise 2 - Equivalent impedance/admittance 2




- Determine the equivalent impedance/admittance for an angular frequency $\omega = 1000$ rad/s.

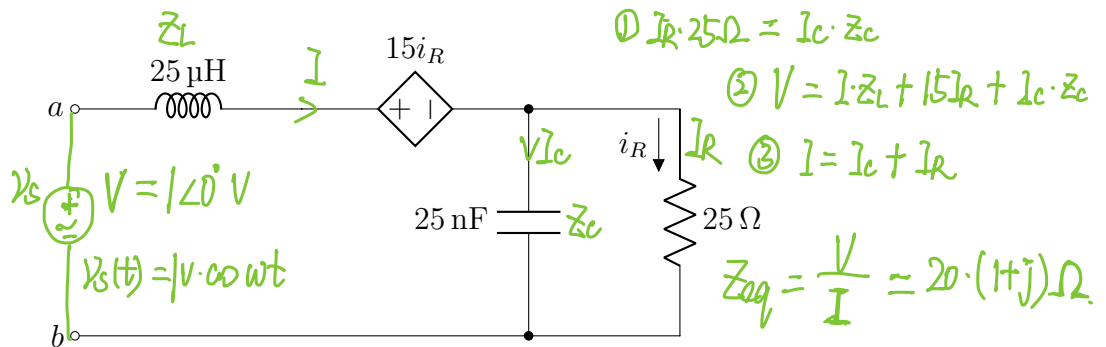Exercise 3 - Equivalent impedance/admittance 2




- Determine the equivalent impedance/admittance for an angular frequency $\omega = 1.6 \text{ Mrad/s}$.

Exercise 4 - Circuit 1

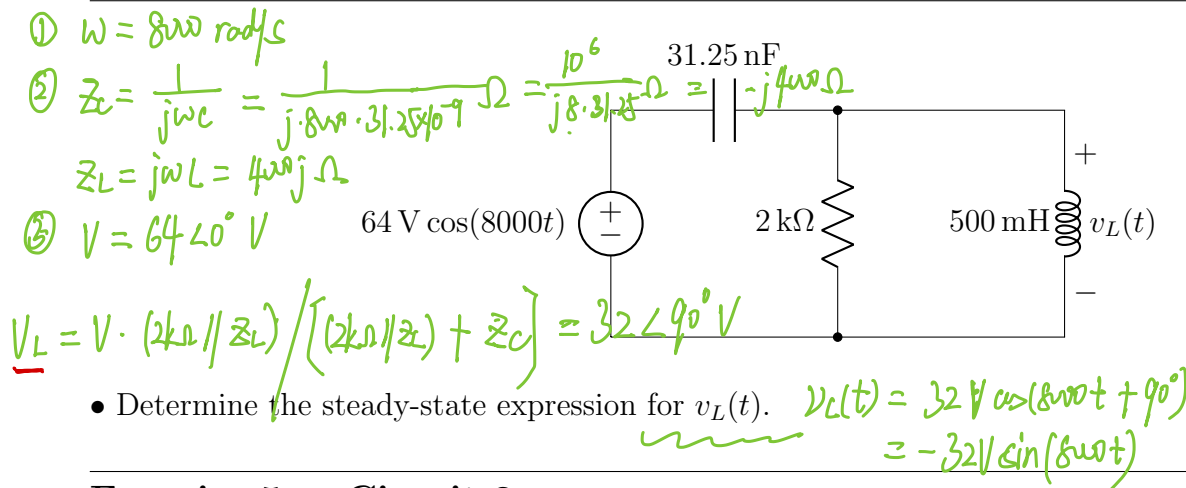

- Determine the steady-state expression for $v_L(t)$.

Exercise 5 - Circuit 2

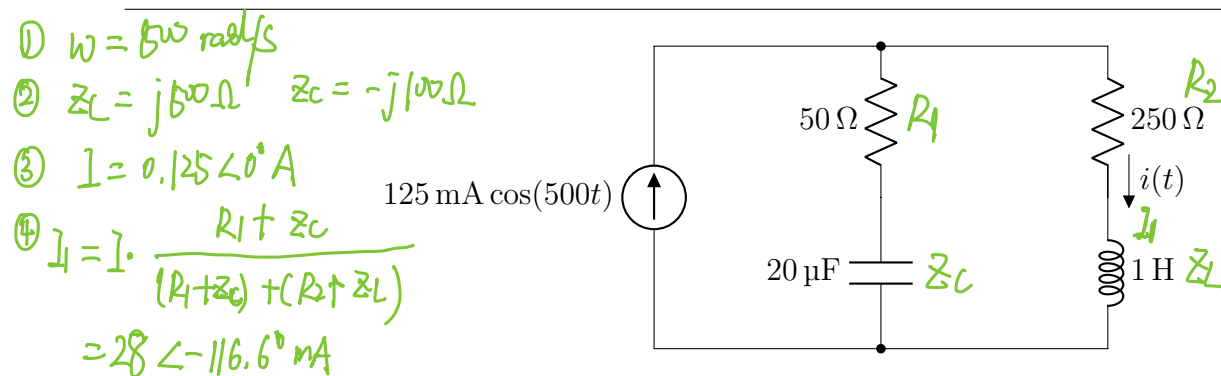

- Determine the steady-state expression for $i(t)$.

⑤ $i(t) = 28 \text{ mA} \cos(500t - 116.6^\circ)$

Exercise 6 - Source transformation

① $\omega = 4000 \text{ rad/s}$

② z_L, z_C

③ $V_1 = 240 \angle 53.13^\circ \text{ V}$

$240 \text{ V} \cos(4000t + 53.13^\circ)$

$V_2 = 96 \angle -90^\circ \text{ V}$

④ $V = (I_1 - I_2) \cdot (z_L \parallel 30\Omega \parallel 20\Omega \parallel z_C)$

- Using source transformation, determine the steady-state expression for $v(t)$.

⑤ $v(t) =$

Exercise 7 - Superposition

① $\omega_1 = 2000 \text{ rad/s}$

z_L, z_C

$V_1 = A_1 \angle \phi_1$

$240 \text{ V} \cos(2000t + 53.13^\circ)$

② $\omega_2 = 8000 \text{ rad/s}$

z_L, z_C

$V_2 = A_2 \angle \phi_2$

- Using superposition, determine the steady-state expression for $v(t)$.

③ $v(t) = A_1 \cos(2000t + \phi_1) + A_2 \cos(8000t + \phi_2)$

Exercise 8 - Circuit 3

① $I_a = \frac{I_b \cdot (15\Omega - j15\Omega)}{(25\Omega + j25\Omega)} = A_1 \angle \phi_1 \text{ A}$


② $I_c = I_a + I_b = 2 \angle 45^\circ \text{ A} = A_2 \angle \phi_2 \text{ A}$

③ $V_s = 5\Omega \cdot I_c + V_1 = A_3 \angle \phi_3 \text{ V}$

④ $i_a = A_1 \cos(800t + \phi_1)$

i_c


v_s

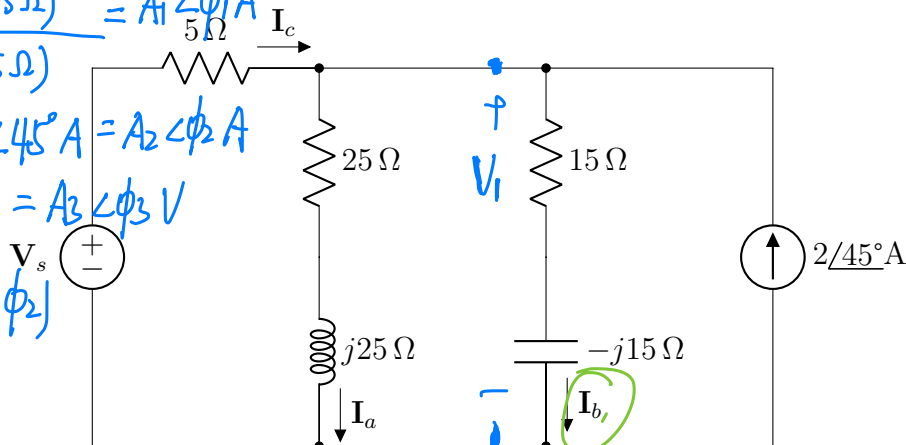

Knowing that $I_b = 5/45^\circ \text{ A}$:

- Determine I_a , I_c and V_s
- For $\omega = 800 \text{ rad/s}$, give the expression for $i_a(t)$, $i_c(t)$ and $v_s(t)$.

Exercise 9 - Circuit 4

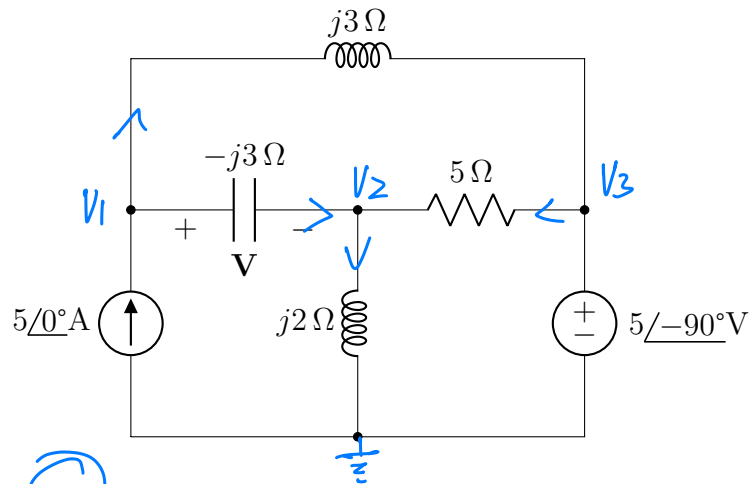

- Determine the phasor **V**.

$$\begin{aligned}
 & V_3 = 5 \angle -90^\circ \text{ V} \\
 & \frac{V_3 - V_2}{5 \Omega} + \frac{V_1 - V_2}{-j3 \Omega} = \frac{V_2}{j2 \Omega} \\
 & \frac{V_1 - V_2}{-j3 \Omega} + \frac{V_1 - V_3}{j3 \Omega} = 5 \angle 0^\circ \text{ A}
 \end{aligned}$$

$$\Rightarrow \begin{cases} V_1 = \\ V_2 = \\ V_3 = \end{cases}$$

$$V = V_1 - V_2$$